

**ENGINEER YOUR FUTURE**

**ECE CAREER FAIR**

- Network with industry personnel from various companies
- Attend talks by the companies
- Learn more about the available jobs and internships opportunities

**Date: 27 March 2015**

**Time: 12 – 5 PM**

**Venue: EA Foyer**

**Attire: Formal**

# EE2022 Electrical Energy Systems

## Per Unit Analysis- Examples and Revision

Lecturer : Dr. Sangit Sasidhar (elesang)

Slides prepared by Dr. Panida Jirutitijaroen

Department of Electrical and Computer Engineering

# 3 $\Phi$ -Steps of Per Unit Analysis


1. Choose  $S_B^{3\Phi}$  for the system.
2. Select  $V_B^{\text{line-to-neutral}}$  or  $V_B^{\text{line-to-line}}$  for different zones.
3. Calculate  $Z_B$  for different zones.
4. Express all quantities in p.u.
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.

Note that the **per unit circuit** is the circuit in **per-phase analysis** with normalization of the voltage magnitude at different locations. This means that **the phase of voltage** in per unit analysis **refers to the line-to-neutral voltage**.

# Example 1

- The one-line diagram of a three-phase power system is shown below. Select a **common base of 100 MVA** and 22kV on the generator side. Draw an impedance diagram with all impedances including the load impedance marked in per-unit. The manufacturer's data for each device is given as follow. 100MVA


- |                  |          |  |
|------------------|----------|--|
| ① – G1: 90 MVA   | 22kV     | <div style="border: 1px solid red; padding: 5px; display: inline-block;"> <math>X = 18\% = 0.18</math><br/> <math>X = 10\% = 0.1</math><br/> <math>X = 6\% = 0.06</math><br/> <math>X = 6.4\% = 0.064</math><br/> <math>X = 8\% = 0.08</math> </div> |
| ①-② – T1: 50 MVA | 22/220kV |  |
| ②-④ – T2: 40 MVA | 220/11kV |  |
| ①-③ – T3: 40 MVA | 22/110kV |  |
| ③-④ – T4: 40 MVA | 110/11kV |  |
- Three-phase Y-connected load absorbs 57 MVA 0.6 pf lagging at 10.45kV.
  - Line 1 and line 2 have per phase reactances of 48.4 and 65.43  $\Omega$  respectively.

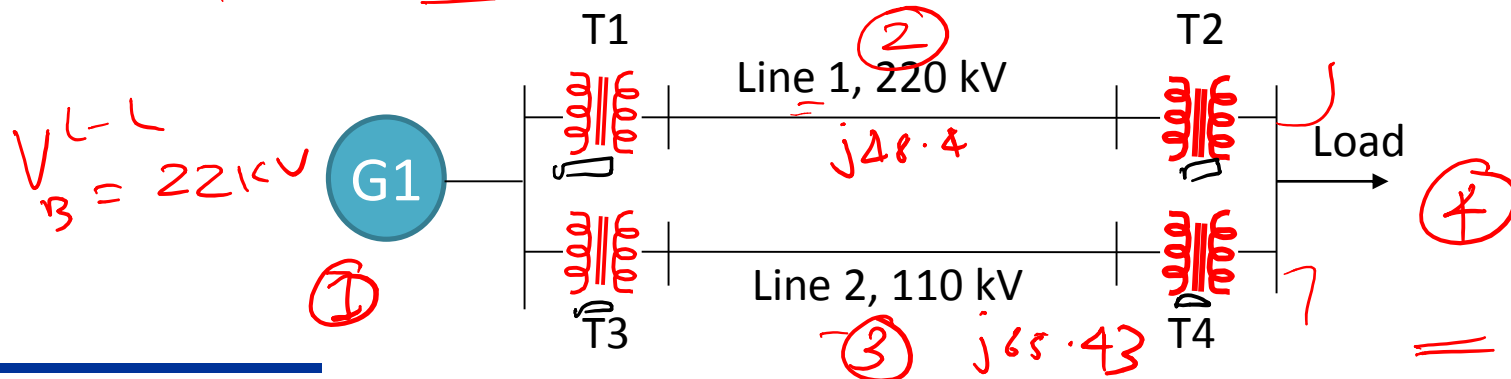

②

# Base Value for V Zone 2

①  $S_B^{3\phi} = 100 \text{ MVA}$

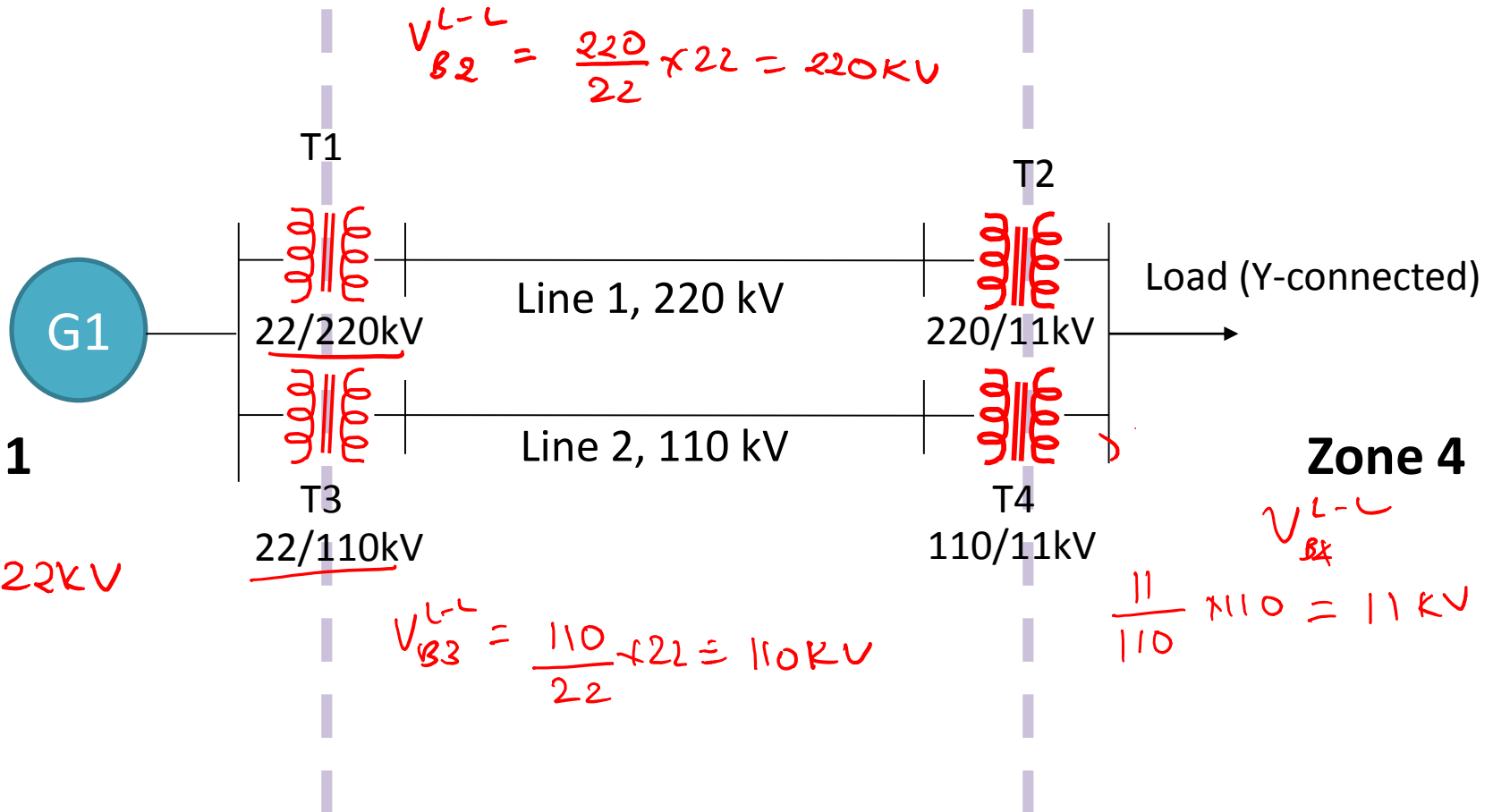


# ③ Base Impedances

$$Z_B = \frac{(V_B^L)^2}{S_B^3}$$
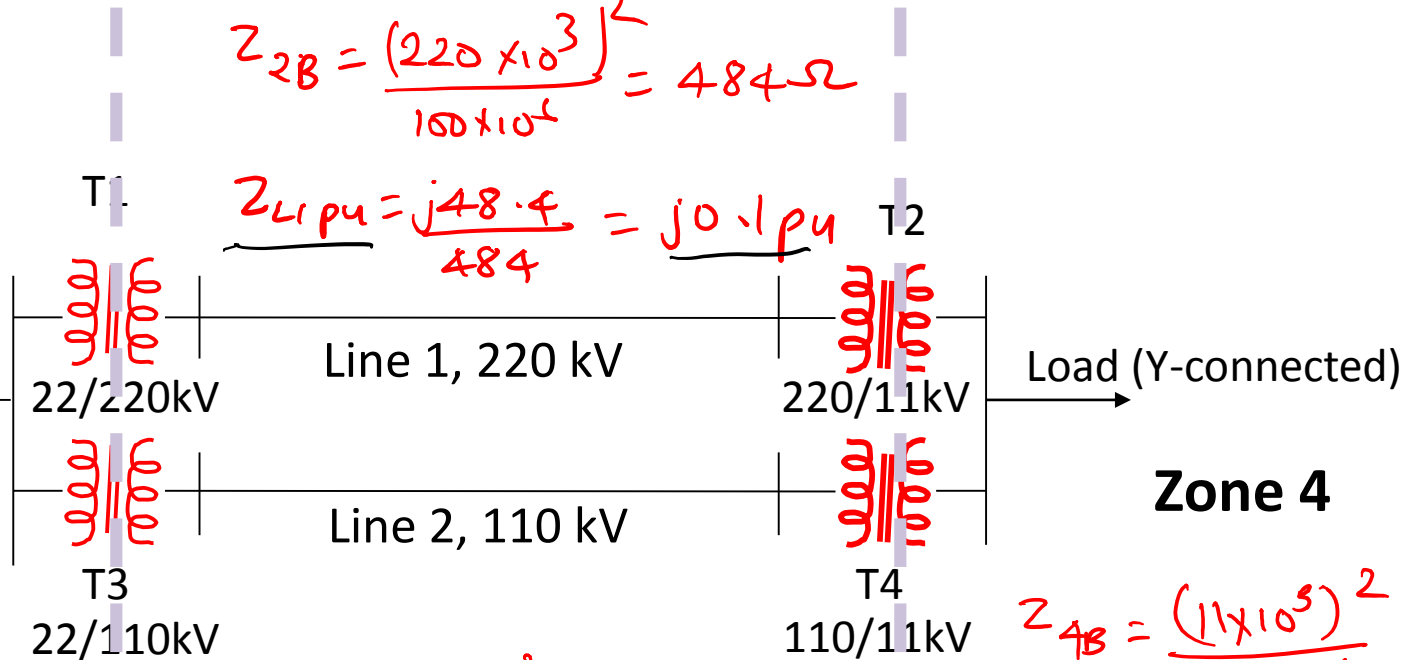
## Zone 2

$$Z_{2B} = \frac{(220 \times 10^3)^2}{100 \times 10^6} = 484 \Omega$$

$$Z_{L1 pu} = \frac{j48.4}{484} = j0.1 pu$$



$$Z_B = \frac{(22 \times 10^3)^2}{100 \times 10^6} = 4.84 \Omega$$

$$Z_{3B} = \frac{(110 \times 10^3)^2}{100 \times 10^6} = 121 \Omega$$

$$Z_{L2 pu} = j \frac{65.43}{121} = j0.54 pu$$

## Zone 3

$$Z_{4B} = \frac{(11 \times 10^3)^2}{100 \times 10^6} = 1.21 \Omega$$

Zone 2

# Load Impedance

$$pf = 0.6 \text{ lag}$$

$$\angle = 53.13^\circ$$

$$V_{LOAD}^{L-L} = 10.45 \text{ KV}$$

$$S_{LOAD}^{3\phi} = 57 \text{ MVA}$$

$$I_{LOAD} ?$$

$$Z_Y \quad \left\{ \quad S_{LOAD}^{3\phi} = \frac{3 V_{L-L}^2}{Z_Y} = \frac{V_{L-L}^2}{Z_Y}$$

$$\Rightarrow \underline{Z_Y} = \frac{V_{LL}^2}{S_{LOAD}^{3\phi}} = \frac{(10.45 \times 10^3)^2}{57 \times 10^6} = 1.1495 - j1.5327 \Omega$$

$$Z_Y = 1.1495 + j1.5327 \Omega$$

$$Z_{GB} = 1.21 \Omega \quad \Rightarrow \quad Z_{Ypu} = \frac{1.1495 + j1.5327}{1.21}$$

$$\boxed{Z_{Ypu} = 0.95 + j1.2667 \text{ p.u.}}$$

# ④ P.U. Impedance with Change of Base

$$Z_{pu}^{new} = Z_{pu}^{old} \times \left( \frac{V_{L-L}^{old}}{V_{L-L}^{new}} \right)^2 \times \left( \frac{S_{new}^{3\phi}}{S_{old}^{3\phi}} \right) = Z_{pu}^{old} \times \frac{S_{new}^{3\phi}}{S_{old}^{3\phi}}$$

G1 90 MVA 22kV  $X = 18\%$

$\Rightarrow$

$$X_G = j0.18 \times \frac{100}{90} = j0.2 pu$$

T1 80 MVA 22/220kV  $X = 10\%$

$\Rightarrow$

$$X_{T1} = j0.1 \times \frac{100}{80} = j0.125 pu$$

T2 40 MVA 220/11kV  $X = 6\%$

$\Rightarrow$

$$X_{T2} = j0.06 \times \frac{100}{40} = j0.15 pu$$

T3 40 MVA 22/110kV  $X = 6.4\%$

$\Rightarrow$

$$X_{T3} = j0.064 \times \frac{100}{40} = j0.16 pu$$



T4 40 MVA 110/11kV  $X = 8\%$

$\Rightarrow$

$$X_{T4} = j0.08 \times \frac{100}{40} = j0.2 pu$$



# Per Unit Equivalent Circuit

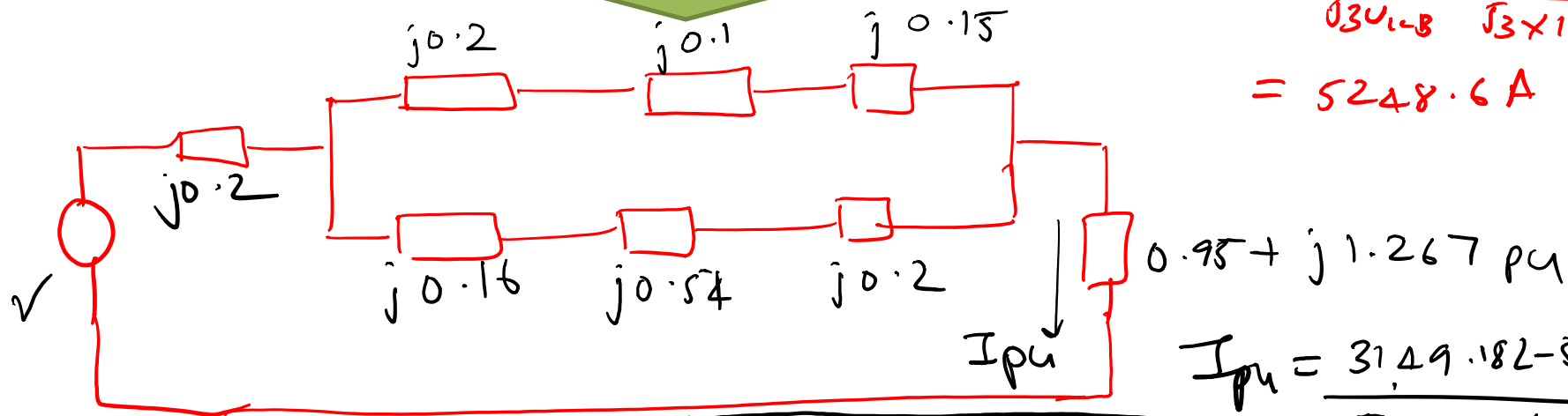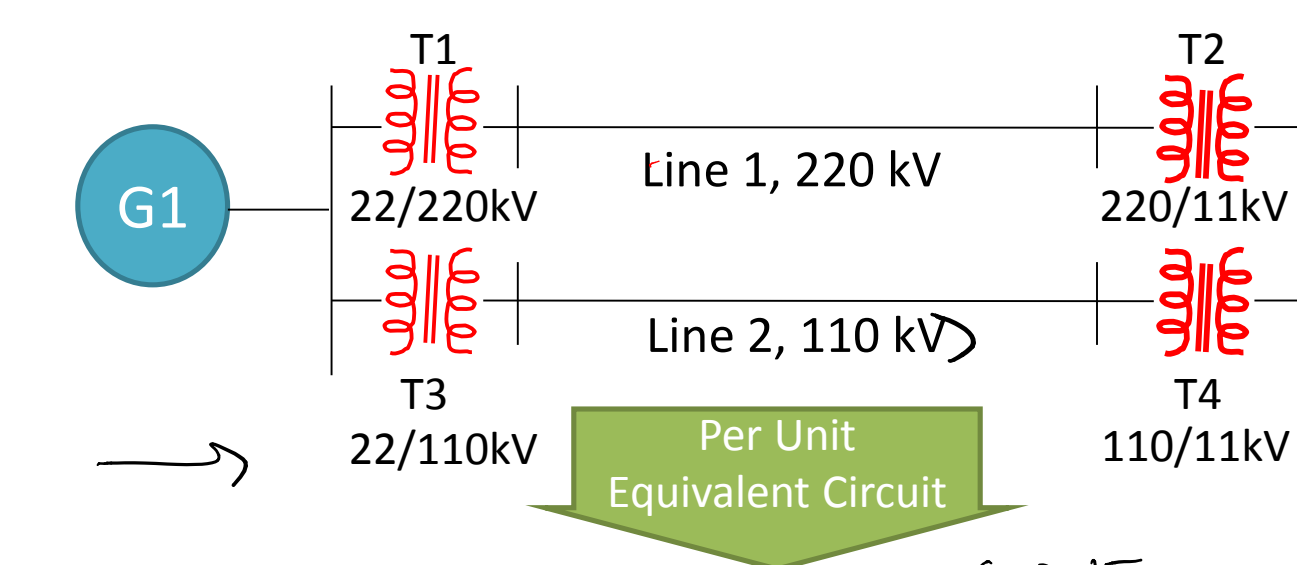

$$I_{pu} = 0.62 - 53.13^\circ$$

$$\textcircled{4} S^{\text{ref}} = \sqrt{3} V_{LL} I_L$$

$$I_L = \frac{57 \times 10^6}{\sqrt{3} \times 10^3 \times 11}$$


$$= 3149.18 \angle -53.13^\circ$$

$$I_B^{\text{ref}} = \frac{S^{\text{ref}}}{\sqrt{3} V_{LL}} = \frac{100 \times 10^6}{\sqrt{3} \times 11 \times 10^3}$$

$$= 5248.6 \text{ A}$$

$$I_{pu} = \frac{3149.18 \angle -53.13^\circ}{5248.6}$$

# Solve and Convert to Actual Quantities

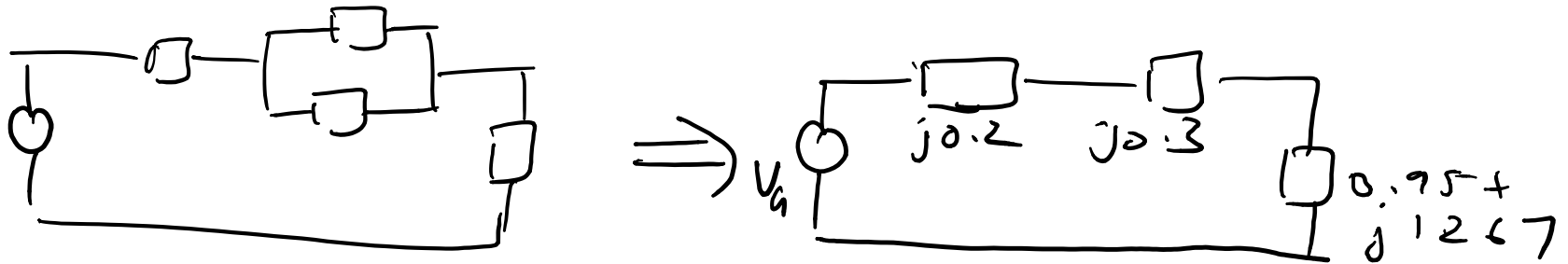



$$I_{pu} = \frac{V_{G, pu}}{Z_{pu}} \Rightarrow V_{G, pu} = I_{pu} \times Z_{pu}$$

$$= (0.6 \angle -53.13) \times (j0.2 + j0.3 + 0.95 + j1.267)$$

$$V_{G, pu} = 1.204 \angle 8.606 \text{ pu}$$

$$\begin{aligned}
 V_G &= V_{G, pu} \times V_{B1} = 1.204 \angle 8.606 \times 22 \times 10^3 \\
 &= 26.488 \angle 8.606 \text{ kV}
 \end{aligned}$$

# Transformers- Review

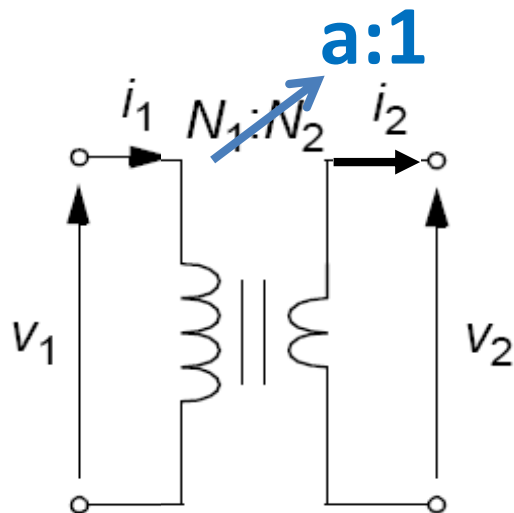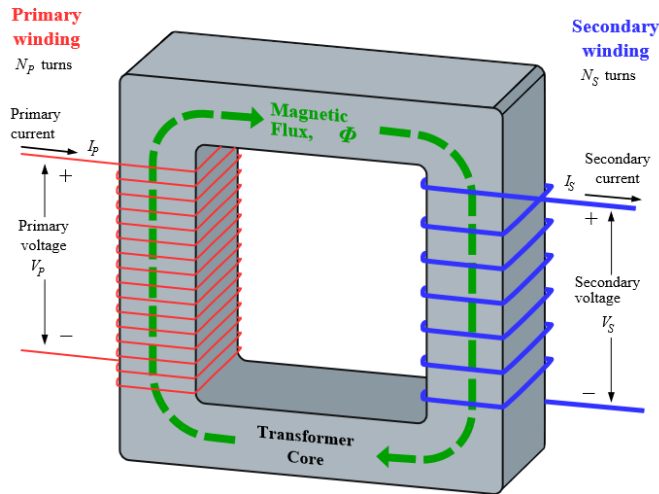

- Define turns ratio as:

$$a \equiv \frac{N_1}{N_2}$$

- From Faraday's and Ampere's Law:

$$V_1 = \left( \frac{N_1}{N_2} \right) V_2 = a V_2$$



$$i_2 = \left( \frac{N_1}{N_2} \right) i_1 = a i_1$$




# An Equivalent Circuit for Transformers

Reflected copper losses and leakage  
reactance of secondary winding.


Copper losses  
Leakage reactance

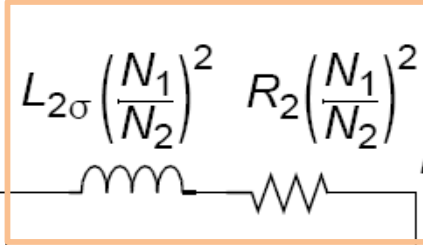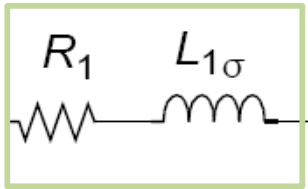



Iron losses  
(core)

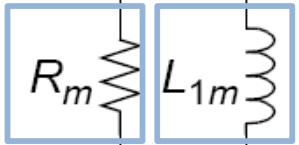

Magnetizing  
susceptance

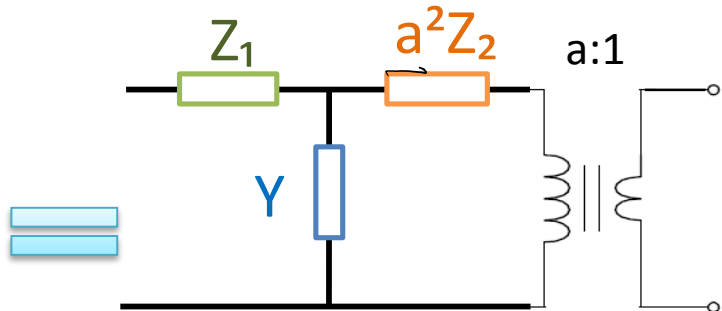


Simplification

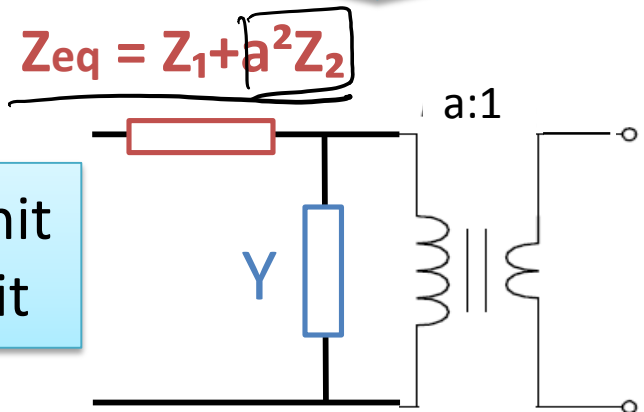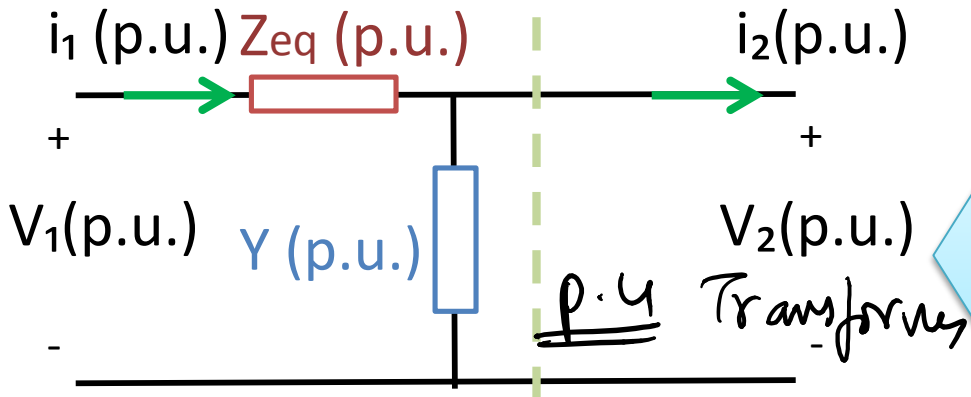





Per unit  
circuit





# 1 $\Phi$ -Steps of Per Unit Analysis

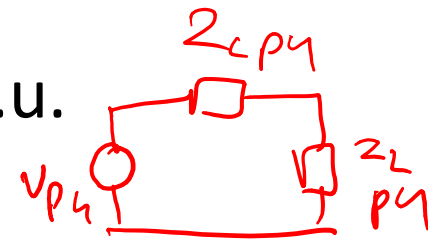1. Choose  $S_B^{1\Phi}$  for the system.
2. Select  $V_B$  for different zones (usually follows transformer voltage ratings).
3. Calculate  $Z_B$  for different zones.  $= \frac{V_B^2}{S_B}$
4. Express all quantities in p.u.
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.



# 3 $\Phi$ Transformer Per Unit Model

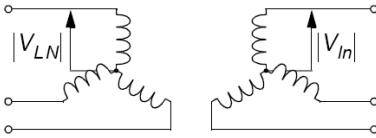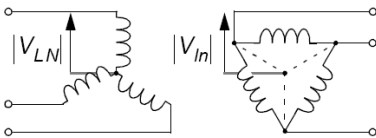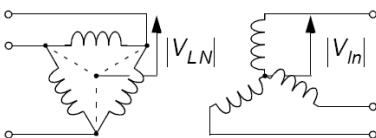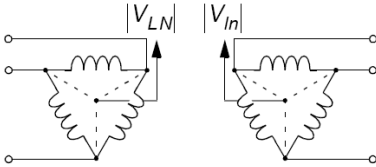designation	winding connection
Yy	
Yd	
Dy	
Dd	

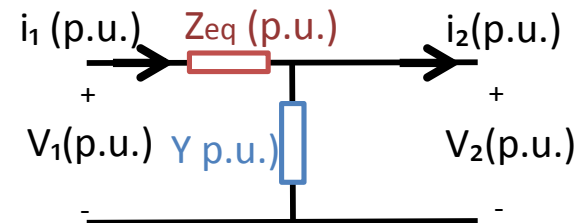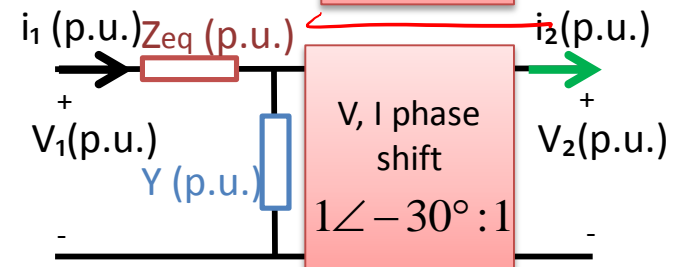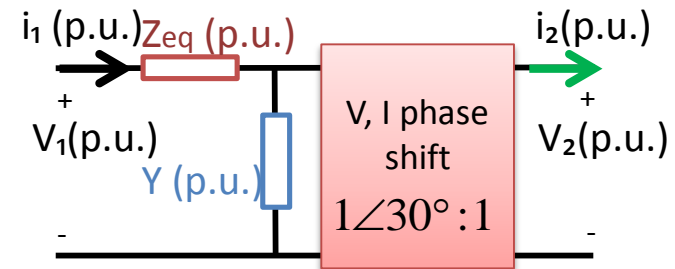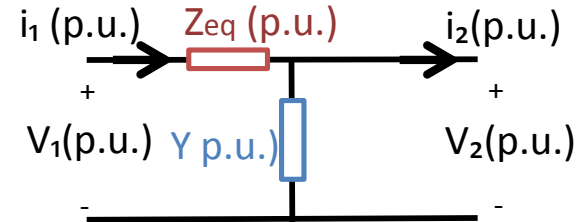

1 pu  $\angle 0$

# 1 $\Phi$ vs 3 $\Phi$ Per Unit Analysis

$$m = \frac{P_L P_N}{P_S P_N} = \frac{P_L / S_B}{P_S / S_B} = \frac{P_L}{P_S}$$

①

$$S_B$$

$$S_B^{3\phi}$$

②

$$V_B \text{ each zone}$$

$$V_B^{L-L} \text{ each zone}$$

③

$$\underline{Z_B} = \frac{V_B^2}{S_B} \text{ each zone}$$

$$Z_B = \frac{(V_B^{L-L})^2}{S_B^{3\phi}} \text{ each zone}$$

④

$$I_B = \frac{S_B}{V_B} \text{ each zone}$$

$$I_B = \frac{S_B^{3\phi}}{\sqrt{3} V_B^{L-L}} \text{ each zone}$$

$$Z_{pu\text{new}} = Z_{pu\text{old}} \cdot \frac{Z_{B\text{old}}}{Z_{B\text{new}}} = Z_{pu\text{old}} \left( \frac{V_{B\text{old}}}{V_{B\text{new}}} \right)^2 \left( \frac{S_{B\text{new}}}{S_{B\text{old}}} \right)$$