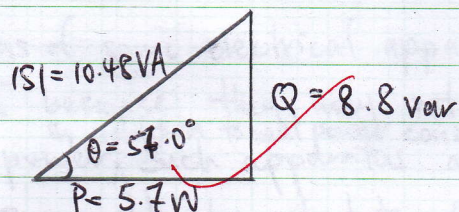



$$L = 0.0852 \text{ H}$$

$$= 85.2 \text{ mH} \approx 89.1 \text{ mH used in experiment}$$


7b 6.1a:




6.1b:

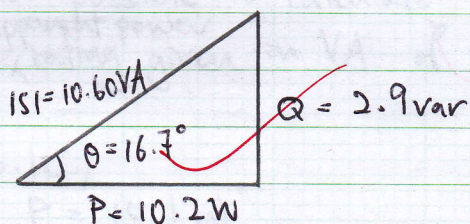


6.1c:

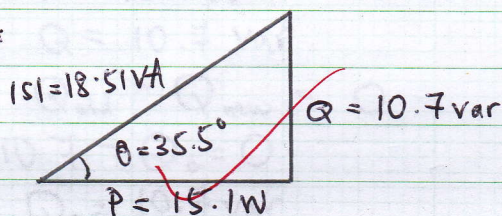


6.1d:

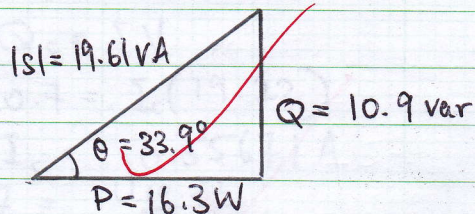

6.2a:

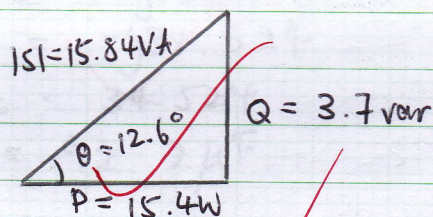

6.2b:

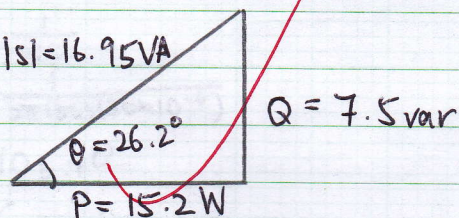

7c

The complex power values ~~at~~ in step 6.1c and step ~~6.2~~ 6.1d ~~differs~~ ^{increased} by ~~1.1 VA~~ ^{1.1 VA}. This should be caused by the increase in overall impedance of the load caused by connecting the transmission line in series with the load. As such, the complex power value obtained from step 6.1d