

# EE2022 Electrical Energy Systems



## Principle of Transformers

Lecturer : Dr. Sangit Sasidhar (elesang)

Slides prepared by Dr. Panida Jirutitijaroen

Department of Electrical and Computer Engineering

# Transformers- Review

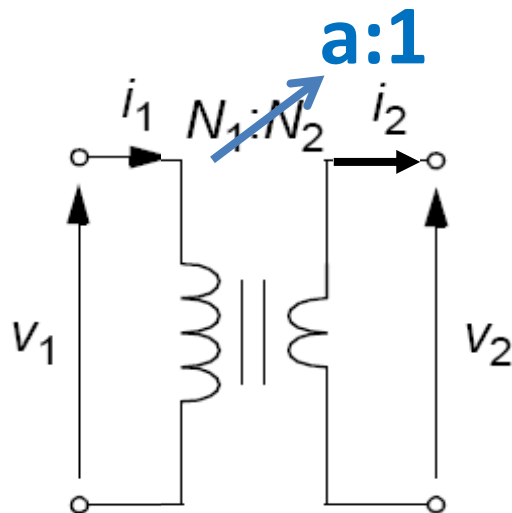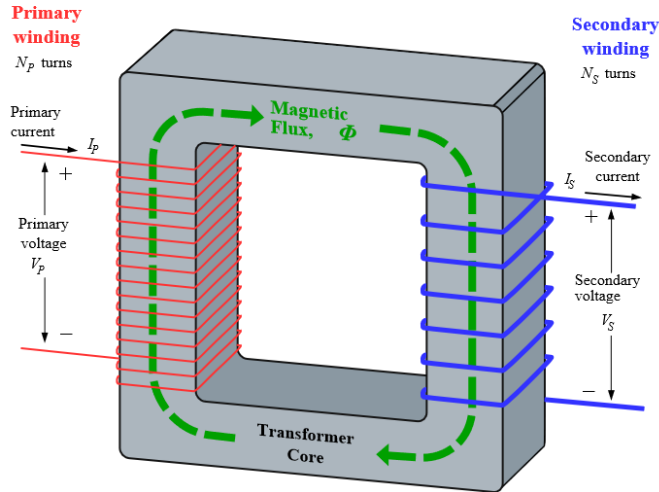

- Define turns ratio as:

$$a \equiv \frac{N_1}{N_2}$$

- From Faraday's and Ampere's Law:

$$V_1 = \left( \frac{N_1}{N_2} \right) V_2 = a V_2$$


$$i_2 = \left( \frac{N_1}{N_2} \right) i_1 = a i_1$$

# Assumptions

1. No resistance in both windings.
2. No leakage flux around the core.
3. No core resistive loss.
4. Core permeability is infinite.

Primary side

Secondary side

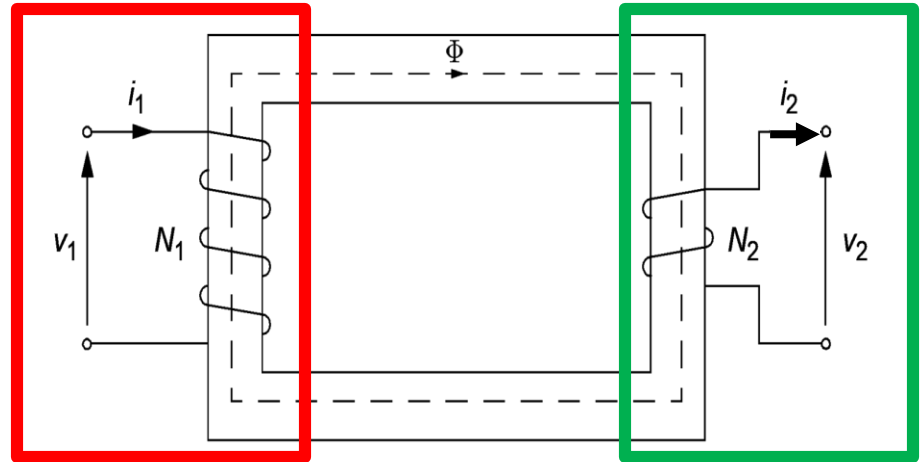

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$i_1 N_1 = i_2 N_2$$

# Outline

- Application of transformers
  - Reflected load
  - Impedance matching for maximum power transfer.
- Practical transformers
  - An equivalent circuit
  - A simplified equivalent circuit
- Transformer parameter tests
  - Short-circuit test
  - Open-circuit test

Reflected load


Impedance matching

# APPLICATION OF TRANSFORMERS
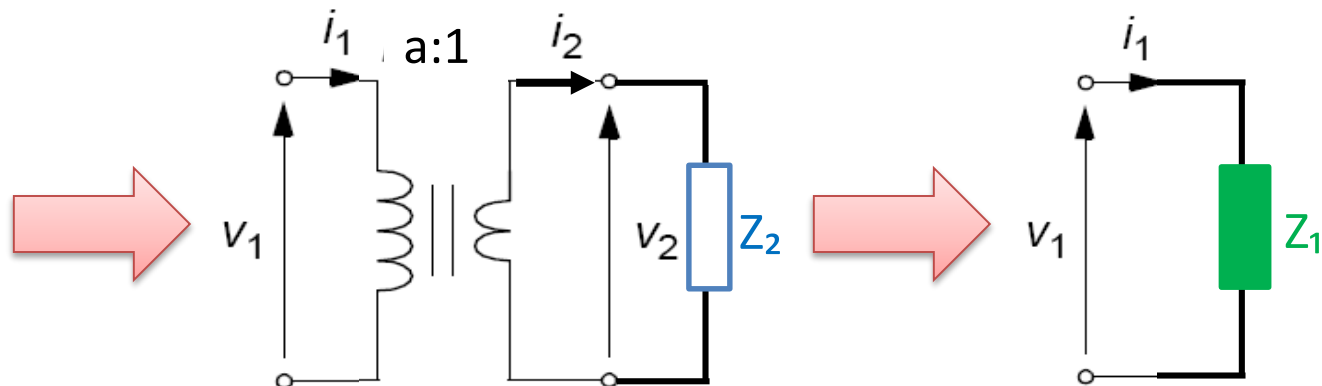
# Reflected Load


- We can reflect a load from one side of a transformer to the other side of the transformer.

Interest  
to find  
reflected  
load " $Z_1$ "



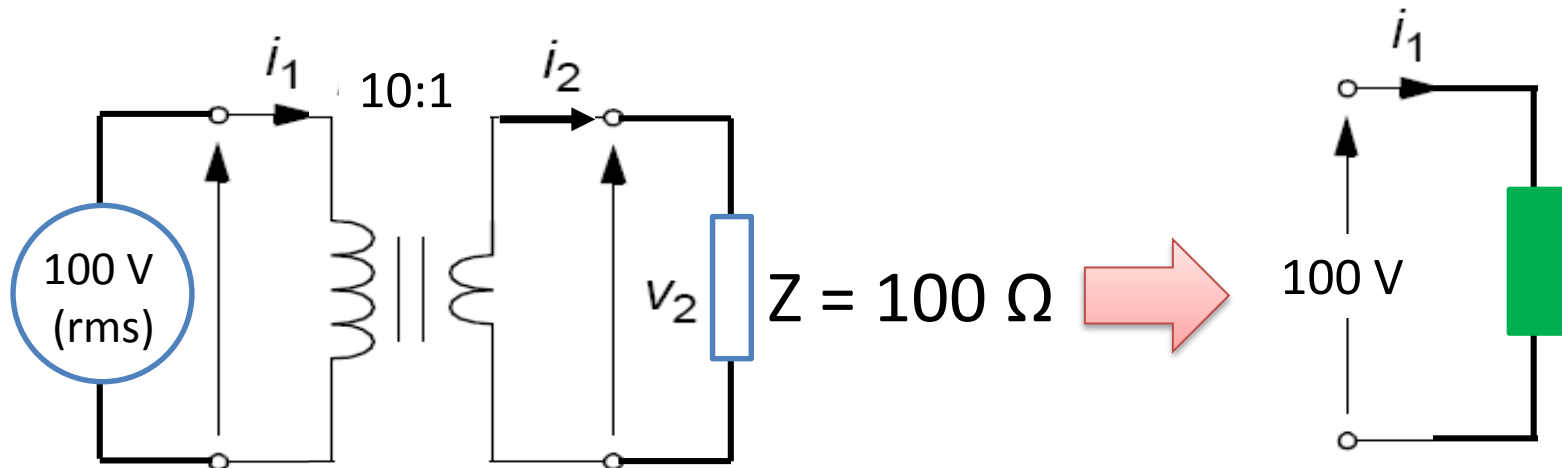
# Example 1

- Find the reflected load of impedance  $100\ \Omega$  seen from the primary side of the transformer.



# Impedance Matching

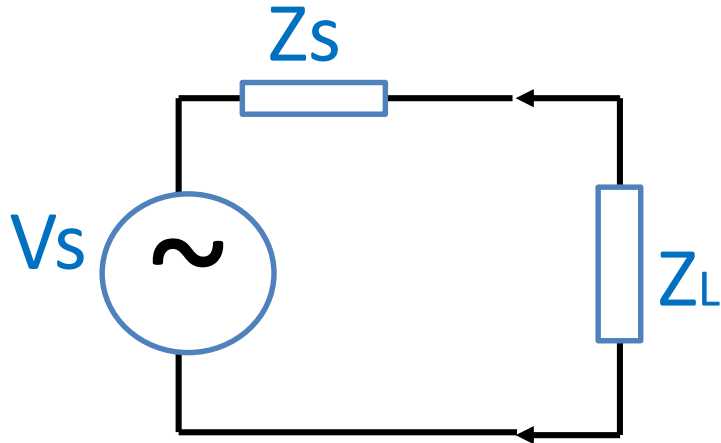

- Under what condition that the **maximum power** be *transferred to the load  $Z_L$* ?



# Impedance Matching

# Maximum Power Transfer Theorem

- From real power expression at the load,


$$P_L = \frac{|V_s|^2}{|Z_S + Z_L|^2} \operatorname{Re}\{Z_L\}$$

- This means that the maximum power will occur when the denominator is minimum.

# Maximum Power Transfer Theorem
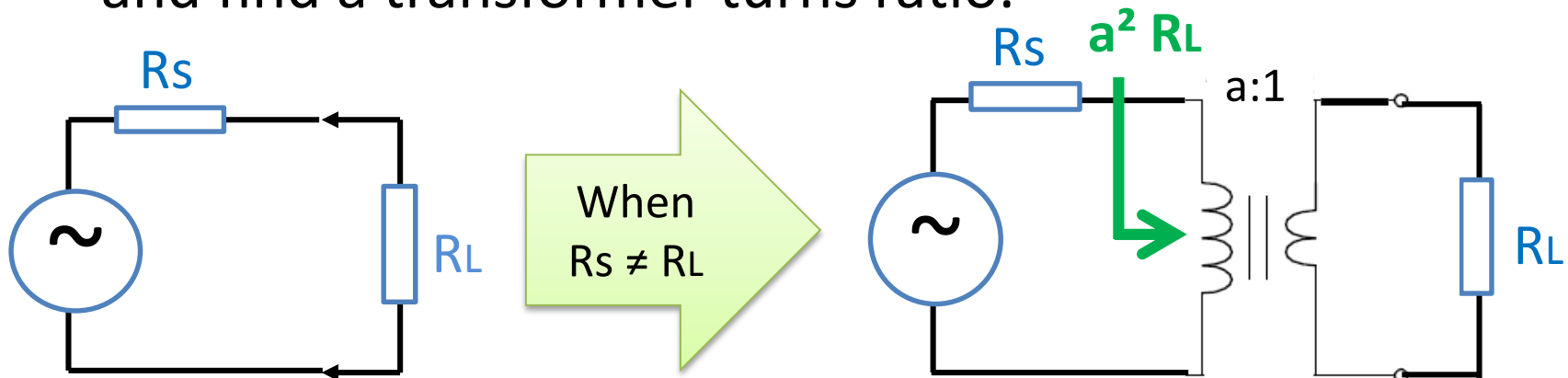
# Impedance Matching for 'R'

- Maximum power transfer occurs when  $R_s = R_L$ .
- In the case that we need to connect the voltage source that has internal impedance of  $R_s$  to a load  $R_L$  that does not satisfy the above condition, we can **design** a **transformer** to *match* impedance for maximum power transfer.
- To find an appropriate transformer, we let  $R_s = a^2 R_L$  and find a transformer turns ratio.



## Example 2

- Given the voltage source with an internal resistance of  $100\ \Omega$ . A transformer is used to connect this voltage source to the load of  $4\ \Omega$  to achieve maximum power transfer at the load. What should be the turns ratio of a transformer?


Transformer components  
Eddy current and hysteresis losses  
Magnetizing current losses  
A practical transformer model  
A simplified model

# PRACTICAL TRANSFORMERS

# Practical Transformers



Pole-mounted single-phase transformer

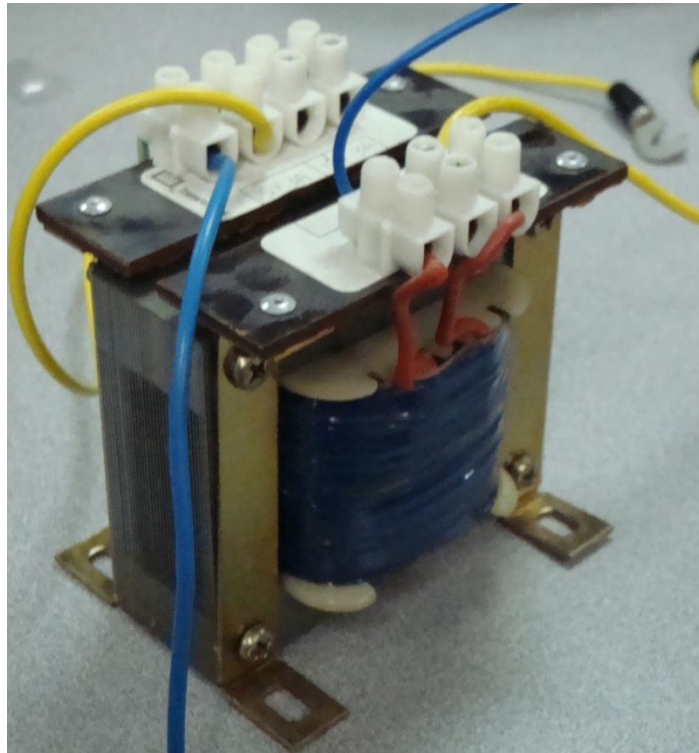


Lab-sized single-phase transformers


# Transformer Components
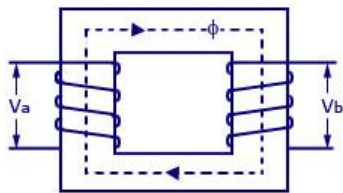
## Magnetic core

- Mainly two types of design.
  - Core type – the magnetic core is surrounded by the windings.
  - Shell type – the windings are surrounded by the core.




1. Core type

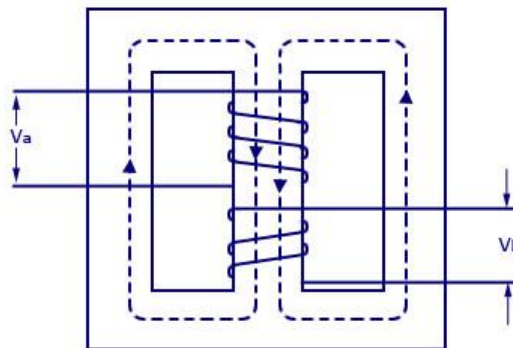

2. Shell type
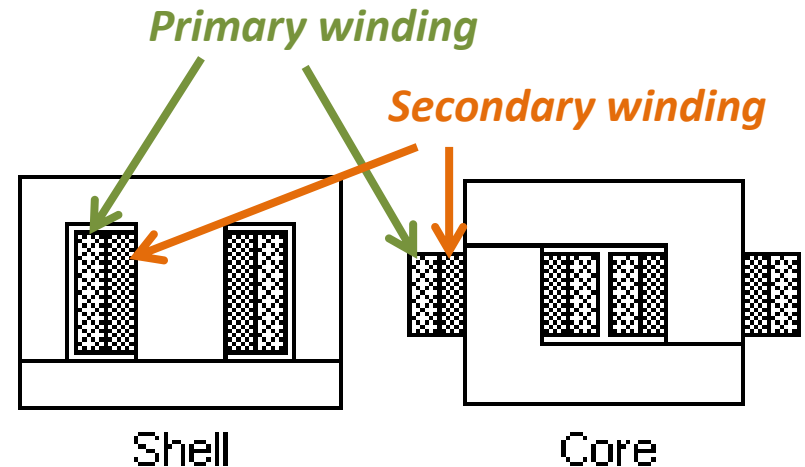
## Primary/Secondary winding

- Windings are placed on top of each other to reduce the amount of flux leakage losses.





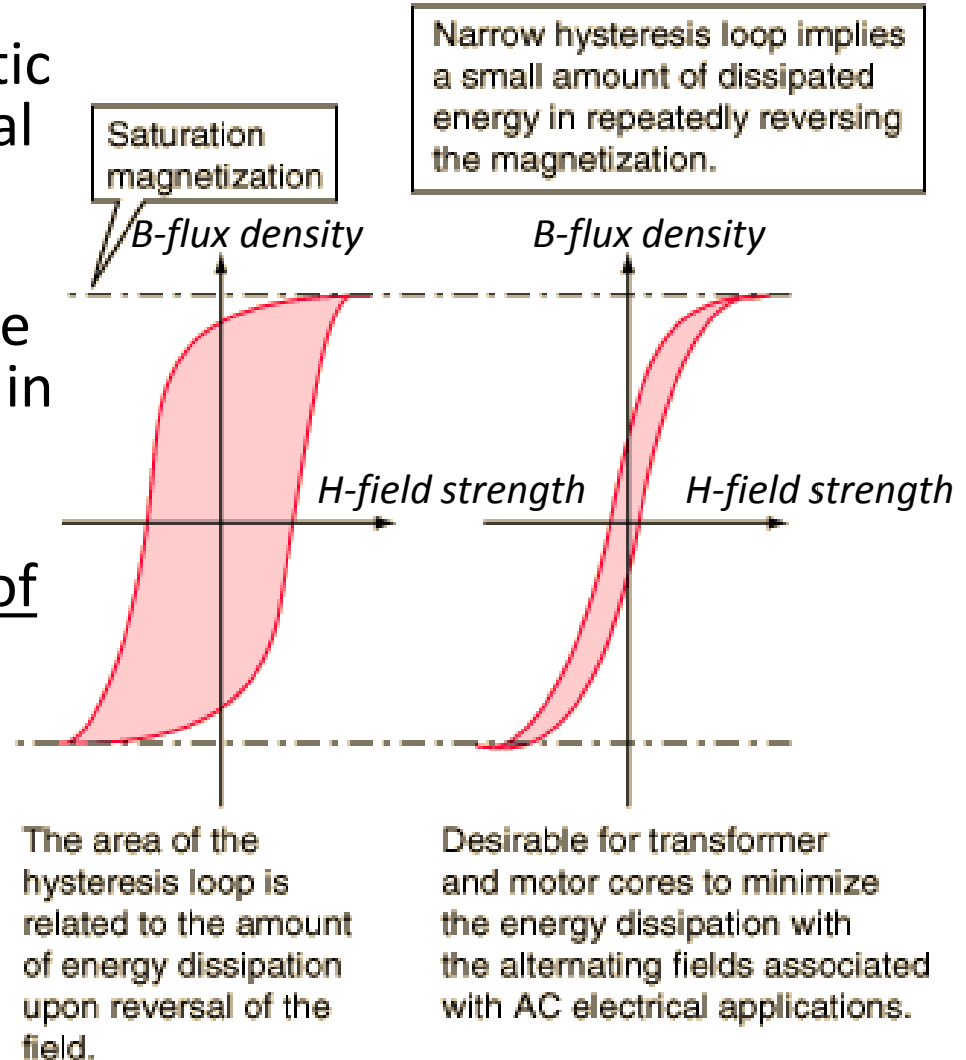
# Hysteresis Losses


- Hysteresis loop is a characteristic of how a ferromagnetic material is magnetized.
- Each time the direction of magnetic field is reversed, some amount of energy is dissipated in the core.
- This means that this loss is proportional to the frequency of electricity.
- Hysteresis loss produces heat and is represented as a **resistance parallel to** the ideal transformer.

Source: <http://hyperphysics.phy-astr.gsu.edu/hbase/solids/hyst.html>



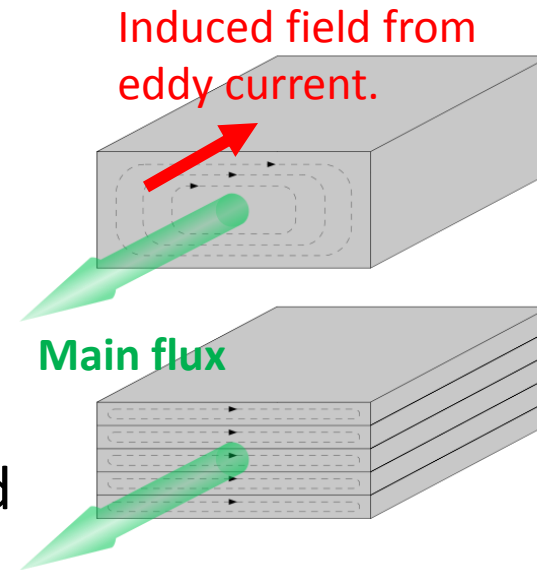
# Eddy Current Losses


- Eddy current refers to small circular current in the magnetic core caused by the flux that passes through the core.
- The magnitude of eddy current losses depends on the strength of the main flux, thus the voltage supplied.
- Eddy current loss produces heat and is represented as a **resistance parallel to** the ideal transformer.
- Eddy current loss can be reduced by making the cores from thin sheets of steel i.e. the core is laminated. The thinner the sheets, the smaller are the eddy current losses.



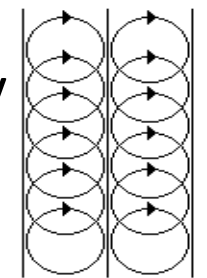
*Eddy currents will induce a magnetic field that opposes to the direction of the main flux.*



Thick Laminations

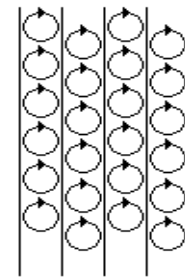



Medium Laminations

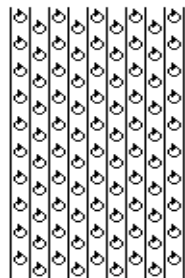

Thin Laminations

Source: <http://sound.westhost.com/xfmr2.htm>

# Core Construction of Transformers

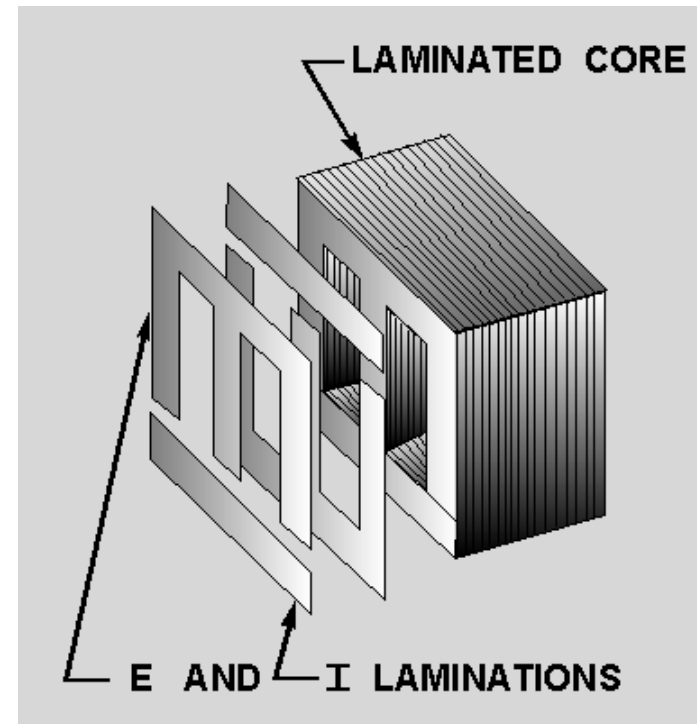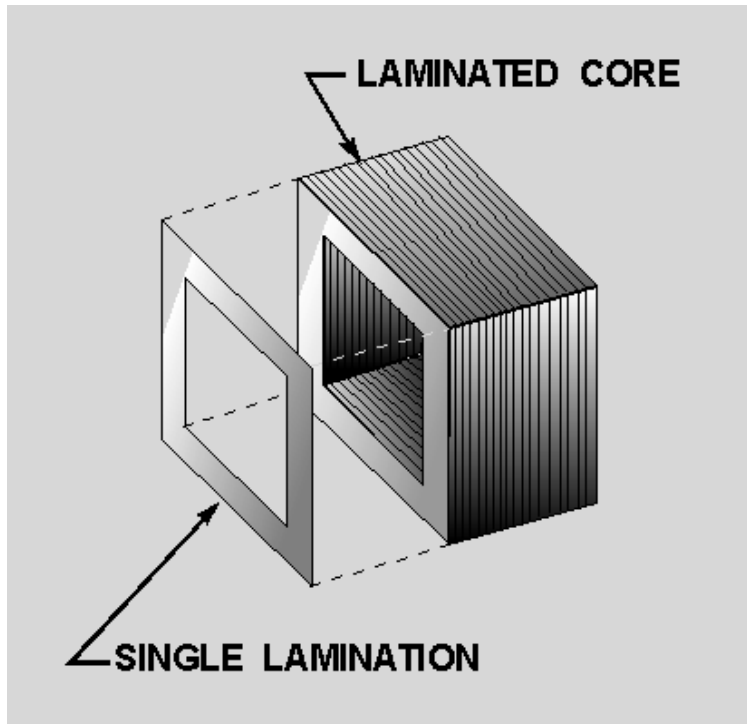


Source: tpub.com

# Ideal VS Practical Transformer

## Ideal transformer

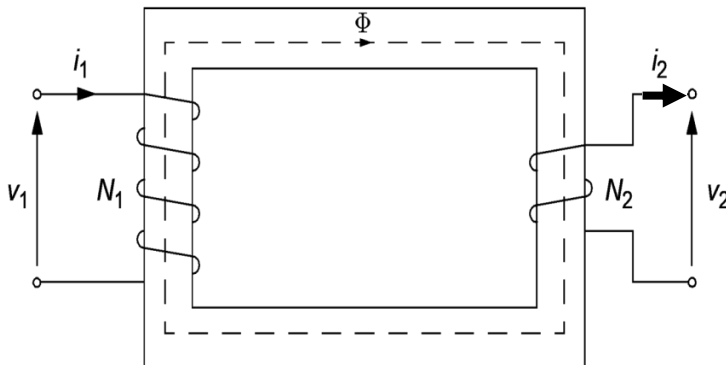1. Zero resistance in the both windings.
2. No leakage flux around the core.
3. No core resistive loss.
4. Core permeability is infinite



## Practical transformer

1. Winding losses (copper losses) represented as **resistance in both windings**.
2. Leakage flux around the core represented as **inductance in both windings**.
3. Core resistive losses (hysteresis loss + eddy current loss) represented as **resistance in parallel to the core**.
4. Magnetic core permeability is finite.

How to represent this effect?

# Finite Core Permeability

- From Ampere's law applied to transformers,

$$\frac{Bl_{path}}{\mu} = i_1 N_1 - i_2 N_2$$

*Recall that in ideal transformer,  $\mu$  is infinite so  $i_1 N_1 = i_2 N_2$*

- When the core material has finite core permeability ( $\mu \neq \infty$ ), and  $V_1 = N_1(j\omega)BA$  (Faraday's law), **assuming a constant  $\mu$ ,**

.


# Magnetizing Current Losses

- From the magnetizing current,


$$i_m = -j \left( \frac{l_{path}}{\omega N_1^2 A \mu} \right) V_1$$

- We find that the current lags the voltage  $V_1$  by  $90^\circ (-j)$ .
- As such, we can use an **inductor** to represent the effect of finite magnetic core permeability in the equivalent circuit.
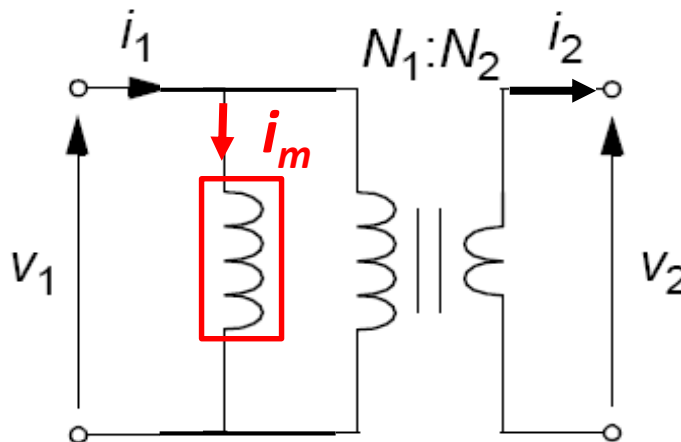
$$i_1 - \left( \frac{N_2}{N_1} \right) i_2 = i_m$$



# Practical Transformers

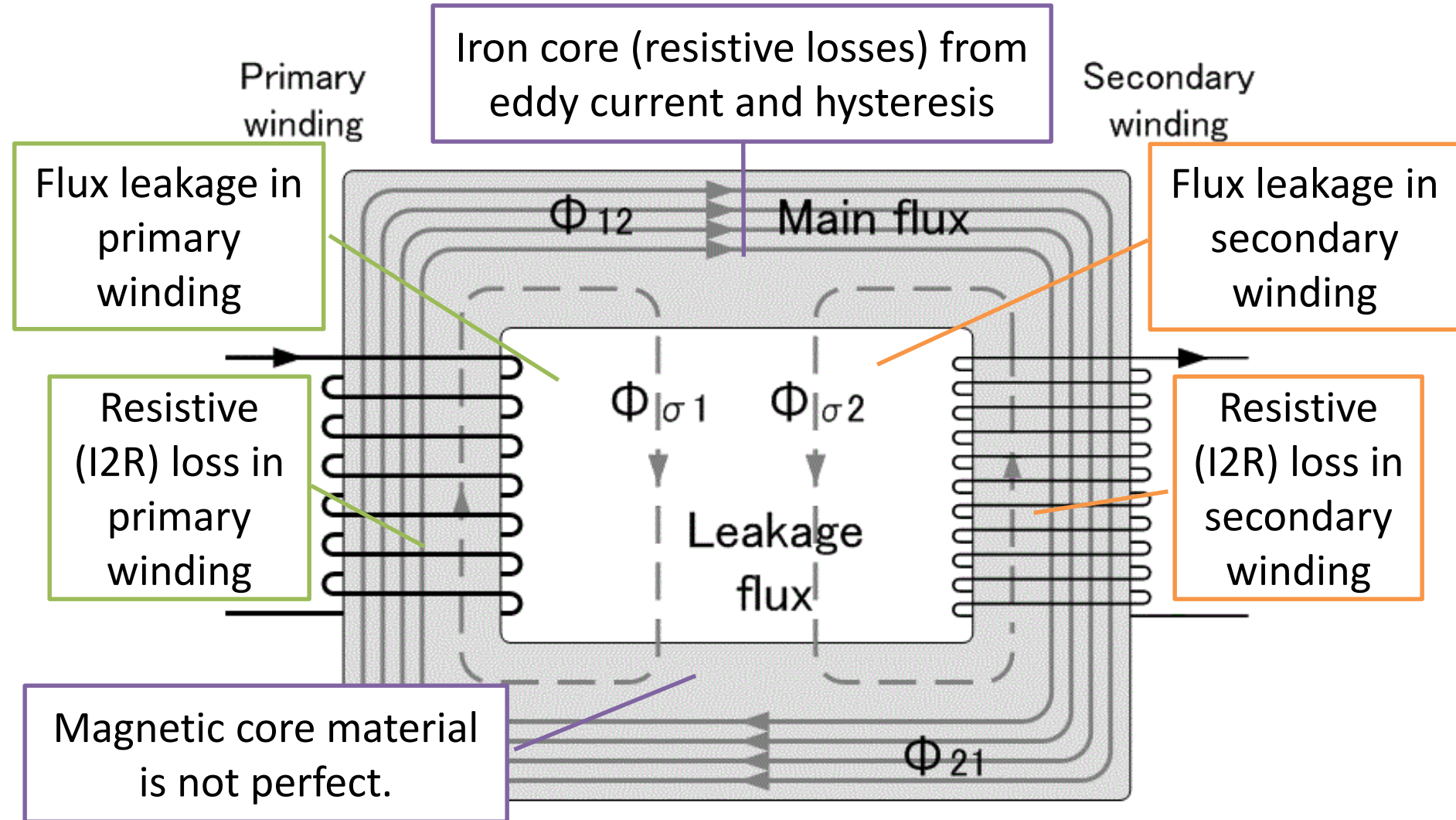


# A Practical Transformer Model


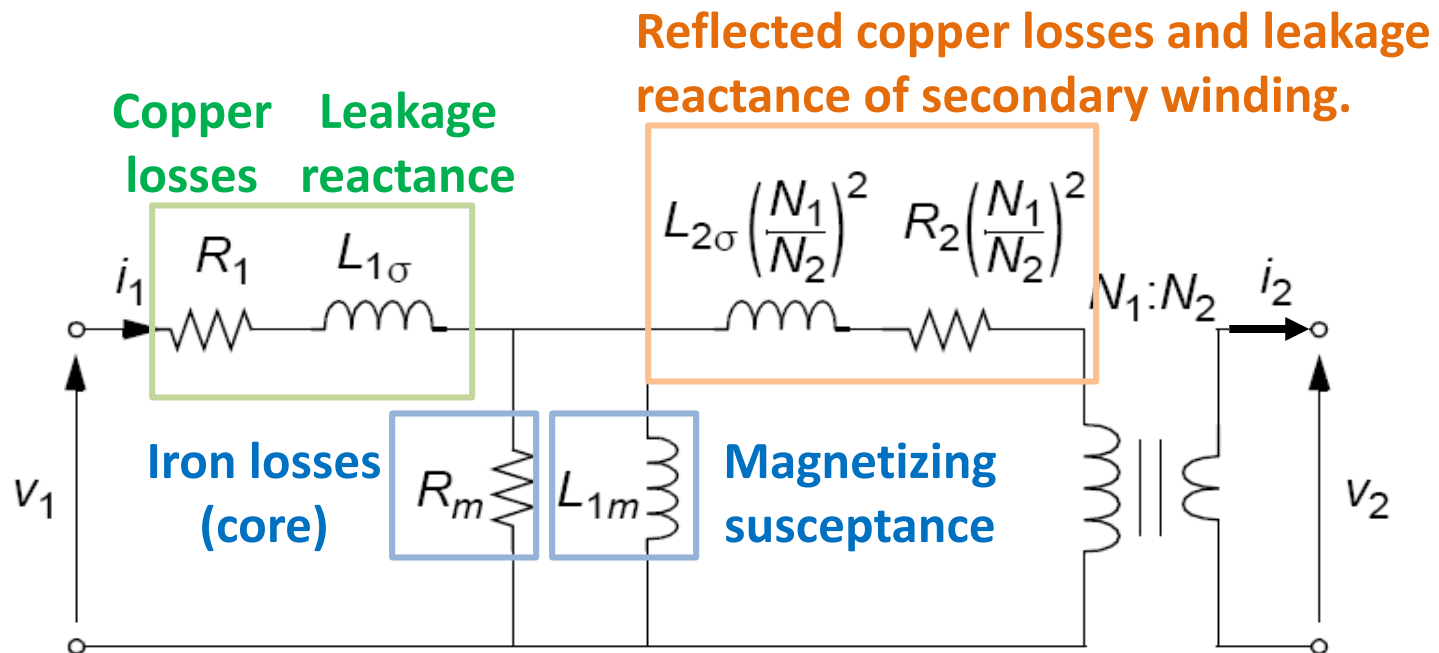
# A Practical Transformer Model


By convention, the **primary side** of transformer is the side with a **higher number** of turns.



Note that in Chapter 3 [Glover, Sarma, and Overbye, “Power System Analysis and Design”], the core losses are represented as ‘shunt admittance’,  $Y = G - jB$  where  $G$  and  $B$  are positive. The imaginary part is negative to represent inductive property.

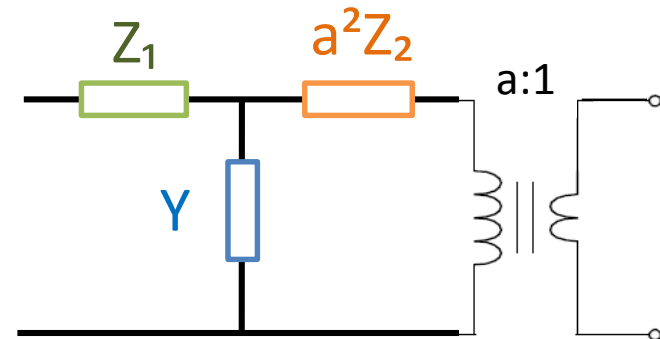
# A Simplified Model

- Typically the admittance,  $Y$ , is very small i.e. resistance is very large.
- This means that the currents flowing through  $Z_1$  and  $a^2 Z_2$  are almost the same.
- We can simply combine  $Z_1$  and  $a^2 Z_2$  to “ $Z_{eq}$ ”, the equivalent series impedance.




Simplification

$$Z_{eq} = Z_1 + a^2 Z_2$$

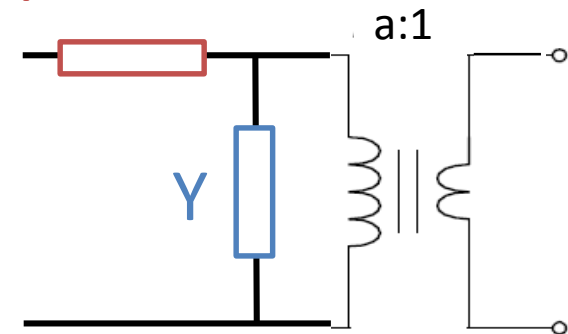
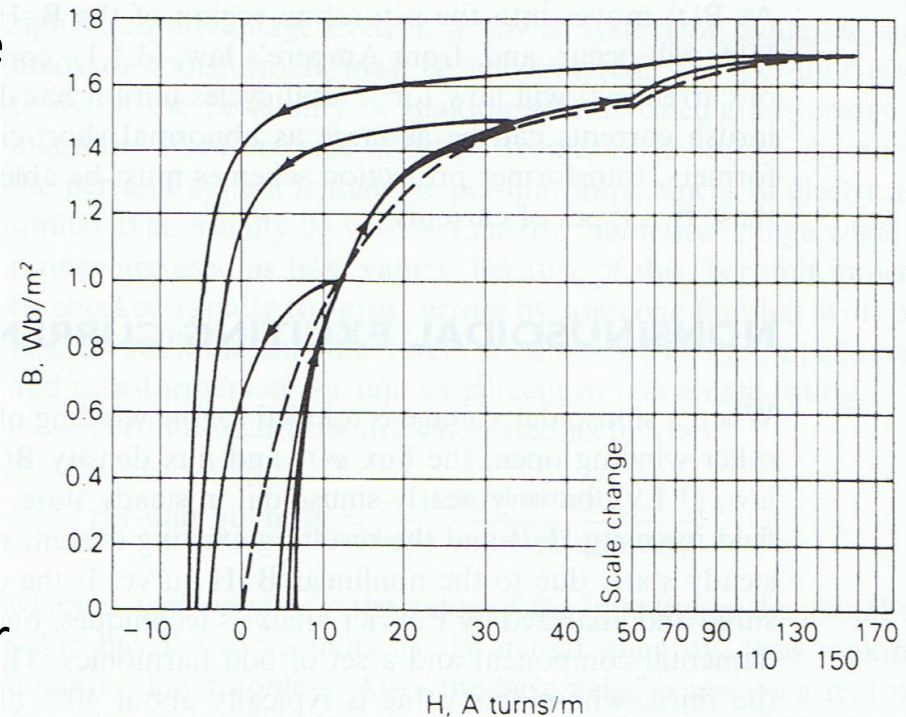
# Saturation

- In practical transformer model, we assume a **constant core permeability** thus linear relationship between  $B$  and  $H$ .
- In fact, the  $B$ - $H$  curve for ferromagnetic materials used for transformer core is nonlinear and has multiple values.
- As  $H$  increases, the core become **saturated** i.e. the magnetic flux density  $B$  increase at a much lower rate.
- This means that there will be high magnetizing current flow making the transformer **to heat up**.
- This effect is **NOT included** in the equivalent circuit.



*B-H curve is approximated by a dashed line.*

$$B = \mu H$$

$B$  = Magnetic flux density (Weber/ $\text{m}^2$  or Tesla)


$H$  = Magnetic field intensity (A/m)

$\mu$  = Magnetic core permeability (H/m)

# Transformer Heating


- Heating is caused by high loading of the transformer, eddy current losses, saturation.
- Heating can lead to winding insulation damage, short circuit, and even explosion.
- In order to prevent overheating, transformers are usually cooled by a fan and a convection oil to reduce heat inside the iron core.

Source: abb.com

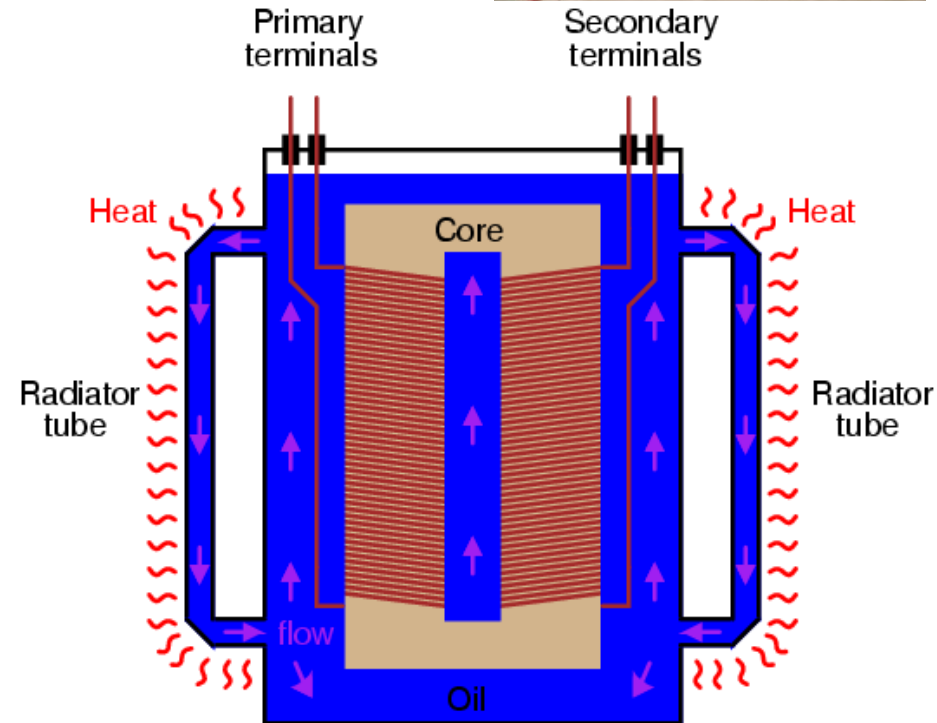


Source: [http://openbookproject.net/electricCircuits/AC/AC\\_9.html](http://openbookproject.net/electricCircuits/AC/AC_9.html)

# Tap Changing Transformer

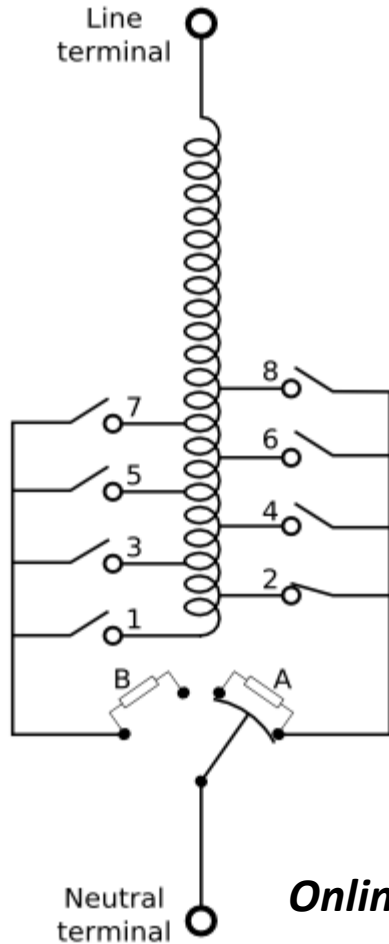

**Online**

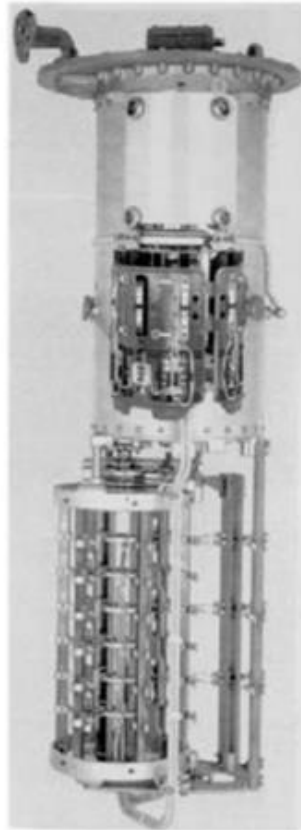


**Design**

Arcing switch

Tap selector

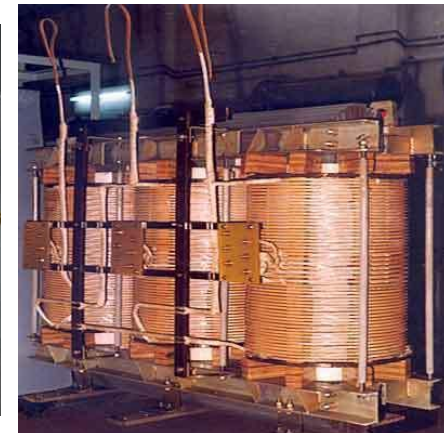- Transformers with tap changer are used to adjust the voltage by changing the turns ratio.
- Tap-changing transformers are used to regulate the voltage at the end users to be at the desired value.
- This can be done both off-line and on-line.



**Off-line** 29


Short-circuit test

Open-circuit test

# TRANSFORMER PARAMETER TESTS
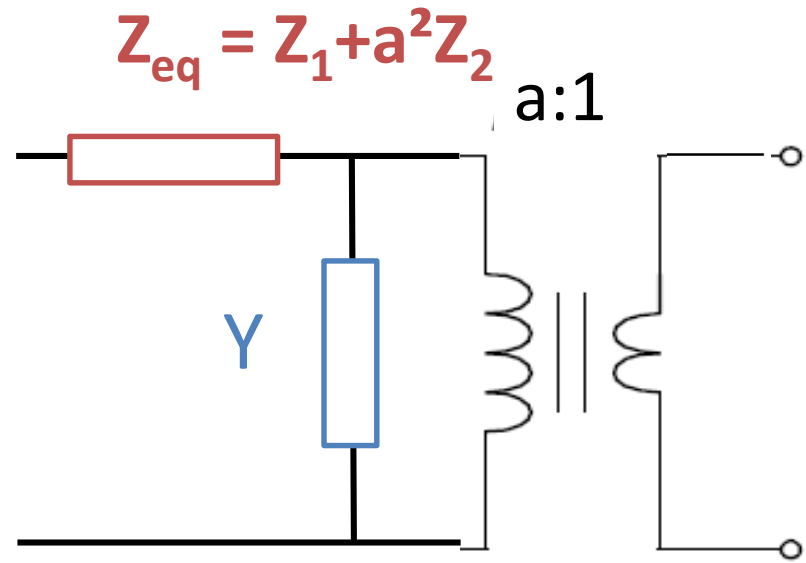
# Transformer Parameters

- Series impedance
  - $Z_1$  and  $Z_2$  are series impedances representing the resistive loss and flux linkage loss in the two windings.
- Shunt admittance
  - $Y$  is a shunt admittance representing iron core loss and magnetizing susceptance.




*Note that by convention, the primary side of a transformer is the side with a higher number of turns. This means that  $a > 1$ .*


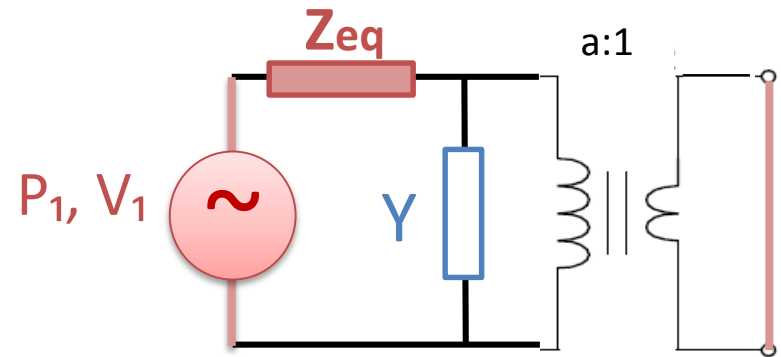
# Short-Circuit Test

- To find equivalent series impedance.
- Short circuit the *secondary* side.
- Apply **rated current** (implies small voltage) at the primary side.
- Measure real power and voltage at the primary side.




*Note that we want small voltage applied to the primary side so that there will be large amount of current passing through the impedance. This will allow more accurate calculation of the series impedance*



# Short-Circuit Test

# Open-Circuit Test

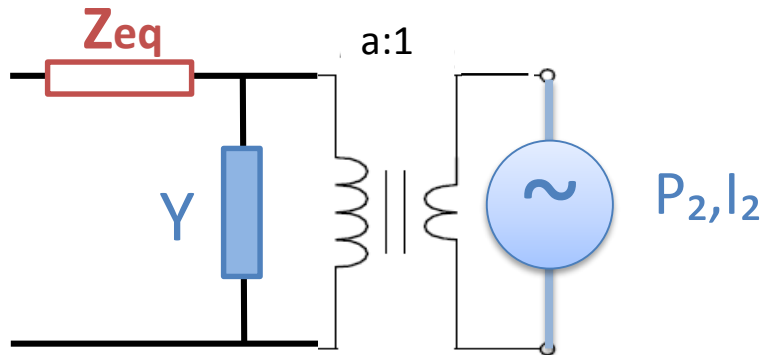

*Note that we want rated voltage at the secondary side so that there will be large amount of current passing through the admittance  $Y$  ( $I=YV$ ). This will allow more accurate calculation of the shunt admittance.*


- To find equivalent shunt admittance.
- Open circuit the *primary* side.
- Apply **rated voltage** at the secondary side.
- Measure real power and current at the secondary side.

# Open-Circuit Test

# Example 3: Short Circuit Test


- Consider a single-phase 20kVA, 480/120 V 60 Hz transformer. During short circuit test, rated current is applied to the primary side. The voltage of **35 V** and real power of **300 W** are measured. Find equivalent series impedance of this transformer.

$$Z_{eq} = R_{eq} + jX_{eq}$$

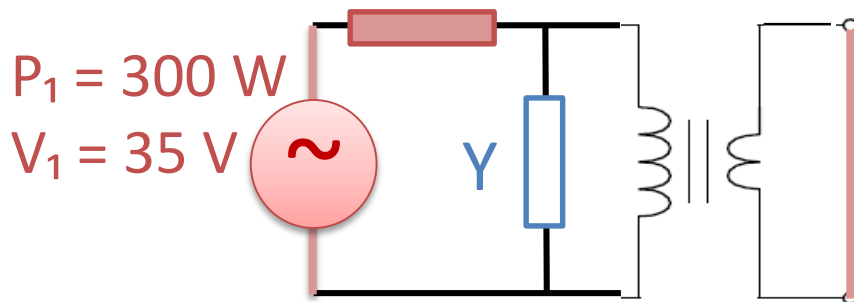
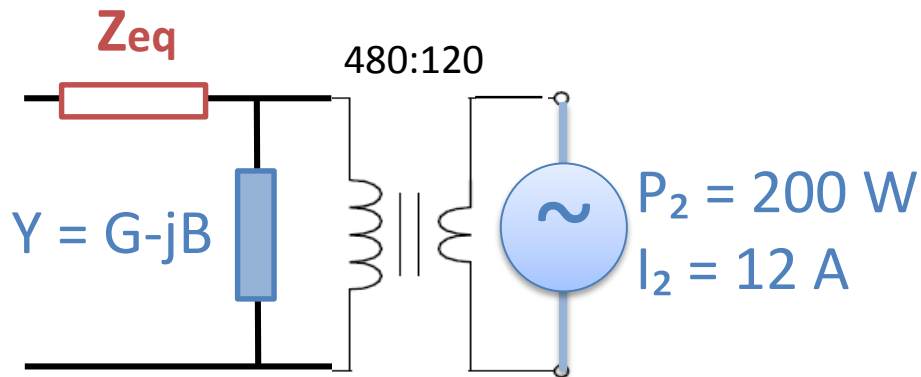
# Example 4: Open Circuit Test

- Consider the same transformer as Example 2. During open circuit test: rated voltage applied to secondary side, then  $I_2 = 12 \text{ A}$  and  $P_2 = 200 \text{ W}$ . Find equivalent shunt admittance  $Y$  of this transformer.



# Summary