

EE2022

Electrical Energy Systems

Lecture 2: AC Systems Fundamentals

Why...?


Why **AC** and not DC ?

Why a **sinusoidal** alternating voltage ?


Why **50 Hz** (or 60 HZ) ?

Why AC and not DC ?

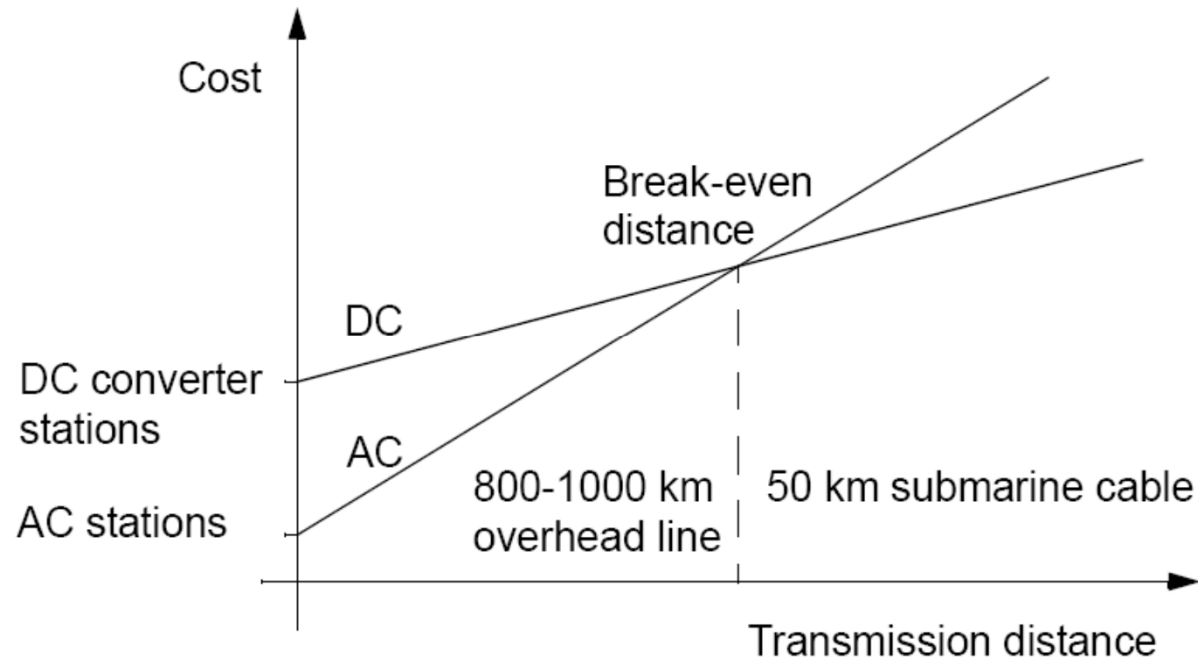Break-even distance for high voltage direct current (HVDC)






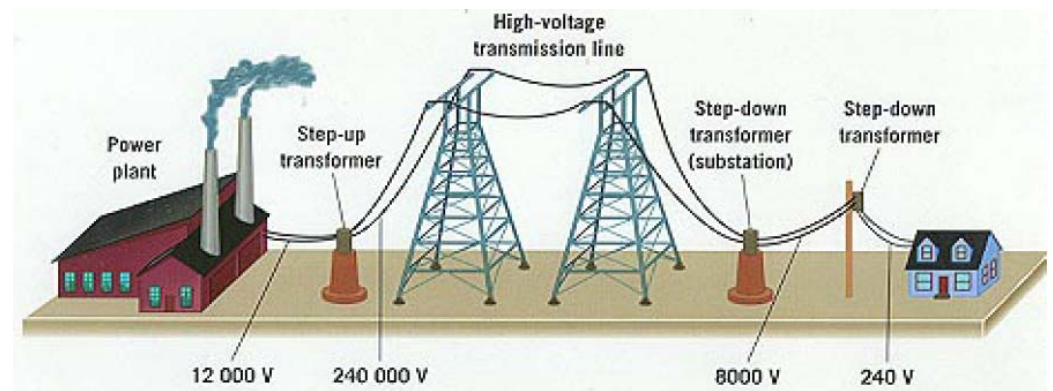Transformers allow easy transformation of voltage



Why a **Sinusoidal** Alternating Voltage ?

Triangular, sinusoidal and block signals

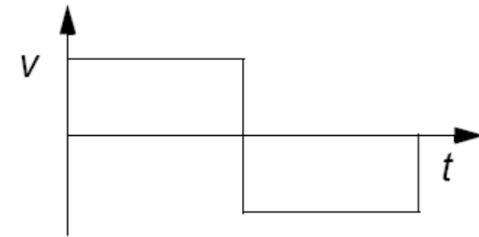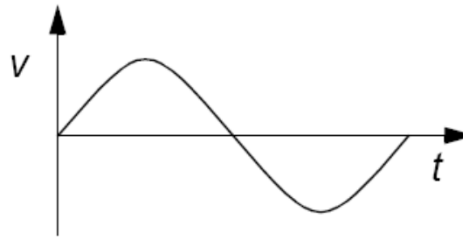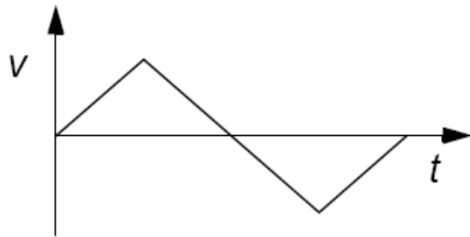

- In linear time in-variant dynamic systems, the basic operators are +, -, x, division, differentiation and integration, etc.
- **For sinusoids, these operations will result in another sinusoid of same frequency and shape!**
- **So all components in the system can be designed for this shape.**

The choice of Frequency

50 Hz and 60 Hz

- **Between 1885 and 1890 in the U.S.A.:**
 - 140, $133\frac{1}{3}$, 125, $83\frac{1}{3}$, $66\frac{2}{3}$, 50, 40, $33\frac{1}{3}$, 30, 25, $16\frac{2}{3}$ Hz
- **Nowadays:**
 - 60 Hz in North America, Brazil and Japan (has also 50 Hz!)
 - 50 Hz in most other countries
- **Exceptions:**
 - 25 Hz Railways (Amtrak)
 - $16\frac{2}{3}$ Hz Railways
 - 400 Hz Oil rigs, ships and airplanes

The choice of Frequency

50 Hz and 60 Hz

- A too low frequency, like 10 or 20 Hz causes flicker
- A too high frequency
 - Increases the **hysteresis** losses:

$$P_{hys} \propto f\psi^{1.5-2.5}$$


- Increases the **eddy current** losses:

$$P_{eddy} \propto f^2\psi^2$$

- Increases the **cable and line impedance**

AC Systems Fundamentals

Sinusoidal Currents And Voltages

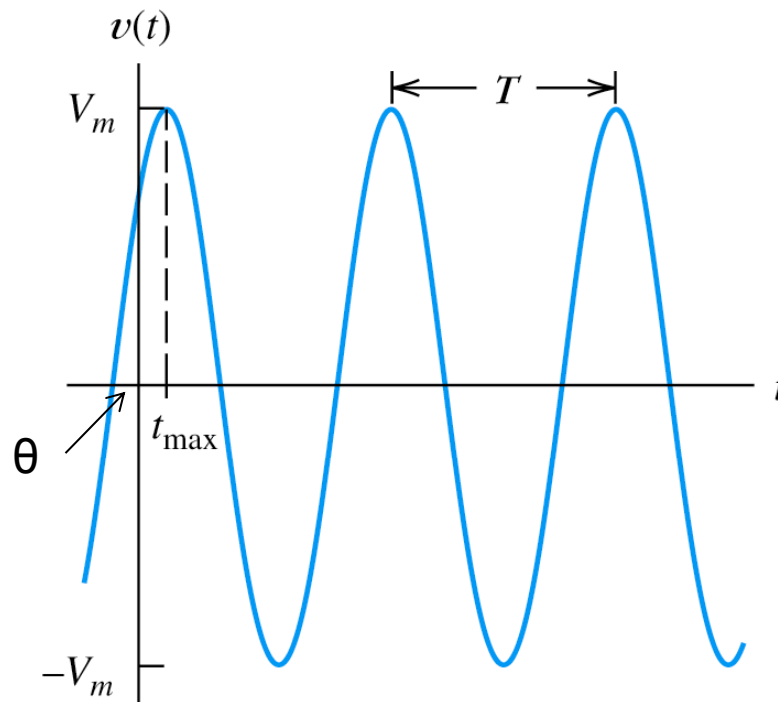

V_m is the peak value

ω is the angular frequency in radians/sec

θ is the phase angle


T is the period

A sinusoidal voltage waveform given by $v(t) = V_m \cos(\omega t + \theta)$.

Note: Assuming that θ is in degrees, we have $t_{\max} = \frac{-\theta}{360} \times T$.

For the waveform shown, θ is -45° .

Root-Mean-Square Values

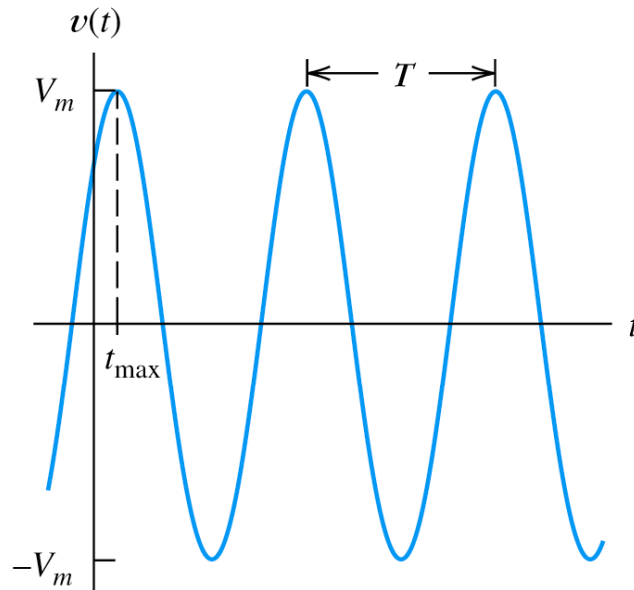

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \frac{V_m}{\sqrt{2}}$$

Figure 5.1 A sinusoidal voltage waveform given by $v(t) = V_m \cos(\omega t + \theta)$.

Note: Assuming that θ is in degrees, we have $t_{\text{max}} = \frac{-\theta}{360} \times T$.

For the waveform shown, θ is -45° .


Rationale for using RMS value

The power absorbed by a resistor of R ohms in a d.c. circuit is

$$P = \frac{V_{dc}^2}{R} = I_{dc}^2 R$$

The power absorbed by a resistor of R ohms in an a.c. circuit is
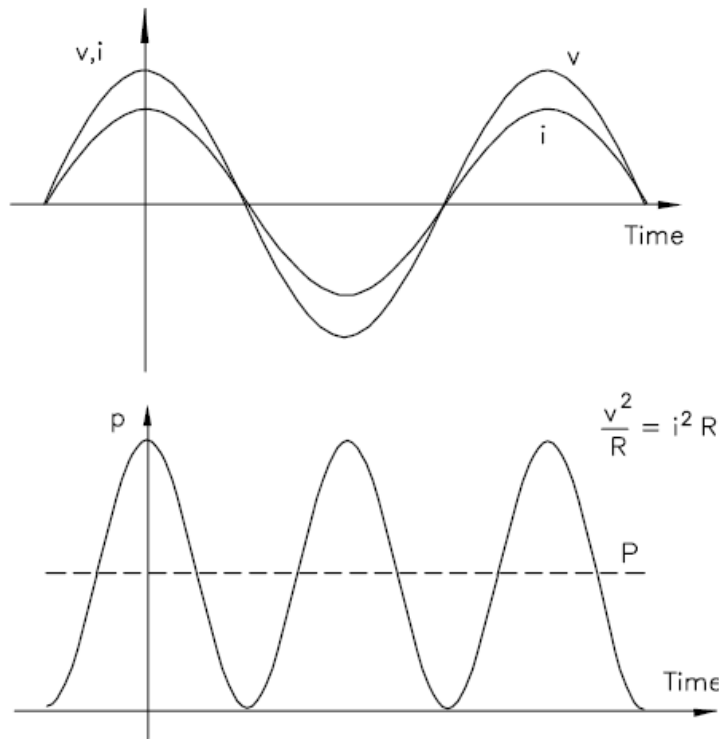
$$P = \frac{I_m^2}{2} R = \frac{V_m^2}{2R}$$



RMS value in Power Calculation

It is desirable to have same form of equation for power in both a.c. and d.c. circuits mainly because of


- Convenience
- Consistence

For d.c. circuits, we have $V_{rms} = V_{dc}$ and $I_{rms} = I_{dc}$. So, for both a.c. and d.c., the power in a resistor is

$$P = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

AC Analysis

Phasors

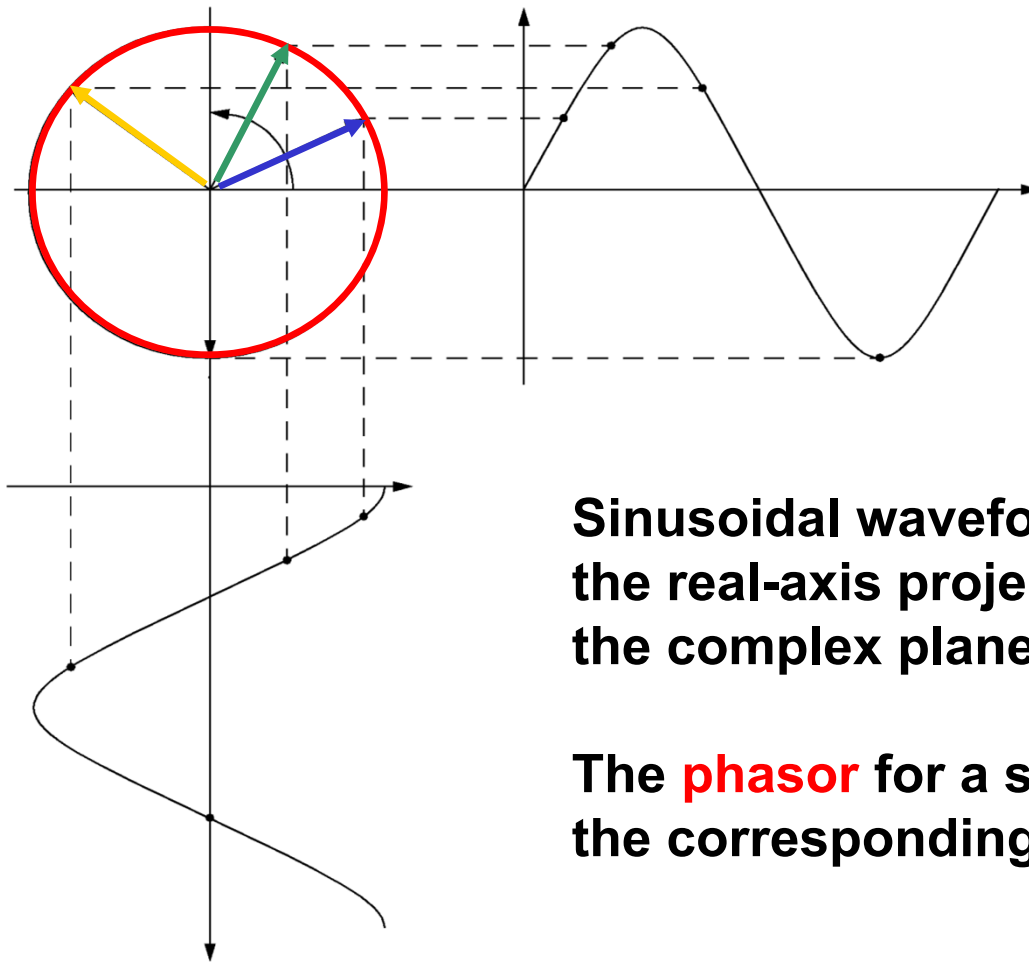

Sinusoidal waveforms can be visualized as the real-axis projection of vectors rotating in the complex plane.



The **phasor for a sinusoid is a snapshot of the corresponding rotating vector at $t = 0$.**

Phasor Representation of a Sinusoidal waveform

Time function : $v_1(t) = V_m \cos(\omega t + \theta_1)$

Phasor : $\mathbf{V}_1 = V_1 \angle \theta_1$

Where V_1 is the RMS value of voltage

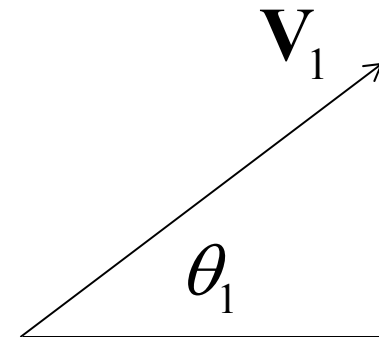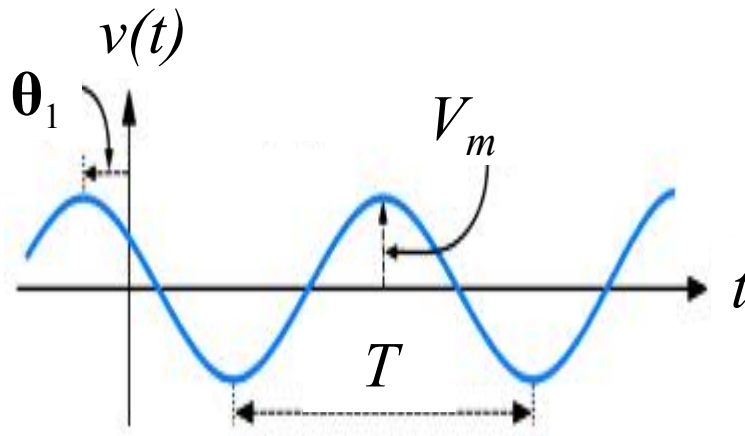

Convention used for Phasors

So far, we have used peak amplitude of cosine wave as the length of phasor.

In AC systems, the **RMS** value of a sine wave or cosine wave is typically used.

$$V_{rms} = \frac{V_m}{\sqrt{2}}, \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_m = \sqrt{2}V_{rms}, \quad I_m = \sqrt{2}I_{rms}$$

Using RMS value doesn't alter the relationship between phasors.

Default conventions used for phasor:

- time domain signal is expressed as cosine function
- length of the phasor is RMS value of the waveform

Example 1: Converting sinusoidal time-domain expression to phasor form



$$v(t) = \sqrt{2}.20 \cos(\omega t - 45)$$

$$V_{rms} = V_m / \sqrt{2} = 20$$

$$\mathbf{V}_1 = 20 \angle -45^\circ$$

Phase Relationships

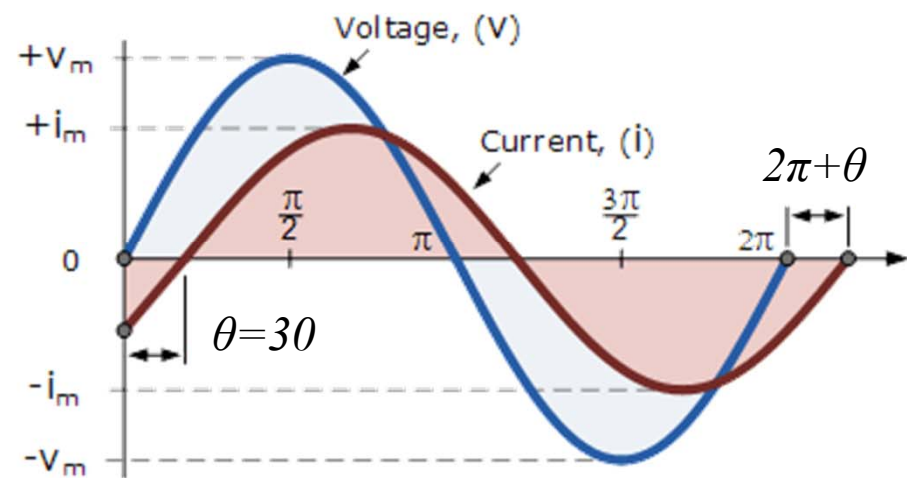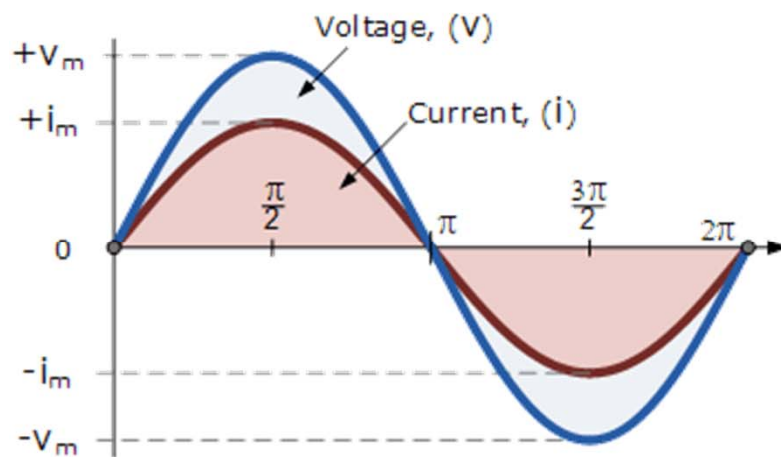Sometimes when we are analysing alternating waveforms we may need to know the position of the phasor, representing the alternating quantity at some particular instant in time especially when we want to compare two different waveforms on the same axis




Phase Relationships

To determine phase relationships from a phasor diagram, consider the phasors to rotate counterclockwise.

Then when standing at a fixed point, if V_1 arrives first followed by V_2 after a rotation of θ , we say that V_1 leads V_2 by θ .


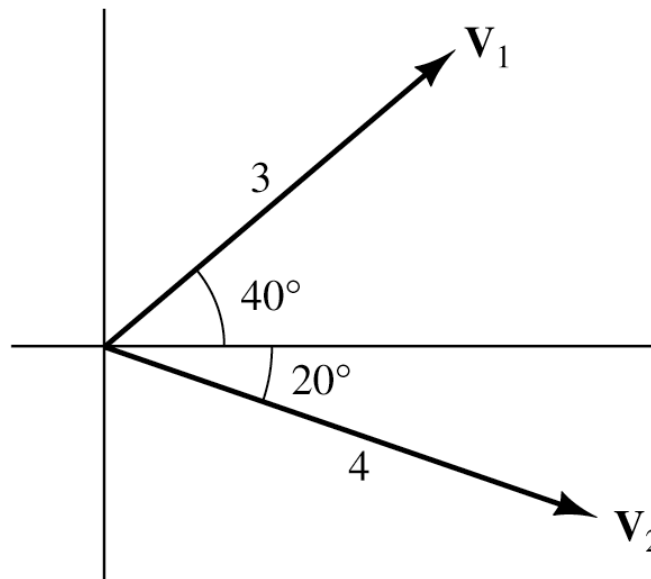
Alternatively, we could say that V_2 lags V_1 by θ .




Because the vectors rotate counterclockwise, v_1 leads v_2 by 60° (or, equivalently, v_2 lags v_1 by 60° .)

Impedance for Circuit Components R, L, C

Voltage and current in a Resistance

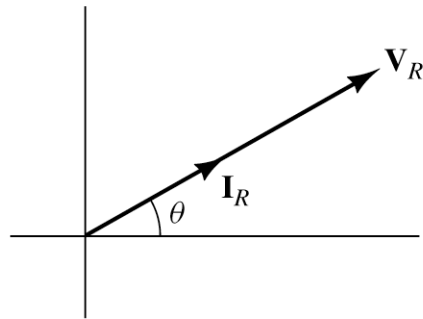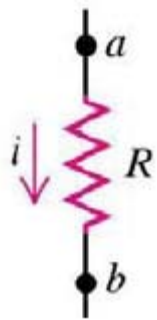

(a) Phasor diagram

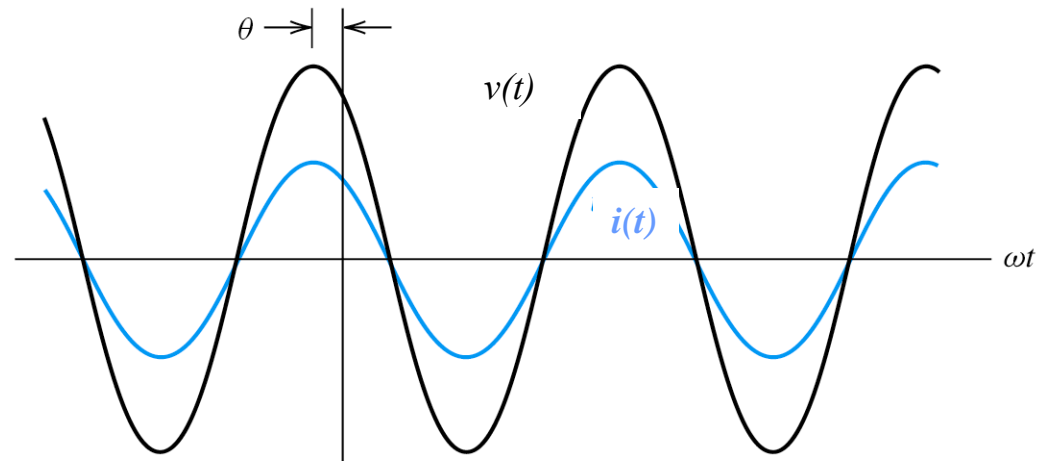


(b) Current and voltage versus time


For a pure resistance, current and voltage are in phase.

$$\mathbf{V}_R = R\mathbf{I}_R$$

Voltage and current in an Inductor

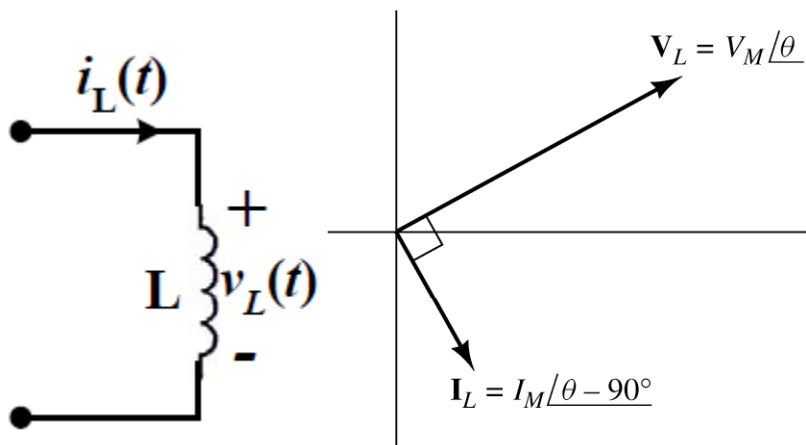

(a) Phasor diagram

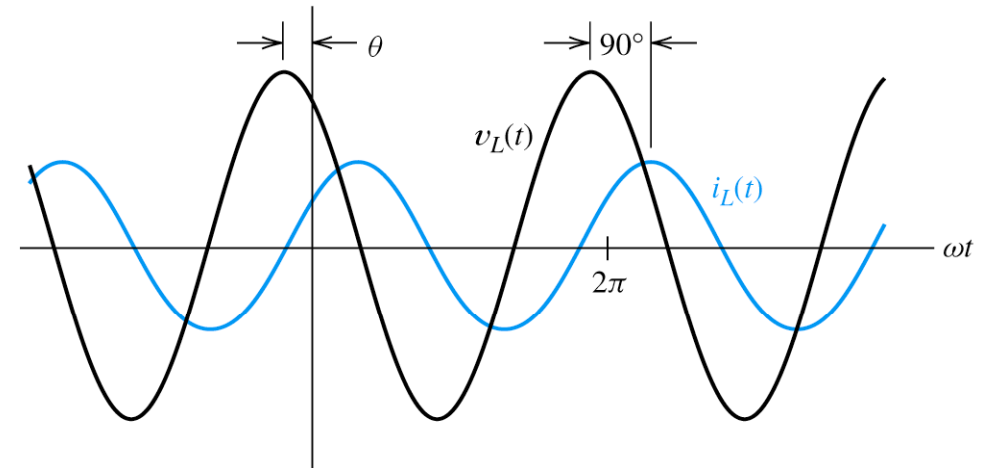

(b) Current and voltage versus time



Current lags voltage by 90° in a pure inductance.

$$\mathbf{V}_L = j\omega L \times \mathbf{I}_L$$


$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$\mathbf{V}_L = Z_L \mathbf{I}_L$$

Voltage and current in a Capacitor

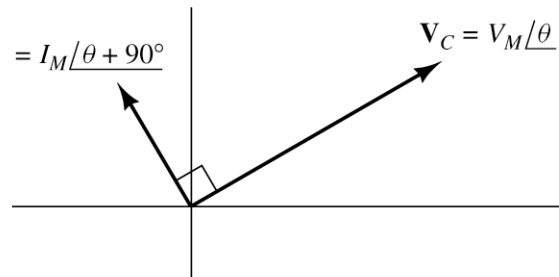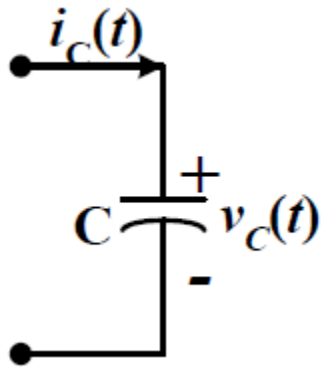

(a) Phasor diagram

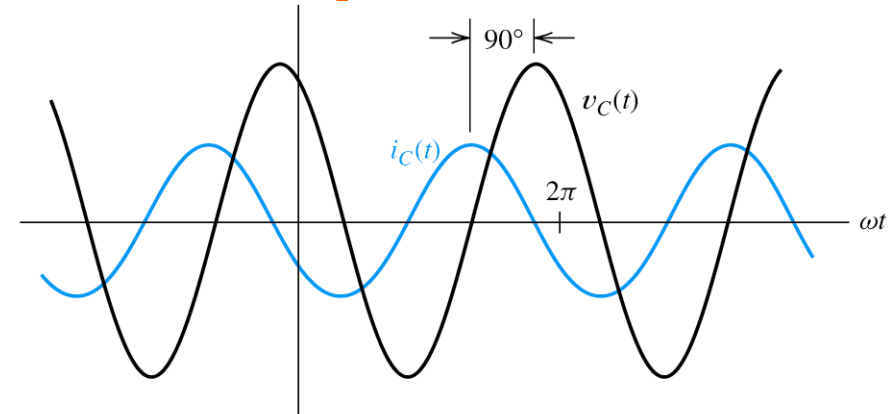










(b) Current and voltage versus time

Current leads voltage by 90° in a pure capacitance.

$$\mathbf{V}_C = \mathbf{Z}_C \mathbf{I}_C$$

$$Z_C = -j \frac{1}{\omega C} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

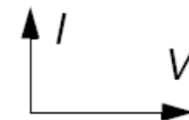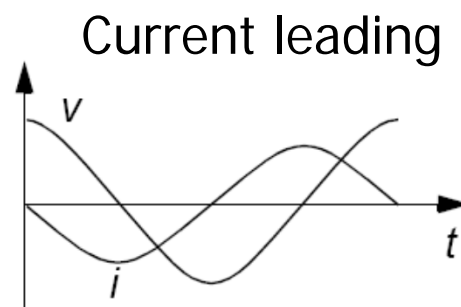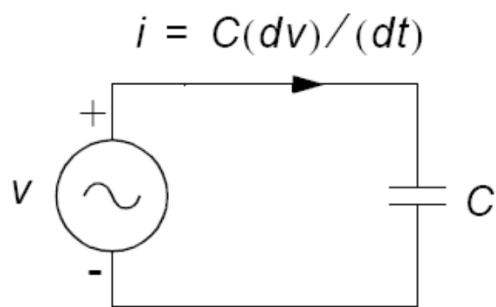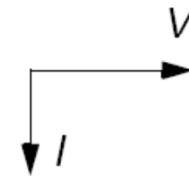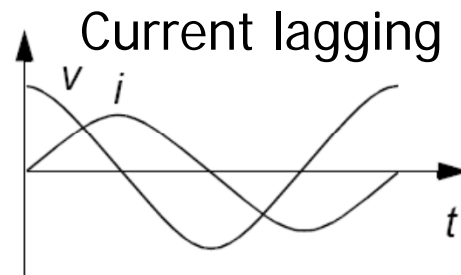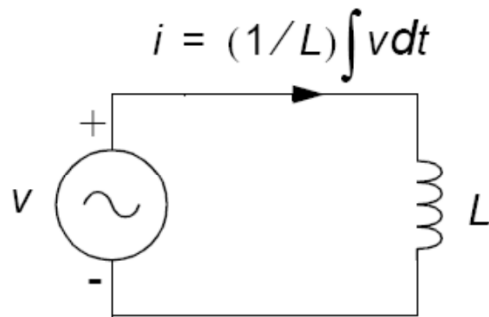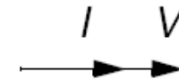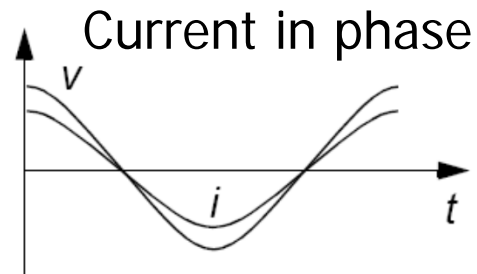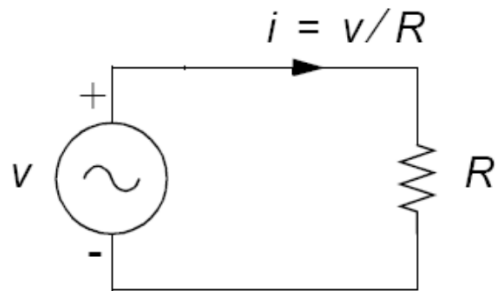Summary: Time \Leftrightarrow Phasor domains




A sinusoidal waveform can be represented as follows:

$$v(t) = V_m \cos(\omega t + 30) = 141.42 \cos(\omega t + 30)$$

Phasor representation:

$$V = 100 \angle 30$$

$$V = 86.6 + j50$$

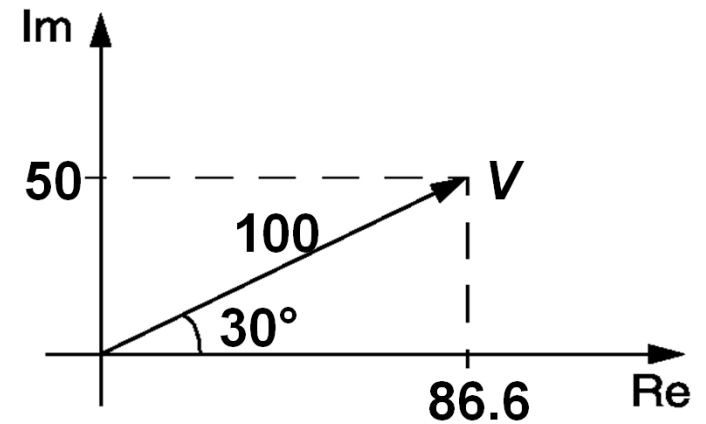

Example 3: Using Phasors to Add Sinusoids

$$v_1(t) = \sqrt{2}.20 \cos(\omega t - 45) \quad v_2(t) = \sqrt{2}.10 \cos(\omega t - 30)$$

$$\mathbf{V}_1 = 20 \angle -45^\circ$$

$$\mathbf{V}_2 = 10 \angle -30^\circ$$

$$\mathbf{V}_s = \mathbf{V}_1 + \mathbf{V}_2$$

$$= 20 \angle -45^\circ + 10 \angle -30^\circ$$

$$= 14.14 - j14.14 + 8.660 - j5$$


$$= 23.06 - j19.14$$

$$= 29.97 \angle -39.7^\circ$$


$$v_s(t) = 42.38 \cos(\omega t - 39.7) \text{ volts}$$

Equivalent time domain and phasor representations


A.C. circuit with a resistance

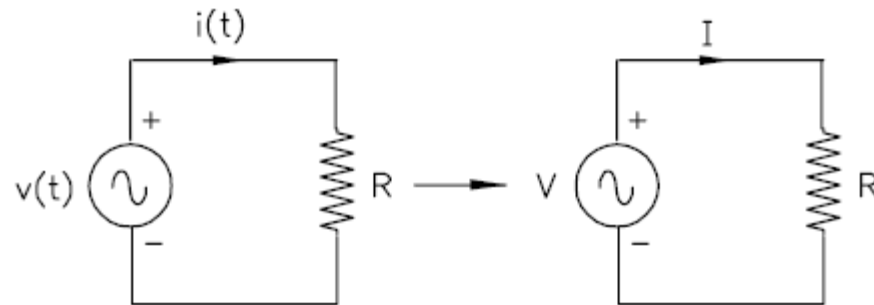

A.C. circuit with an inductance




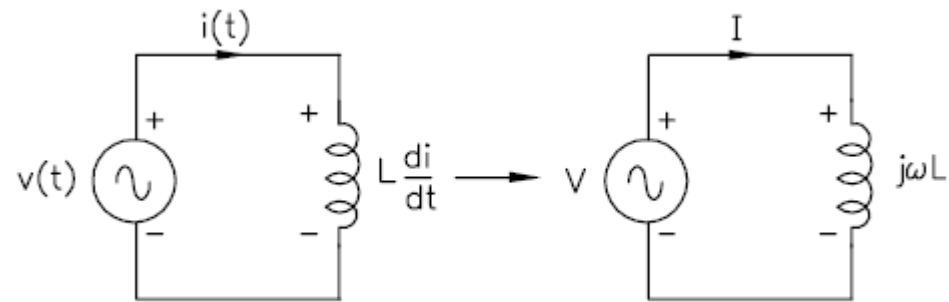


A.C. circuit with a capacitance

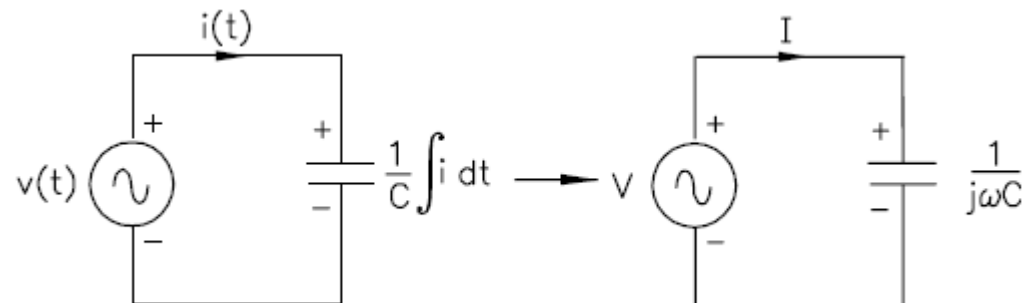


Element	Voltage	Current	Impedance
R	$ V \angle 0^\circ$	$\frac{ V \angle 0^\circ}{R}$	R
L	$\omega L I \angle 90^\circ$	$ I \angle 0^\circ$	$j\omega L$
C	$ V \angle 0^\circ$	$\omega C V \angle 90^\circ$	$\frac{1}{j\omega C}$

Complex Impedance

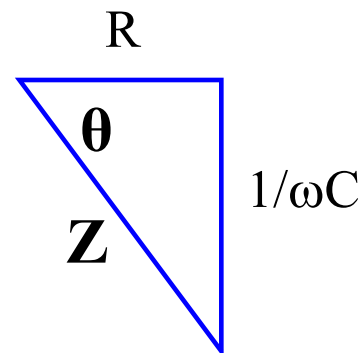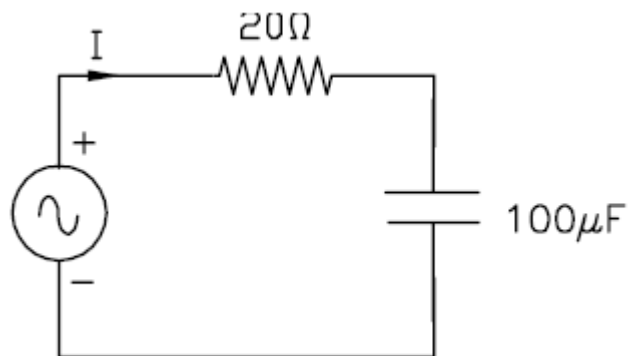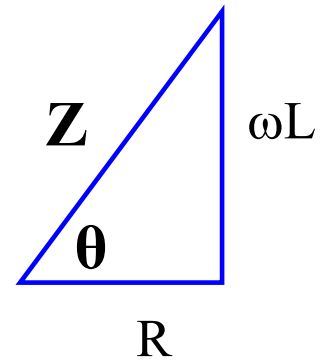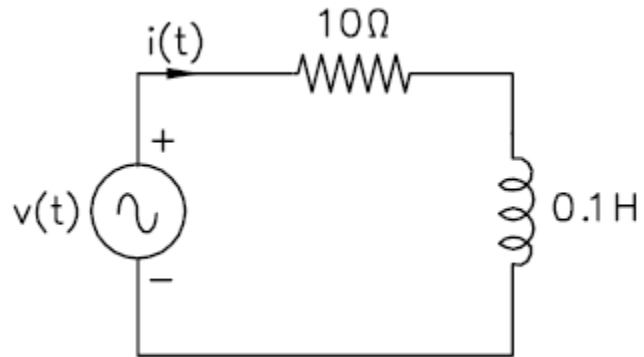

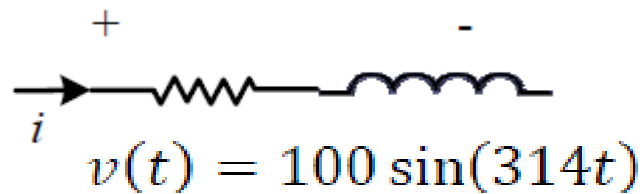
Example 4: A time-varying voltage $v(t)$ is applied across a series combination of 100Ω resistor and 0.1 H inductor. Find the peak amplitude of the resulting current waveform.



Series Resonance

Series circuit comprising inductor, capacitor and resistance has some interesting behavior.

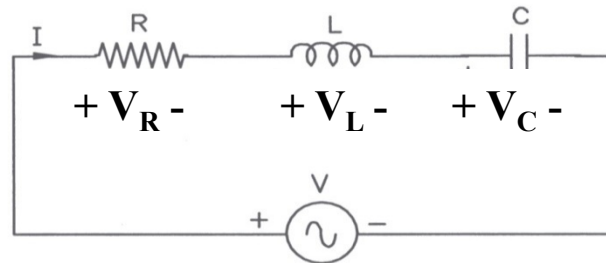This can be analyzed when we connect the circuit across variable frequency source.




Impedance: $Z = R + j\omega L - \frac{j}{\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$

$= |Z| \angle \theta$

Magnitude and phase angle:

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$
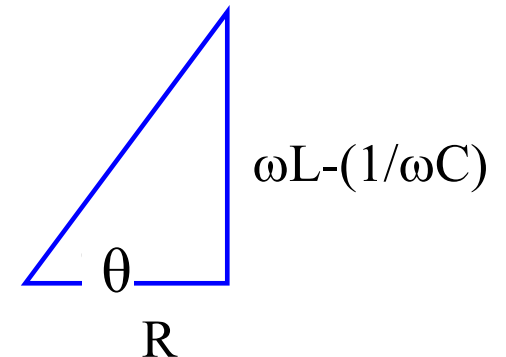
$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$




Current flow in the circuit

$$I = \frac{V}{R + j\omega L - \frac{j}{\omega C}}$$

Frequency response of Series resonant circuit

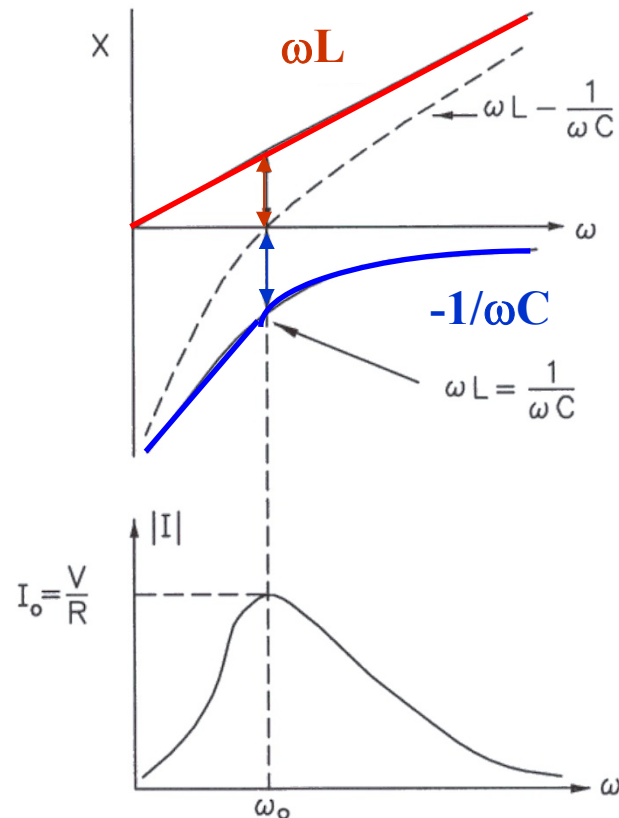Variation of inductive and capacitive reactance with respect to frequency



Variation of current with respect to frequency

$$I = \frac{V}{R + j\omega L - \frac{j}{\omega C}}$$

The resonant frequency (ω_0) is defined to be the frequency at which the circuit impedance is purely resistive (i.e. total reactance is zero).

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$


At resonant frequency:

Impedance of the inductance = Impedance of the capacitance

$$\omega_o L = \frac{1}{\omega_o C}$$



$$\omega_o^2 = \frac{1}{LC}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

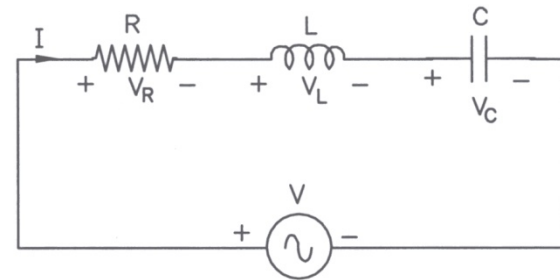


Note that at resonance:

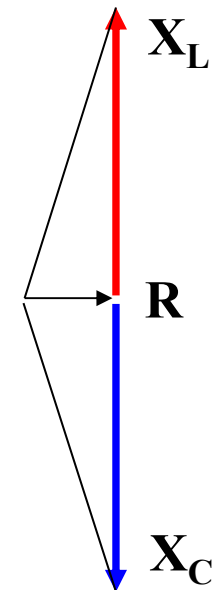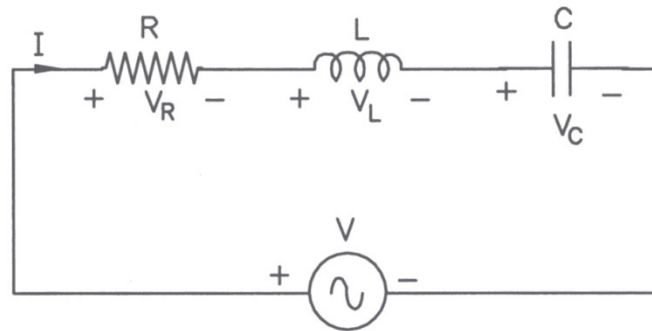The admittance or impedance is purely resistive. In other words, the L-C series combination acts as a short circuit.




Note that at resonance:

The magnitude of I is maximum

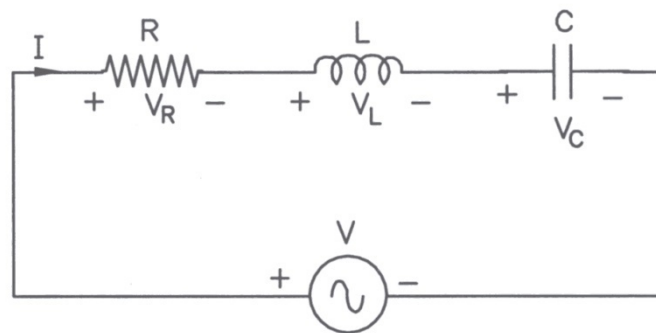



$$I = \frac{V}{R + j\omega L - \frac{j}{\omega C}}$$

$$I_o = \frac{V}{R}$$

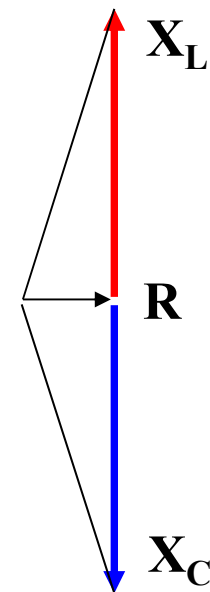

Note that at resonance:

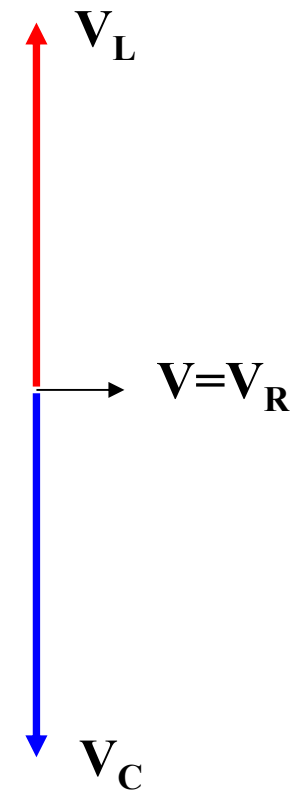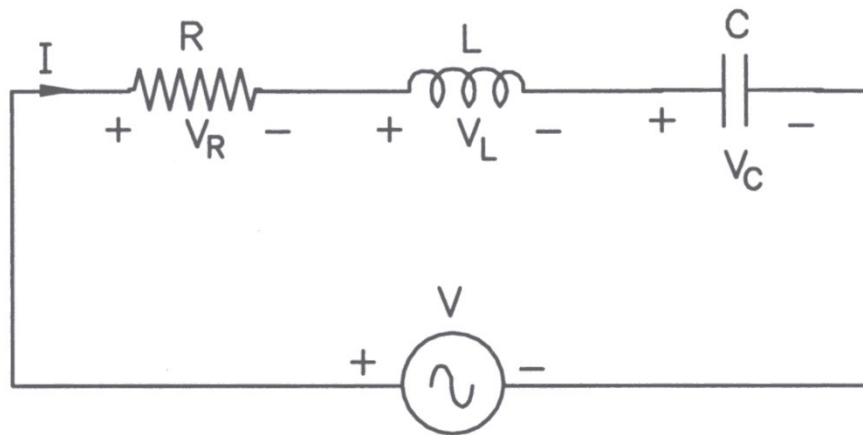The voltage across the inductor or capacitor can be much higher than the source voltage.



Frequency Response of Series RLC Circuits

Current

$$I = \frac{V}{R + j\omega L - \frac{j}{\omega C}}$$

The power dissipated in the circuit is maximum at resonance

$$P(\omega_o) = |I_o|^2 R = \frac{|V|^2}{R}$$

Example 5

For the circuit shown below, determine the **frequency** at which resonance occurs. What is the **current** flow in the circuit at that frequency?

Also, determine the **ratio of voltage across the inductor to that across the resistor**.

$$\omega_o = \frac{1}{\sqrt{LC}} = 5 \times 10^4 \text{ rad/s}$$


$$f_o = \frac{\omega_o}{2\pi} = 7.958 \text{ kHz}$$

$$I_o = \frac{V}{R} = \frac{100}{5} = 20 \text{ A}$$


$$|V_L| = \omega_o L I_o = 4000 \text{ V}$$

$$|V_C| = \frac{I_o}{\omega_o C} = 4000 \text{ V}$$

$$\frac{|V_L|}{|V_R|} = \frac{\omega_o L I_o}{R I_o} = \frac{\omega_o L}{R} = \frac{200}{5} = 40$$

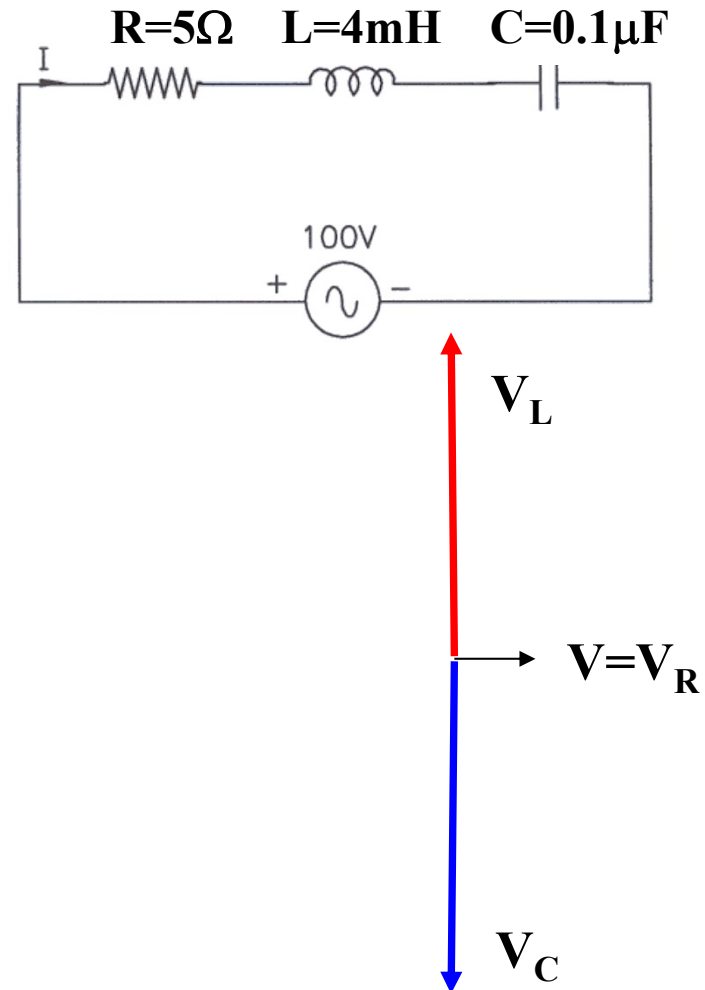

Parallel RLC Circuits

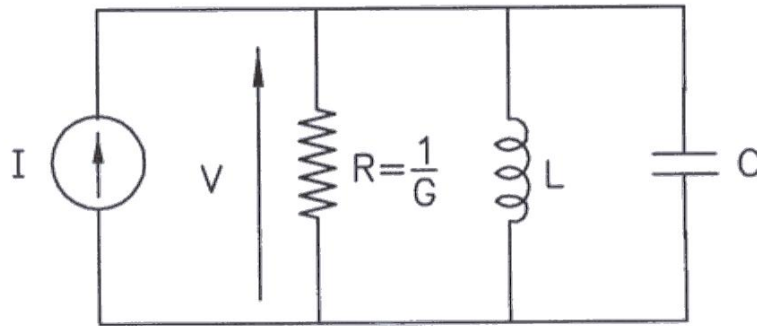


Similar behavior is observed when R, L and C are connected in parallel.

The admittance of the circuit is $Y = G + j\omega C - \frac{j}{\omega L}$

$$|V| = \frac{|I|}{|Y|} = \frac{|I|}{\sqrt{G^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}}$$

At resonance: $\omega_o L = \frac{1}{\omega_o C}$

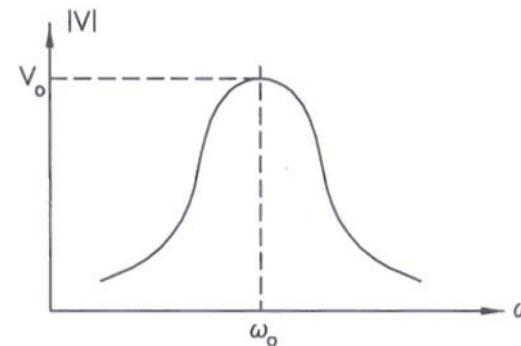

Example 6


A circuit, having a resistance of 4Ω , an inductance of 0.5H and a variable capacitor in series, is connected across a 100V , 50Hz supply. Calculate

- capacitance to give resonance,
- the voltage across the inductance and capacitance and
- the ratio of voltage across the inductor to that across the resistor.

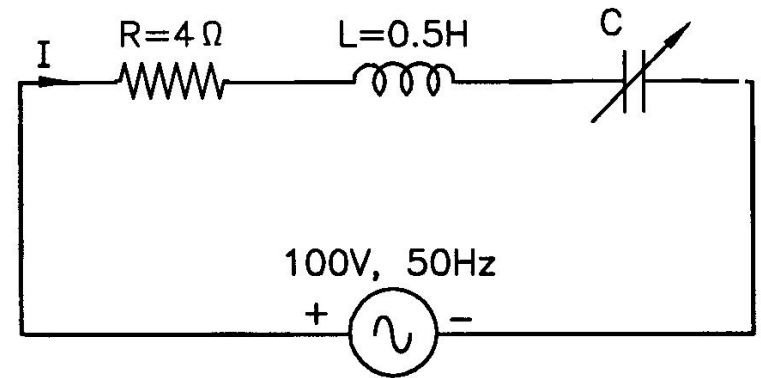(a) For resonance

$$2\pi fL = \frac{1}{2\pi fC}$$

$$C = \frac{1}{(2\pi \times 50)^2 \times 0.5} = 20.3\mu\text{F}$$



(b) At resonance

$$I = \frac{V}{R} = \frac{100}{4} = 25\text{A}$$

$$|V_L| = 2\pi fLI = 2 \times 3.14 \times 50 \times 0.5 \times 25 = 3925\text{V}$$

$$|V_C| = |V_L| = 3925\text{V}$$

(c) Ratio $|V_L|$ to $|V_R|$

$$\frac{|V_L|}{|V_R|} = \frac{2\pi \times 50 \times 0.5}{4} = 39.25$$

