

EE2022 ELECTRICAL ENERGY SYSTEMS

(Tutorial #1 solutions)

Solution Q1:

$$(a) V_1 = \frac{40}{\sqrt{2}} \angle -90^\circ + \frac{60}{\sqrt{2}} \angle -45^\circ + \frac{30}{\sqrt{2}} \angle 0^\circ = \frac{109.72}{\sqrt{2}} \angle -48.69^\circ$$

$$\text{Hence, } v_1(t) = 109.72 \cos(628t - 48.69^\circ)$$

$$(b) V_2 = \frac{20}{\sqrt{2}} \angle -90^\circ + \frac{10}{\sqrt{2}} \angle 60^\circ + \frac{5}{\sqrt{2}} \angle 70^\circ = \frac{9.44}{\sqrt{2}} \angle -44.71^\circ$$

$$\text{Hence, } v_2(t) = 9.44 \cos(314t - 44.71^\circ)$$

Solution Q2:

The current through the resistor and capacitor are respectively,

$$i_i(t) = \frac{v(t)}{R} = 7.071 \cos(314.16t + 10^\circ)$$

$$i_2(t) = C \frac{dv}{dt} = -12.247 \sin(314.16t + 10^\circ)$$

So, the current supplied by the source is

$$\begin{aligned} i(t) &= i_1(t) + i_2(t) \\ &= 7.071 \cos(314.16t + 10^\circ) - 12.247 \sin(314.16t + 10^\circ) \end{aligned}$$

In phasor form, this current can be written as:


$$I = 5 \angle 10^\circ + 8.66 \angle 100^\circ = 10 \angle 70^\circ$$

The time domain expression for the current is

$$i(t) = 14.14 \cos(314.16t + 70^\circ)$$

Solution Q3:

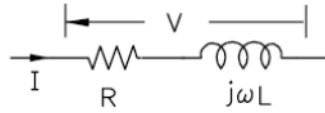Current $i(t) = 2\sqrt{2}\cos(5000t + 30^\circ)\text{mA}$




The impedance and voltage phasors can be determined as follows:

$$I = 2 \times 10^{-3} \angle 30^\circ \text{ A}$$

$$Z = R + j\omega L = 2309 + j5000 \times 0.8 = 2309 + j4000 \Omega$$


$$V = Z I = (2309 + j4000) \times 2 \times 10^{-3} \angle 30^\circ = 9.24 \angle 90^\circ \text{ V}$$
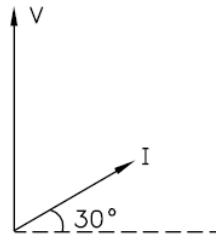
$$v(t) = 9.24 \sqrt{2} \cos(5000t + 90^\circ) \text{ V}$$



Solution Q4:

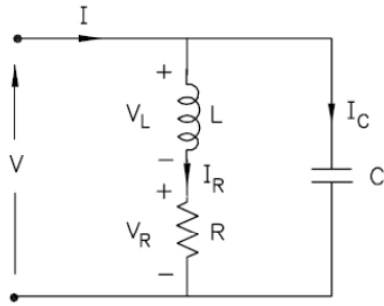$L = 2\text{H}$, $R = 3\Omega$, $C = 0.2\mu\text{F}$ and $v_R = 6\sqrt{2}\cos 2t$ volts.



As $v_R = 6\sqrt{2}\cos 2t$, we have $V_R = 6\angle 0^\circ$. Hence,

$$I_R = \frac{V_R}{R} = \frac{6\angle 0^\circ}{3} = 2\angle 0^\circ \text{ A}$$


$$V_L = j\omega L I_R = j2 \times 2 \times 2\angle 0^\circ = 8\angle 90^\circ \text{ V}$$

$$V = V_R + V_L = 6\angle 0^\circ + 8\angle 90^\circ = 6 + j8 = 10\angle 53.13^\circ \text{ V}$$

$$I_C = j\omega C V = j2 \times 0.2 \times (6 + j8) = -3.2 + j2.4 = 4\angle 143.13^\circ \text{ A}$$


$$I = I_L + I_C = 2 - 3.2 + j2.4 = -1.2 + j2.4 = 2.68\angle 116.57^\circ \text{ A}$$

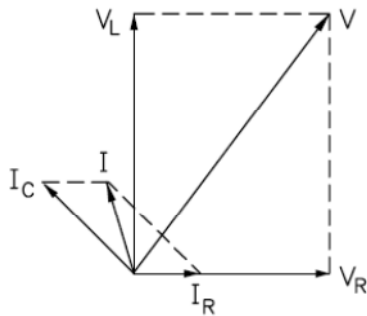The phasor diagram can be drawn as follows:



Solution Q5:

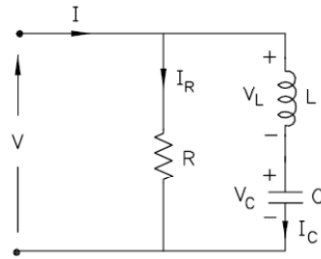$R = 2\Omega$, $L = 3.25\text{mH}$ and $C = 100\mu\text{F}$, $v_C = 100\sqrt{2}\cos(2000t - 90^\circ)$ volts



(a) As $v_C = 100\sqrt{2}\cos(2000t - 90^\circ)$ volts, we get

$$V_C = 100\angle -90^\circ$$

$$I_C = j\omega C V_C = j2000 \times 10^{-4} \times 100\angle -90^\circ = 20\angle 0^\circ \text{ A}$$

$$V_L = j\omega L I_C = j2000 \times 3.25 \times 10^{-3} \times 20\angle 0^\circ = 130\angle 90^\circ \text{ A}$$


(b) So, the voltage V across the circuit and hence currents I_R and I are

$$V = V_C + V_L = 100\angle -90^\circ + 130\angle 90^\circ = -j100 + j130 = j30 \text{ V}$$

$$I_R = \frac{V}{R} = \frac{j30}{2} = 15\angle 90^\circ \text{ A}$$


$$I = I_C + I_R = 20\angle 0^\circ + 15\angle 90^\circ = 20 + j15 = 25\angle 36.9^\circ \text{ A}$$

(c) Phasor diagram:

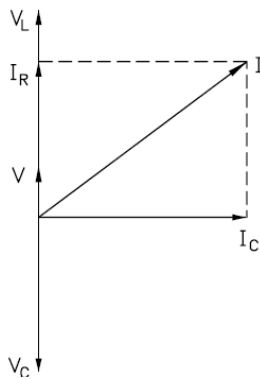

(d) $i(t) = 25\sqrt{2}\cos(2000t + 36.9^\circ) \text{ A}$

Solution Q6:

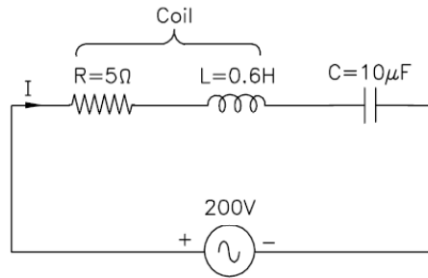

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$I = \frac{V}{Z}$$

Current flow in the circuit will be maximum when the impedance is minimum. Hence,

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}} = 408.248 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = 64.97 \text{ Hz}$$

$$I = \frac{V}{R} = \frac{200}{5} = 40 \text{ A}$$

$$|V_L| = \omega L I = 9798 \text{ V}$$

$$|V_C| = \frac{I}{\omega C} = 9798 \text{ V}$$

$$\frac{|V_L|}{|V|} = \frac{\omega L I}{R I} = \frac{\omega_o L}{R} = \frac{244.95}{5} = 48.99$$

Solution Q7.

(a)

$$P = V_{rms} I_{rms} \Rightarrow I_{rms} = \frac{120 \text{ W}}{200 \text{ V}} = 0.6 \text{ Amp}$$

(b)

$$R_{lamp} = \frac{200 \text{ V}}{0.6 \text{ A}} = 333.33 \Omega$$

(c)

With the capacitor connected in series, the total impedance is $Z = R_{lamp} - jX_C$.

When connected to 240 V source, we still want the voltage across the lamp to the rated value of 200 V, and hence 0.6A current through the lamp.

$$|Z| = \frac{240 \text{ V}}{0.6 \text{ A}} = 400 \Omega$$

$$Z = \sqrt{R_{lamp}^2 + X_C^2} \Rightarrow X_C^2 = Z^2 - R_{lamp}^2$$


$$X_C = \sqrt{400^2 - (333.33)^2} = 221.11 \Omega$$

$$X_C = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_C} = \frac{1}{(2\pi \times 50)(221.11)} = 14.4 \mu\text{F}$$

EE2022 ELECTRICAL ENERGY SYSTEMS

(Tutorial #2 solutions)

Solution Q1:

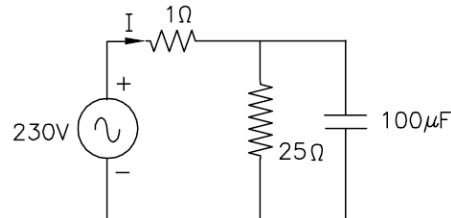

The load admittance is

$$\begin{aligned} Y_L &= \frac{1}{25} + j377 \times 100 \times 10^{-6} \\ &= 0.04 + j0.0377 = 0.05497 \angle 43.3^\circ \end{aligned}$$

So, impedance of the load is

$$Z_L = \frac{1}{Y_L} = 18.193 \angle -43.3^\circ = 13.239 - j12.478 \, \Omega$$

Total impedance of the network is

$$Z = 1 + Z_L = 14.239 - j12.478 = 18.933 \angle -41.23^\circ \, \Omega$$

So, the current supplied by the source is

$$I = \frac{230}{18.933 \angle -41.23^\circ} = 12.15 \angle 41.23^\circ \, \text{A}$$

Apparent power delivered to the load is

$$|S_{Load}| = |Z_L| |I|^2 = 18.193 \times 12.15^2 = 2686 \, \text{VA}$$

Power factor of the load is obtained using the load impedance angle

$$\text{Power Factor} = \cos(-43.3^\circ) = 0.728 \, \text{leading}$$

Power factor is leading because of the capacitive load. Apparent power delivered by the source is

$$|S_{source}| = |V| |I| = 230 \times 12.15 = 2794 \, \text{VA}$$

Solution Q2:

The power drawn by the load is 25 kW. So,



$$P = |V| |I| \cos \theta = 500 \times |I| \times 0.5$$

$$|I| = \frac{25 \times 10^3}{500 \times 0.5} = 100 \text{ A}$$

$$\cos \theta = 0.5$$

$$\theta = 60^\circ$$

$$I = 100 \angle -60^\circ \text{ A}$$

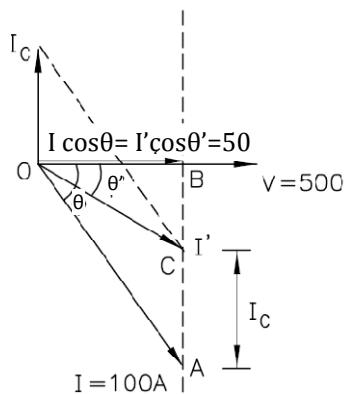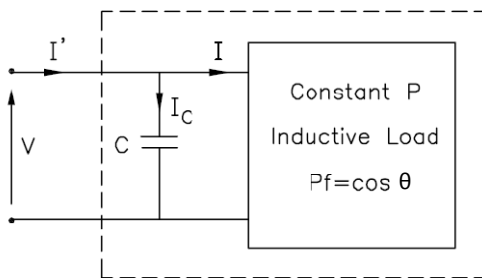

The power factor is improved to 0.95 lagging by connecting a capacitor across the load. Hence,

$$\cos \theta' = 0.95$$

$$\theta' = 18.19 \text{ deg}$$


$$\tan \theta' = \frac{CB}{OB} = \frac{AB - |I_C|}{50} = \frac{100 \sin \phi - |I_C|}{50} = \frac{86.8 - |I_C|}{50}$$

$$|I_C| = 70.37 \text{ A} = \omega C |V| = 2\pi \times 50 \times C \times 500$$

$$C = 448.2 \text{ } \mu\text{F}$$

Solution Q3:

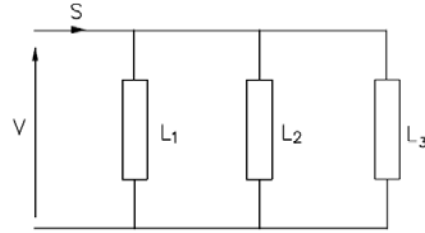L1: 5 kW at 0.8 p.f. lagging, L2: 10 kW at 0.6 p.f. lagging and L3: 15 kW at 0.8 p.f. leading



The complex power consumption of the loads are computed as follows:

$$P_1 = |S_1| \times 0.8$$

$$|S_1| = 6250 \text{ VA}$$

$$S_1 = 6250 \angle 36.87^\circ = 5000 + j3750$$

$$P_2 = |S_2| \times 0.6$$

$$|S_2| = 16666.67 \text{ VA}$$

$$S_2 = 16666.67 \angle 53.13^\circ = 10000 + j13333.33$$

$$P_3 = |S_3| \times 0.8$$

$$|S_3| = 18750 \text{ VA}$$

$$S_3 = 18750 \angle -36.87^\circ = 15000 - j11250$$

Hence, overall power factor as seen by the source can be calculated as:

$$S = S_1 + S_2 + S_3$$

$$= 30000 + j5833.33$$

$$= 30561.87 \angle 11^\circ \text{ VA}$$

$$\text{p.f.} = \cos 11^\circ = 0.982 \text{ lagging}$$

Solution Q4:

As the power delivered is 10kW at 0.5 p.f. lagging,

$$|I| = \frac{P}{V \cos \phi} = \frac{10000}{200 \times 0.5} = 100 \text{ A}$$

$$I = 100 \angle 60^\circ = 50 - j86.6 \text{ A}$$

When a capacitor of $1000\mu F$ is connected across the supply, the capacitor current is

$$I_C = j\omega CV = j314 \times 1000 \times 10^{-6} \times 200 = j62.8 \text{ A}$$

So the total current drawn from the supply is

$$I_T = I + I_C = 50 - j23.8 = 55.38 \angle -25.45^\circ$$

The power factor as seen by the source is

$$\text{p.f.} = \cos(-25.45^\circ) = 0.902 \text{ lagging}$$

Solution Q5:

Current drawn from the substation is

$$|I_1| = \frac{P}{|V| \cos \theta} = \frac{1500 \times 10^3}{500 \times 0.6} = 5000 \text{ A}$$

If the power factor could be improved to unity, then current drawn would be

$$|I_2| = \frac{P}{|V| \cos \theta} = \frac{1500 \times 10^3}{500 \times 1.0} = 3000 \text{ A}$$

The transmission line losses in both the cases are

$$P_{loss1} = R |I_1|^2 = 0.005 \times 5000^2 = 125 \text{ kW}$$

$$P_{loss2} = R |I_2|^2 = 0.005 \times 3000^2 = 45 \text{ kW}$$

So, cost of energy wasted will be high in the first case.

This example illustrates that for the same real power demand, if the power factor of the load decreases, then $|I|$ increases, resulting in heavy transmission line losses.

A poor power factor results in higher current and hence higher power loss.

NATIONAL UNIVERSITY OF SINGAPORE

Department of Electrical Engineering

EE2022 ELECTRICAL ENERGY SYSTEMS

(Solution for Tutorial #3)

6. Line current, $I_{line} = \frac{100}{|10-j9|} = 7.43 \text{ A}$

Line-to-neutral voltage at the source,

$$|V_{Line-neutral}| = |I_{line}| \times |Z_{total}| = 7.43|(2+j3) + (10-j9)| = 99.7 \text{ V.}$$

Line voltage at the source,

$$V_{Line-Line} = \sqrt{3} \times |V_{Line-neutral}| = \sqrt{3} \times 99.7 = 173 \text{ V.}$$

7. We first need to combine the two loads, Δ is transformed to Y,

$$Z_Y = \frac{Z_{\Delta}}{3} = \frac{21 \angle 30^\circ}{3} = 7 \angle 30^\circ \Omega.$$

Now we have two balanced Y connected loads of $9 \angle -60^\circ \Omega$ and $7 \angle 30^\circ \Omega$ in parallel.

The total load impedance per phase, $Z_{Y,total} = \frac{(7 \angle 30^\circ) \times (9 \angle -60^\circ)}{(7 \angle 30^\circ + 9 \angle -60^\circ)} = 5.53 \angle -7.87^\circ \Omega$


The rms line current is found from,

$$I_{line} = \frac{V_{line-to-neutral}}{|Z_Y|} = \frac{V_{line-to-line}}{\sqrt{3}|Z_Y|} = \frac{208}{\sqrt{3} \times 5.53} = 21.7 \text{ A}$$

The total power absorbed by the two loads is ,

$$|P_{3\Phi}| = \sqrt{3}|V_{line-to-line}||I_{line}| \times \text{p.f.} = \sqrt{3} \times 208 \times 21.7 \times \cos(7.87) = 7744.15 \text{ W}$$

8.

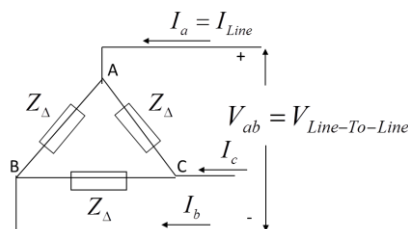

For a balanced three-phase load, $|P_{3\Phi}| = \sqrt{3}|V_{line-to-line}||I_{line}| \times \text{p.f.}$ By substituting

$|V_{line-to-line}| = 208 \text{ V}$, $P_{3\Phi} = 2000 \text{ W}$, $\text{p.f.} = 0.8$ in the above equation, we have $|I_{line}| = 6.94 \text{ A}$.

The phase current that pass through an impedance z can be found from

$$|I_{Phase}| = \frac{|I_{line}|}{\sqrt{3}} = 4.01 \text{ A.}$$

Let $V_{line-to-line} = 208 \angle 0^\circ$, the angle of the phase current can be found from power factor leading.

$$\angle I_{Phase} = +\cos^{-1} 0.8 = 36.87^\circ$$

Note that the phase angle is positive because the power factor is leading.

We can find the impedance of Δ -connected load as follows.

$$Z_{\Delta} = \frac{V_{ab}}{I_{ab}} = \frac{V_{line-to-line}}{I_{phase}} = \frac{208 \angle 0^{\circ}}{4.01 \angle 36.87^{\circ}} = 51.9 \angle -36.87^{\circ} = 41.44 - j31.08 \Omega$$

9.

a) Power triangle for the induction motor.

From $P_{3\Phi} = |S_{3\Phi}| \times p.f.$, given that the real power, $P_{3\Phi} = 400 \text{ kW}$, we can find,


$$|S_{3\Phi}| = \frac{P_{3\Phi}}{p.f.} = \frac{400}{0.8} = 500 \text{ kVA}.$$

Then, the reactive power can be found from,

$$Q_{3\Phi} = |S_{3\Phi}| \times \sin(\cos^{-1}(p.f.)) = 500 \times \sin(\cos^{-1} 0.8) = 300 \text{ kVAR}.$$

Since the power factor is *lagging*, this reactive power is *absorbed* by the induction motor.

The power triangle is given below.

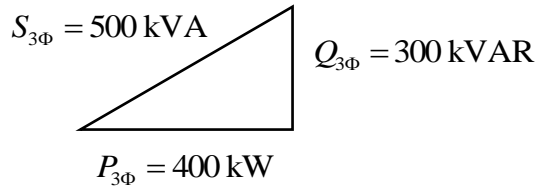

Power triangle for the synchronous motor.


$$S_{3\Phi} = 150 \text{ kVA}$$

$$P_{3\Phi} = |S_{3\Phi}| \times p.f. = 150 \times 0.9 = 135 \text{ kW}.$$

Since the power factor is *leading*, this reactive power is *injected* by the synchronous motor.

$$Q_{3\Phi} = |S_{3\Phi}| \times \sin(\cos^{-1}(p.f.)) = 150 \times \sin(-\cos^{-1} 0.9) = -65.4 \text{ kVAR}.$$

$$P_{3\Phi} = 135 \text{ kW}$$

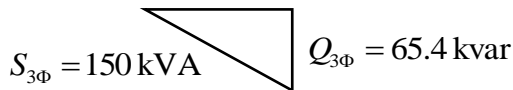

Power triangle for the combined-motor load.


$$P_{3\Phi} = 400 + 135 = 535 \text{ kW}.$$

$$Q_{3\Phi} = 300 - 65.4 = 234.6 \text{ kVAR}$$

Since the reactive power is positive, this reactive power is *absorbed* by the combined-motor load.

The magnitude of apparent power is found below.

$$S_{3\Phi} = \sqrt{|P_{3\Phi}|^2 + |Q_{3\Phi}|^2} = 584.2 \text{ kVA}.$$

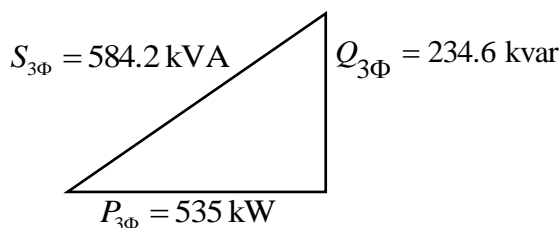

- b) Power factor of the combined-motor load,

$$p.f. = \frac{P_{3\Phi}}{|S_{3\Phi}|} = 0.916$$

Since the load absorbs reactive power, the power factor is 0.916 lagging.

- c) From $|S_{3\Phi}| = \sqrt{3}|V_{line-to-line}||I_{line}|$, we can find the line current below.

$$|I_{line}| = \frac{|S_{3\Phi}|}{\sqrt{3}|V_{line-to-line}|} = \frac{584.2 \times 10^3}{\sqrt{3} \times 4160} = 81.1 \text{ A}$$

- d) To make the source power factor unity, the reactive power supplied by the capacitor bank,

$$Q_{c,3\Phi} = -234.6 \text{ kVAR.}$$

For a delta connected capacitor bank, the voltage applied to the capacitor at each phase is the line-to-line voltage.

$$Q_{c,1\Phi} = \frac{Q_{c,3\Phi}}{3} = -78.2 \text{ kVAR}$$

The capacitive reactance at each phase, $X_{c,1\Phi}$, can be found from $Q_{c,1\Phi} = \frac{|V_{line-to-line}|^2}{X_{c,1\Phi}}$.

We have,

$$X_{c,1\Phi} = \frac{|V_{line-to-line}|^2}{Q_{c,1\Phi}} = \frac{4160^2}{-78.2 \times 10^3} = -221.3 \Omega.$$

The capacitive reactance is then -j221.3 Ω .

- e) With the capacitor bank installed, power factor=1.

Active power delivered by the source, $P_{3\Phi} = \sqrt{3}|V_{line-to-line}||I_{line}| \times p.f. = 535 \text{ kW}$.

With the capacitor bank installed, power factor=1. The line current magnitude is found below.

$$|I_{line}| = \frac{|P_{3\Phi}|}{\sqrt{3}|V_{line-to-line}| \times p.f.} = \frac{535 \times 10^3}{\sqrt{3} \times 4160 \times 1} = 74.3 \text{ A}$$

Note that once the power factor is adjusted to 1, the line current magnitude is reduced from 81.1 A to 74.3 A. This helps to reduce the power losses in the transmission lines.

NATIONAL UNIVERSITY OF SINGAPORE
Department of Electrical Engineering
EE2022 ELECTRICAL ENERGY SYSTEMS
(Solution for Tutorial #4)

4.

Using the short length model, $l = 16 \text{ km}$, $Z = 16 \times (0.125 + j0.4375) = 2 + j7 \Omega$. Per phase equivalent model is shown in Fig. 1.

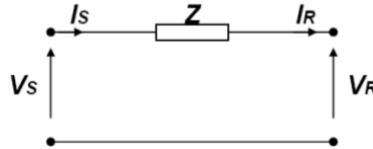


Fig.1

The voltage and current at sending and receiving end can be found from the following.

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & 2 + j7 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

The receiving end voltage is given as 64 kV line-to-line. Let the voltage at the load be reference angle, we can find the voltage per phase as follows.

$$V_R = \frac{64 \times 10^3}{\sqrt{3}} \angle 0^\circ = 36.95 \angle 0^\circ \text{ kV}.$$

The receiving end current, I_R , can be found from the complex power consumed by the load at the receiving end, denoted by $S_{3\phi,R}$, of 70 MVA, 0.8 lagging.

$$|I_R| = \frac{|S_{1\phi,R}|}{|V_R|} = \frac{|S_{3\phi,R}|}{3|V_R|} = \frac{70 \times 10^6}{3 \times 36.95 \times 10^3} = 631.48 \text{ A}$$

The angle of receiving end current is found from power factor. The angle is negative because power factor is lagging.

$$\angle I_R = -\cos^{-1}(0.8) = -36.87^\circ$$

Sending end voltage is found below.

$$V_S = V_R + (2 + j7) \times I_R = 36950.42 \angle 0^\circ + (2 + j7) \times (631.48 \angle -36.87^\circ) = 40.71 \angle 3.91^\circ \text{ kV}.$$

Note that the no load voltage for short transmission line model is the same as sending end voltage at full load.

$$\text{Voltage regulation} = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\% = \frac{40.71 - 36.95}{36.95} \times 100\% = 10.17\%$$

The complex power delivered at the load is given as 70 MVA, 0.8 lagging. Thus, real power delivered at the load is

$$P_{3\phi,R} = |S_{3\phi}| \times p.f. = 70 \times 0.8 = 56 \text{ MW}.$$

We then find real power at the sending end. For a short transmission line, sending end current is the same as receiving end current, $I_S = I_R = 631.48 \angle -36.87^\circ$.

The sending end three-phase complex power is found from $S_{3\phi,S} = 3V_S I_S^*$,

$$S_{3\phi,S} = 3 \times 40707.94 \angle 3.91^\circ \times 631.48 \angle 36.87^\circ = 58.39 + j50.37 \text{ MVA}$$

Three-phase real power at sending end $P_{3\phi,S} = 58.39 \text{ MW}$. The transmission efficiency is found below.

$$\eta = \frac{P_{R,3\phi}}{P_{S,3\phi}} \times 100\% = \frac{56}{58.39} \times 100\% = 95.91 \%$$

5.

The nominal pi-circuit is a medium-length line model, which is shown in Fig. 2.

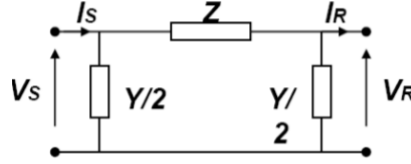


Fig.2

Given per phase series impedance per km and shunt admittance per km, the total impedance and admittances are found.

$$Z = 200 \times (0.08 + j0.48) = 16 + j96 \Omega$$

$$Y = 200 \times (j3.33 \times 10^{-6}) = (j6.66 \times 10^{-4}) \text{ siemens}$$

The ABCD parameters in the medium-length model can be found from below.

$$A = D = \frac{ZY}{2} + 1 = 0.9680 + j0.0053$$

$$B = Z = 16 + j96 \Omega$$

$$C = Y \left(1 + \frac{ZY}{4} \right) = (-1.7742 \times 10^{-6} + j6.5535 \times 10^{-4}) \text{ S}$$

At full load, the line delivers 250 MW at 0.99 p.f. lagging at 220 kV (line-to-line). We first find the receiving end voltage per phase.

$$V_R = \frac{220 \times 10^3}{\sqrt{3}} \angle 0^\circ = 127.02 \angle 0^\circ \text{ kV}.$$

The receiving end current, I_R , can be found from the complex power consumed by the load at the receiving end, denoted by $P_{3\phi,R}$, of 250 MW, 0.99 lagging.

$$|I_R| = \frac{|P_{3\phi,R}|}{3|V_R| \times \text{p.f.}} = \frac{250 \times 10^6}{3 \times 127.02 \times 10^3 \times 0.99} = 662.69 \text{ A}.$$

The angle of receiving end current is found from power factor. The angle is negative because power factor is lagging.

$$\angle I_R = -\cos^{-1}(0.99) = -8.11^\circ$$

Using ABCD parameters found earlier, together with receiving end voltage and current, the sending end voltage and current is found.

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 155.40 \angle 23.58^\circ \text{ kV} \\ 635.38 \angle -0.34^\circ \text{ A} \end{bmatrix}$$

6.

This is a medium length line as shown in Fig. 2.

Given per phase series impedance per km and shunt admittance per km, the total impedance and admittances are found.

$$Z = 130 \times (0.036 + j \times 100 \Pi \times 0.8 \times 10^{-3}) = 4.68 + j32.67 \Omega$$

$$Y = 130 \times (j \times 100 \Pi \times 0.0112 \times 10^{-6}) = (j4.57 \times 10^{-4}) \text{ Siemens}$$

The ABCD parameters in the medium-length model are found below.

$$A = D = \frac{ZY}{2} + 1 = 0.9925 + j0.0011$$

$$B = Z = 4.68 + j32.67$$

$$C = Y \left(1 + \frac{ZY}{4}\right) = (-0.2448 \times 10^{-8} + j0.4557 \times 10^{-5})$$

The receiving end load is 270 MVA with 0.8 lagging power factor at 325 kV. $V_R = \frac{325}{\sqrt{3}} \angle 0^\circ \text{ kV}$,

Find the receiving end current, I_R ,

$$|I_R| = \frac{|S_{3\Phi,R}|}{3|V_R|} = \frac{270 \times 10^6}{3 \times 187.64 \times 10^3} = 479.65 \text{ A.}$$

When power factor is 0.8, lagging.

$$I_R = |I_R| \angle -\cos^{-1}0.8 = 479.64 \angle -36.87^\circ \text{ A}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 187.64 \times 10^3 \angle 0^\circ \\ 479.64 \angle -36.87^\circ \end{bmatrix} = \begin{bmatrix} 197764 \angle 3.30^\circ \text{ V} \\ 430.27 \angle -27.66^\circ \text{ A} \end{bmatrix}$$

At full load, $|V_{R,FL}| = 187.64 \text{ kV}$.

$$\text{At no load, } I_R = 0, |V_{R,NL}| = \left| \frac{V_S}{A} \right| = \left| \frac{197764 \angle 3.30^\circ}{(0.9925 + j0.0011)} \right| = 199.25 \text{ kV}$$

$$\% \text{ Regulation} = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\% = \frac{199.25 - 187.64}{187.64} \times 100\% = 6.19\%.$$

Transmission line efficiency:

$$S_{3\Phi,S} = 3V_S I_S^* = 3 \times 197764 \angle 3.30^\circ \times 430.27 \angle -27.66^\circ = 218.9 + j131.3 \text{ MVA.}$$

$$\eta = \frac{P_{R,3\Phi}}{P_{S,3\Phi}} \times 100\% = \frac{270 \times 0.8}{218.9} \times 100\% = 98.7\%$$

When power factor is 0.95, lagging.

$$I_R = |I_R| \angle -\cos^{-1}p.f. = 479.64 \angle -18.19^\circ \text{ A}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 187.64 \times 10^3 \angle 0^\circ \\ 479.64 \angle -18.19^\circ \end{bmatrix} = \begin{bmatrix} 193796 \angle 4.26^\circ \text{ V} \\ 456.70 \angle -7.88^\circ \text{ A} \end{bmatrix}$$

At full load, $|V_{R,FL}| = 187.64 \text{ kV}$.

$$\text{At no load, } I_R = 0, |V_{R,NL}| = \left| \frac{V_S}{A} \right| = \left| \frac{193796 \angle 4.26^\circ}{(0.9925 + j0.0011)} \right| = 195.26 \text{ kV}$$

$$\% \text{ Regulation} = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\% = \frac{195.26 - 187.64}{187.64} \times 100\% = 4.06\%.$$

Transmission line efficiency:

$$S_{3\Phi,S} = 3V_S I_S^* = 3 \times 193796 \angle 4.26^\circ \times 456.70 \angle -7.88^\circ = 259.58 + j55.84 \text{ MVA.}$$

$$\eta = \frac{P_{R,3\Phi}}{P_{S,3\Phi}} \times 100\% = \frac{270 \times 0.95}{259.58} \times 100\% = 98.8\%$$

When the power factor is close to one, the transmission line efficiency and voltage regulation is improved.