

2nd Mid-term Test @ LT5

- Monday, March 30th 5:00pm to 5:45pm @ LT5
- 10%
- Materials (Lectures 11-17, Tutorials 5-6):
 - Transformers
 - Renewable Energy
 - Per Unit Analysis
- Format:
 - Closed book.
 - 45 minutes.



EE2022 Electrical Energy Systems

Per Unit Analysis- Three Phase

Lecturer : Dr. Sangit Sasidhar (elesang)

Slides prepared by Dr. Panida Jirutitijaroen

Department of Electrical and Computer Engineering

Outline


- Single-phase per unit analysis (cont)
- Three-phase transformers
 - Possible connections
 - Phase shift introduced by delta-wye or wye-delta connections
 - Per unit equivalent models
- Three-phase per unit analysis

Advantages of Per Unit Analysis

- Simplify calculation by eliminating transformers.
- Helps to spot errors in the data
 - p.u. is more uniform compare to actual impedance value of different sizes of equipments.
- Helps to detect abnormality in the system
 - Operator at control center can spot over/under voltage/current rating easily.




Steps of Per Unit Analysis

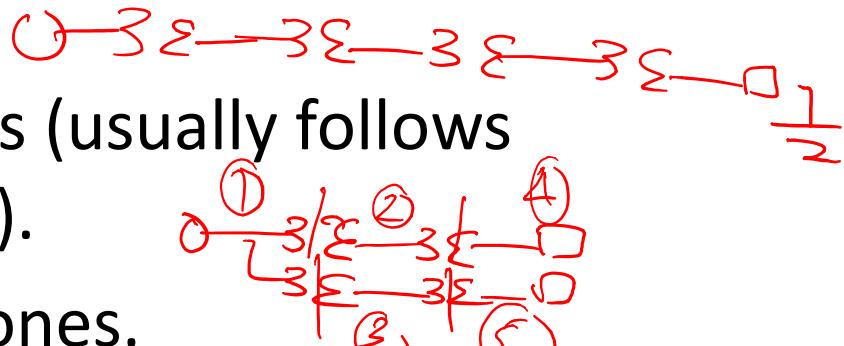1. Choose $\underline{S_B^{1\Phi}}$ for the system.
 2. Select V_B for different zones (usually follows transformer voltage ratings).
 3. Calculate Z_B for different zones.
 4. Express all quantities in p.u.
 5. Draw impedance diagram and solve for p.u. quantities.
 6. Convert back to actual quantities if needed.
- 


$$Z_B = \frac{V_B^2}{S_B}$$

An Equivalent Circuit for Transformers

Copper losses Leakage reactance

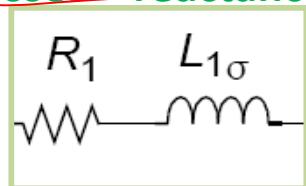


Iron losses (core)

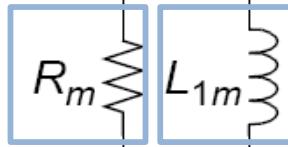


Reflected copper losses and leakage reactance of secondary winding.

$$L_{2\sigma} \left(\frac{N_1}{N_2}\right)^2 R_2 \left(\frac{N_1}{N_2}\right)^2$$

Magnetizing susceptibility

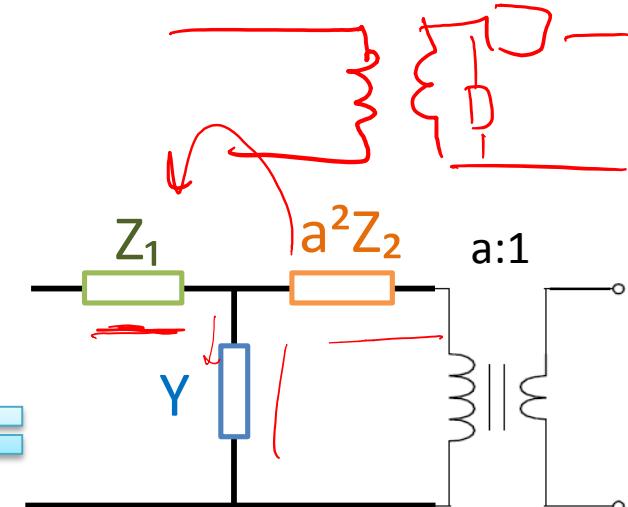


Simplification

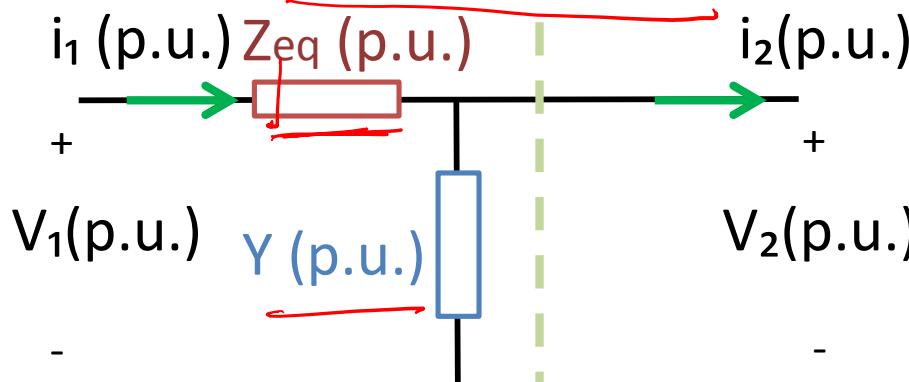


$$Z_{eq} = Z_1 + a^2 Z_2$$

Per unit circuit

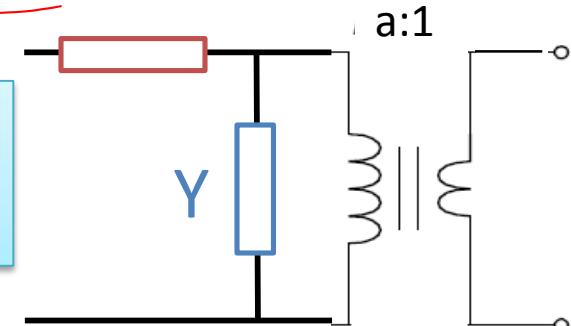


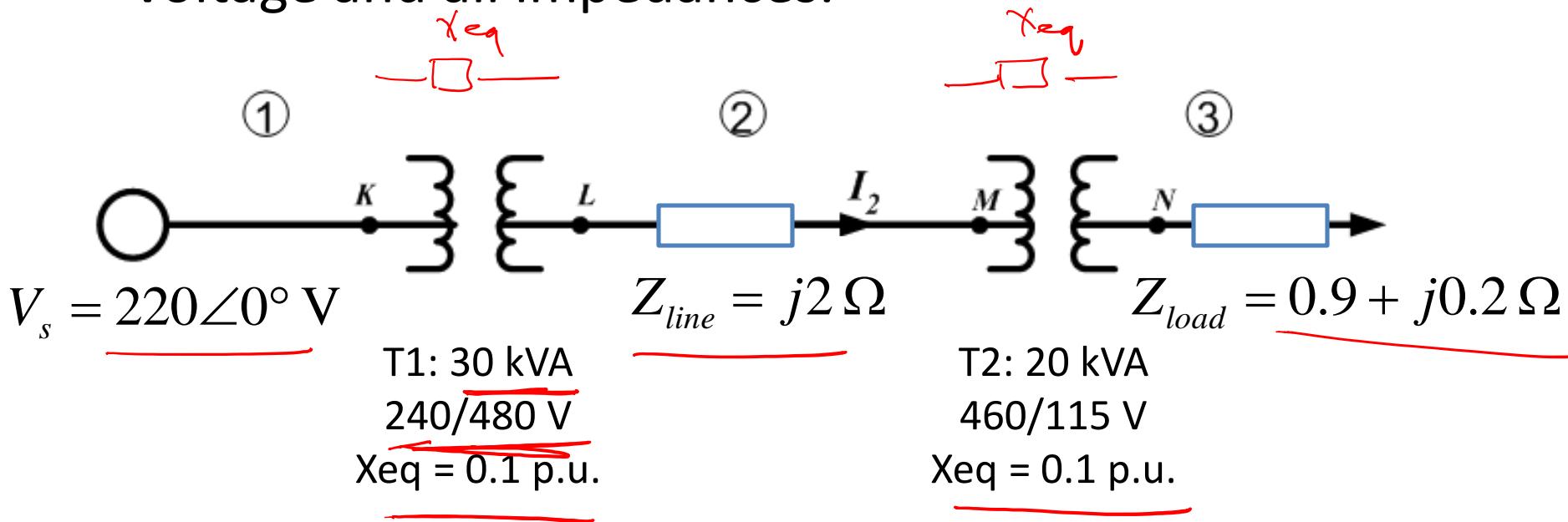Example : 1Φ, Per Unit Analysis

- Three zones of a single-phase circuit are shown below. Use base value of 30 kVA and 240 V in zone 1, draw per unit circuit and find per unit value of source voltage and all impedances.



$$S_B = 30 \text{ kVA}$$

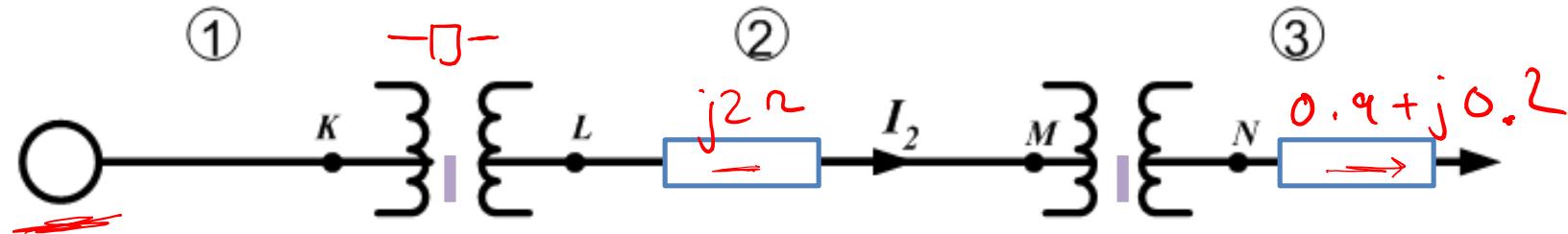

$$V_{B1} = 240 \text{ V}$$

$$V_{B2} = \left(\frac{480}{240} \right) \times 240 = 480 \text{ V}$$


$$Z_{B1} = \frac{240^2}{30 \times 10^3} = 1.92 \Omega$$

$$\begin{aligned} V_{\text{source}} &= \frac{220 \angle 0^\circ}{240} \\ &= 0.9167 \angle 0^\circ \text{ pu} \end{aligned}$$

$$Z_{\text{line pu}} = \frac{j2}{7.68}$$

$$= j0.2604 \text{ pu}$$
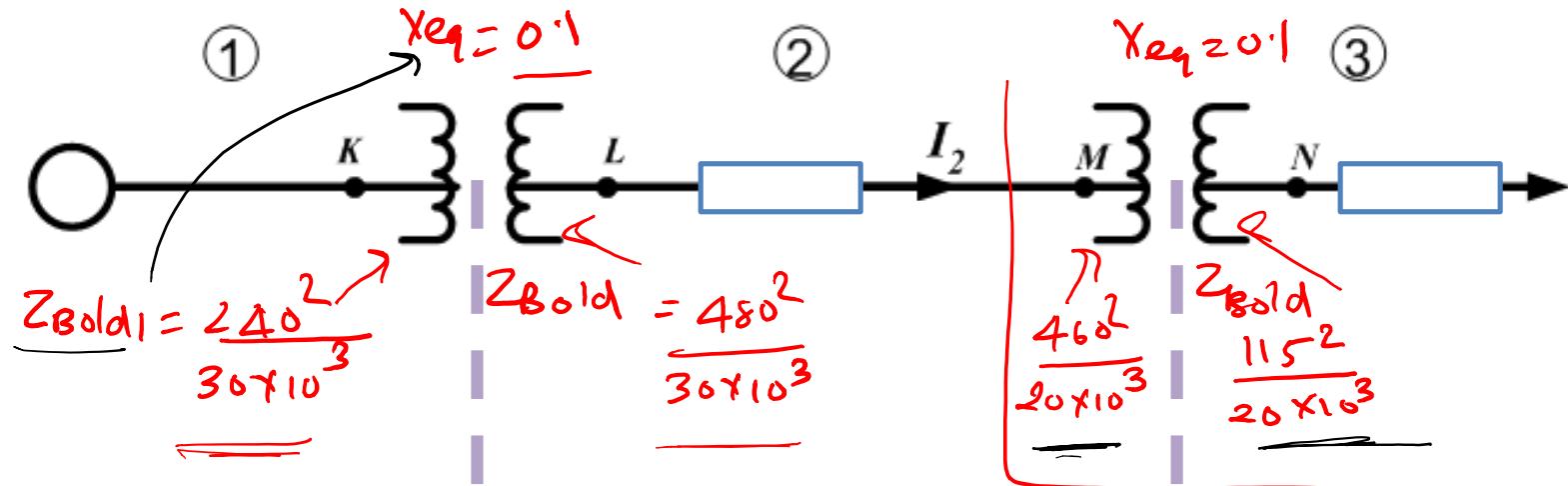
$$\begin{aligned} Z_{B3} &= \frac{120^2}{30 \times 10^3} = 0.48 \Omega \\ Z_{\text{load pu}} &= \frac{0.9 + j0.2}{0.48} \\ &= 1.875 + j0.4167 \text{ pu} \end{aligned}$$



$$Z_{actual} = \frac{240^2}{30 \times 10^3} \times 0.1$$

$$Z_{actual} = \frac{480^2}{30 \times 10^3} \times 0.1$$

$$Z_{pu} = \frac{\frac{240^2}{30 \times 10^3} \times 0.1}{1.92}$$

$$= 0.1$$


$$Z_{pu \text{ new}} = \frac{\frac{480^2}{30 \times 10^3} \times 0.1}{7.68}$$

$$= 0.1$$

$$Z_{actual} = \frac{460^2}{20 \times 10^3} \times 0.1$$

$$Z_{pu \text{ new}} = \frac{\frac{460^2}{20 \times 10^3} \times 0.1}{7.68}$$

$$= 0.1378 \text{ pu}$$

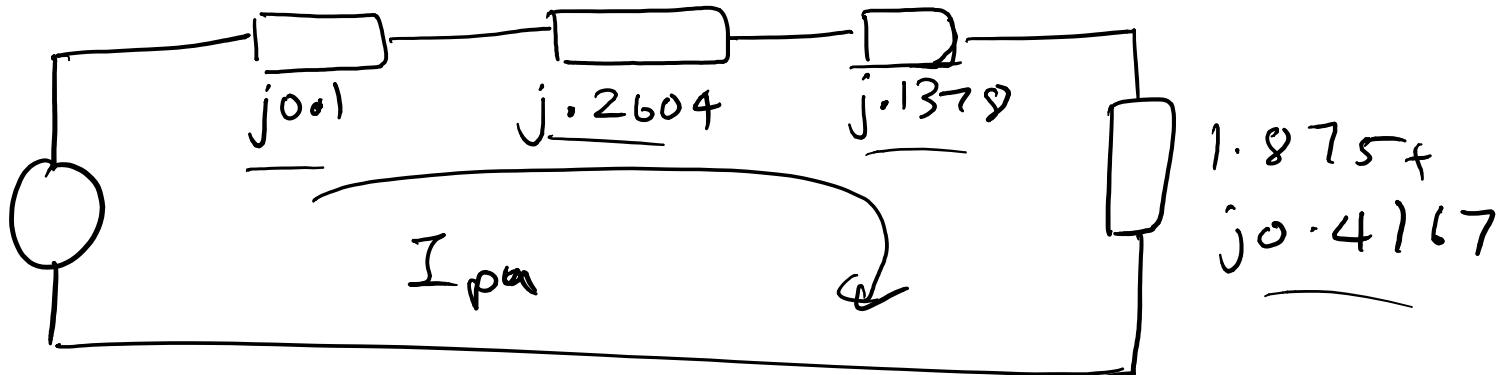$0.9167 \angle 0^\circ V$


$$I_{pu} = \frac{V_s}{Z_{eq}} = \frac{0.9167 \angle 0^\circ}{j.1 + j.2604 + j.1378 + 1.875 + j.4167}$$

$$= 0.4395 \angle -26.01^\circ pu$$

$$I_1 = I_{pu} \times I_{B1}$$

$$I_3 = I_{pu} \times I_{B3}$$

$$I_2 = I_{pu} \times I_{B2}$$


Three-phase transformer connections

Phase shift

Per-unit equivalent models

THREE PHASE TRANSFORMERS


Three-Phase Transformers

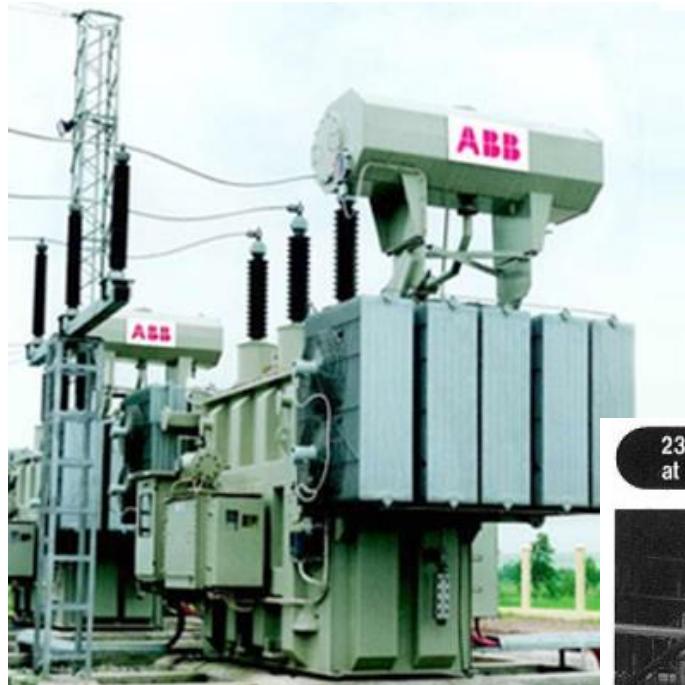

*Pole-mounted
three single-phase
transformers.*




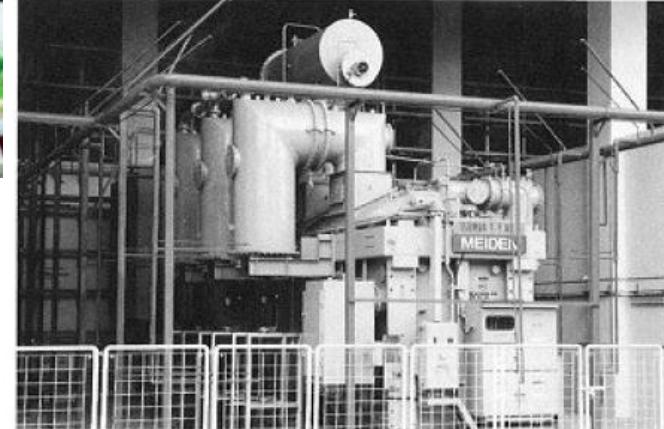*Three-phase transformers
at substations*











Source: <http://www.meidensg.com.sg>

Three Single-Phase Transformers








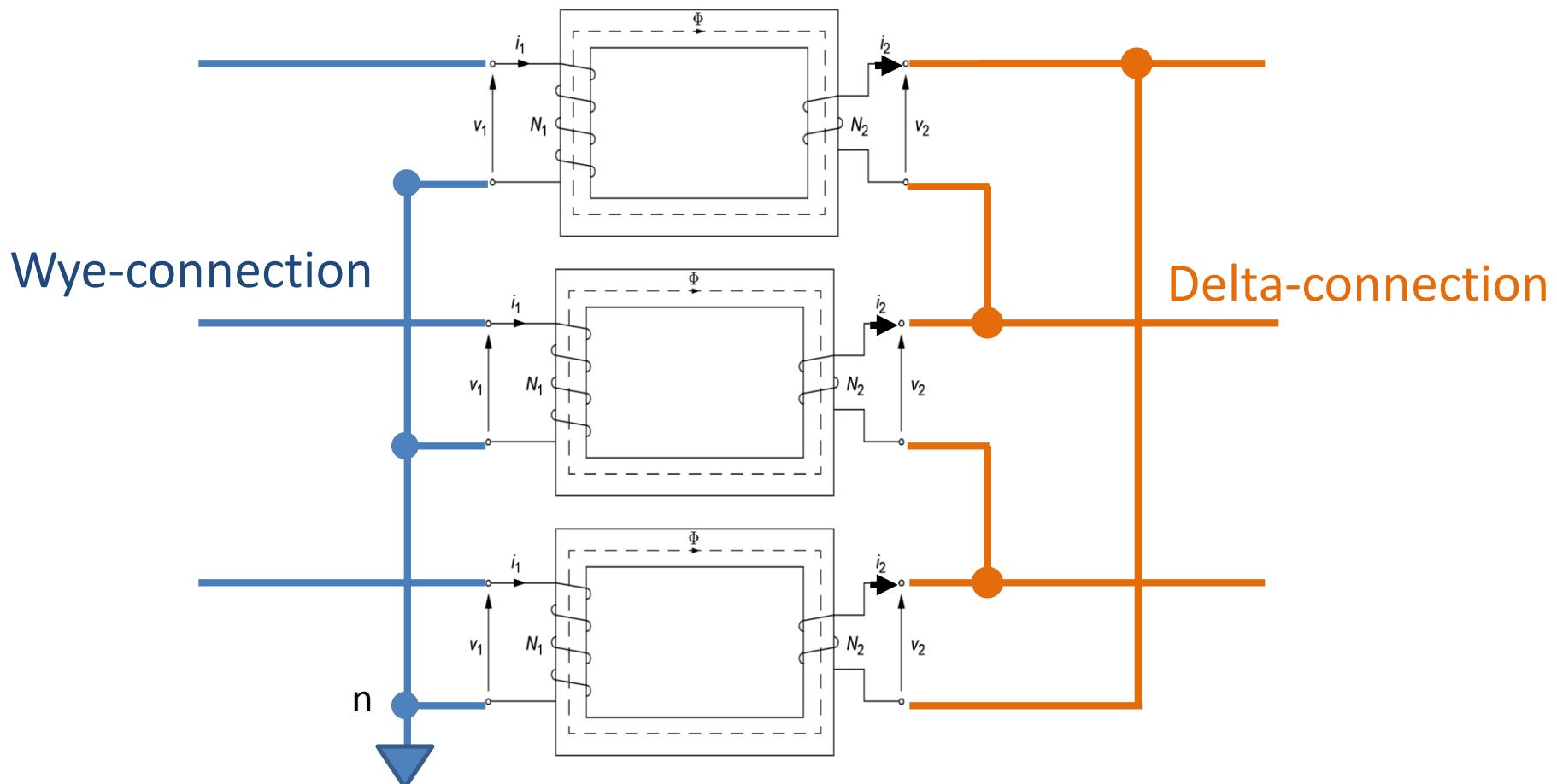


3Φ Transformer Connection

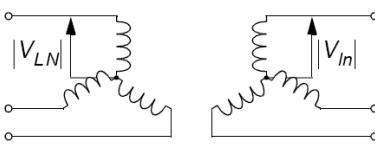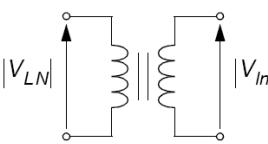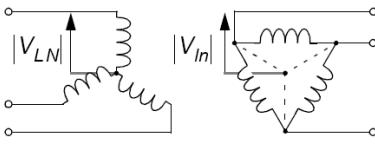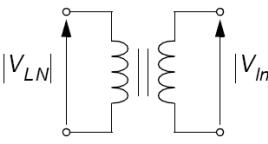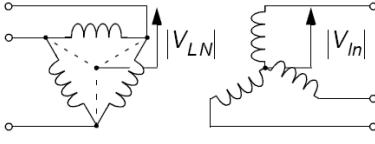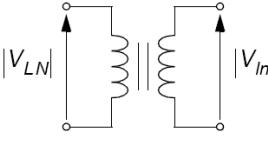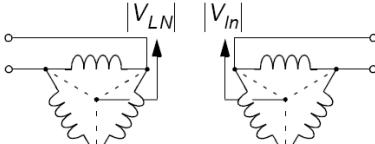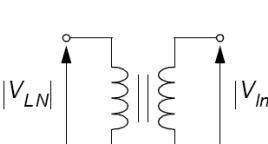
designation	winding connection	single-phase equivalent
Yy		
Yd		
Dy		
Dd		

- The voltage rating of a three phase transformer is the ratio between **line-to-line** voltage at the primary side and **line-to-line** voltage at the secondary side.
- The single-phase equivalent shows line-to-neutral voltage.
- For Y-Y and Δ-Δ transformers, voltage and current in both primary and secondary are in phase. The ratio of the voltage and current follows the turn ratio of the transformer.
- The same does not apply to Y-Δ and Δ-Y connections.

3Φ Transformer Connection

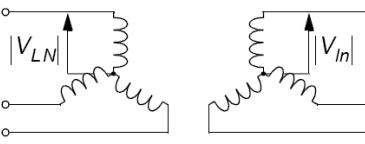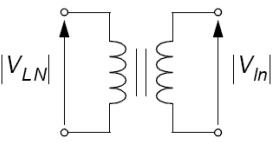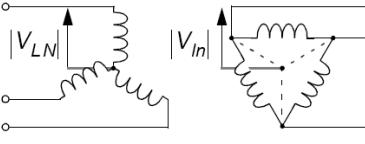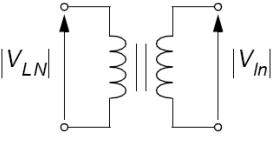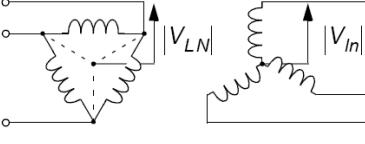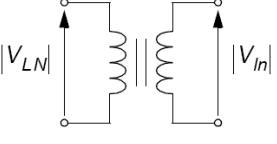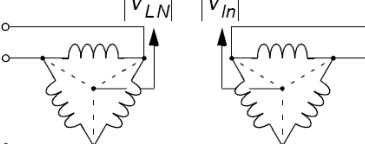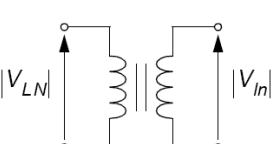
designation	winding connection	single-phase equivalent
Yy		
Yd		
Dy		
Dd		

Per phase per unit circuit

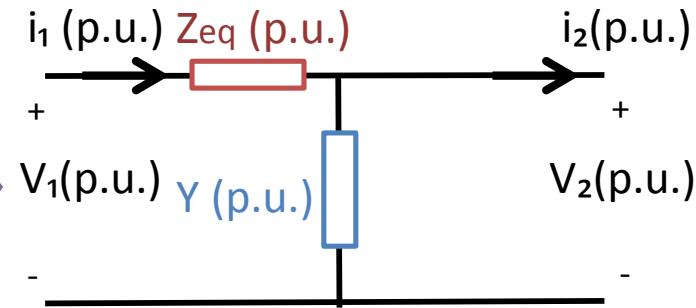


Wye-Delta and Delta-Wye transformer connections introduce some phase shift to the voltage.


Per phase per unit circuit

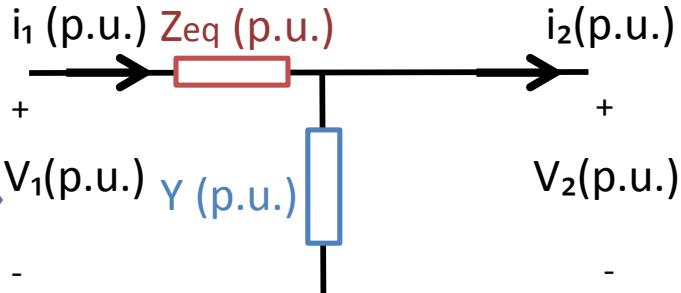

Wye-Delta 3Φ Transformers

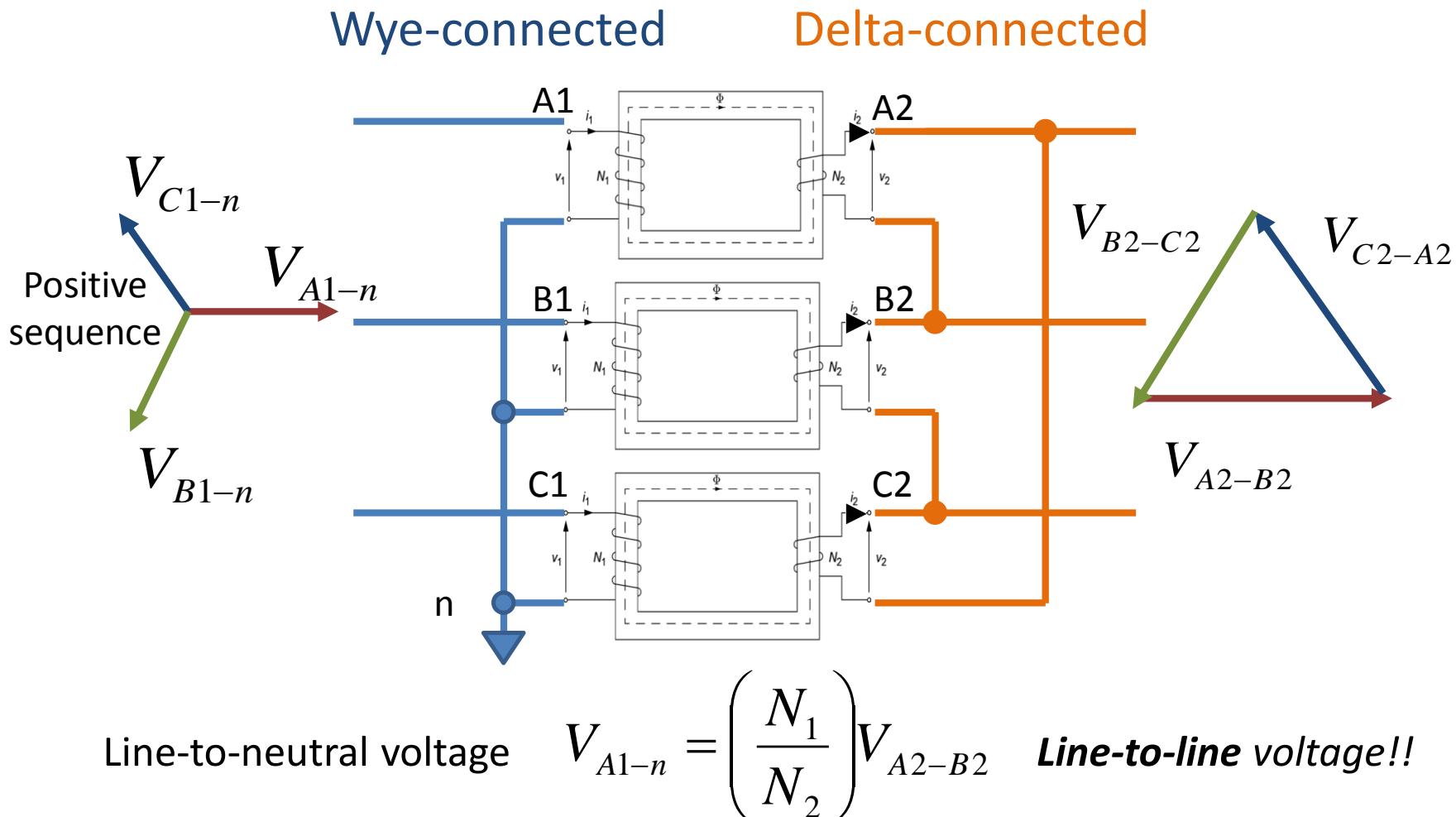

Wye-Delta 3Φ Transformer

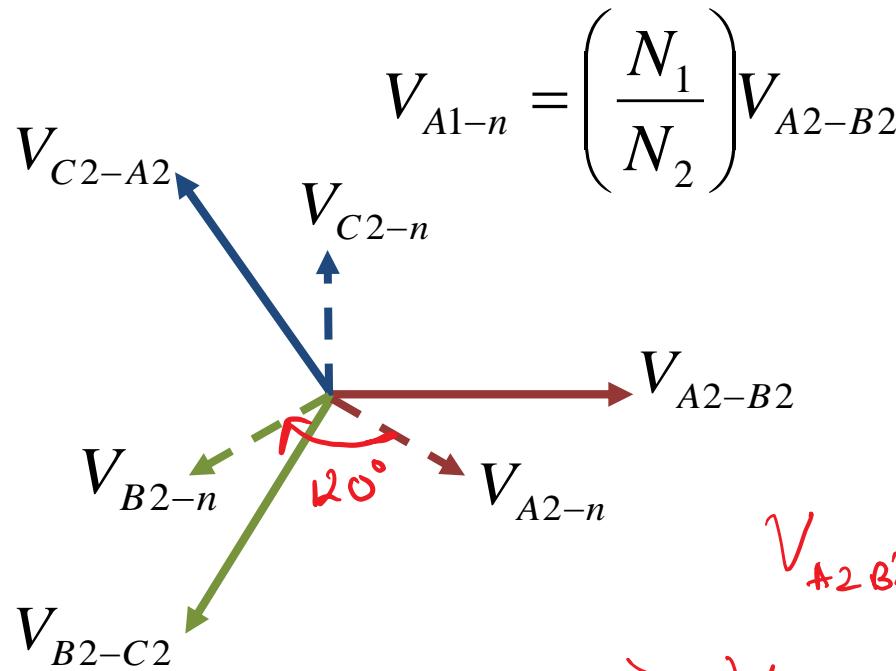

$$V_{A1-n} = \left(\frac{N_1}{N_2} \right) V_{A2-B2}$$

For a positive sequence,

$$\begin{aligned} V_{A2-B2} &= V_{A2n} - V_{B2n} \\ &= V_{A2n} - V_{A2n} L - 120^\circ \\ V_{A2B2} &= \sqrt{3} V_{A2n} \angle 30^\circ \end{aligned}$$

$$\Rightarrow V_{A1n} = \boxed{\left(\frac{N_1}{N_2} \right) \sqrt{3} V_{A2n} \angle 30^\circ}$$


The line-to-neutral voltage at the primary side leads the line-to-neutral voltage at the secondary side by 30 degrees. The same is true for the current.

Y-Δ 3Φ Transformer: Per Phase Model





For a positive sequence voltage source,


$$\frac{V_{A1n}}{\sqrt{V_{A2n}}} = \frac{1\angle 30^\circ}{1}$$
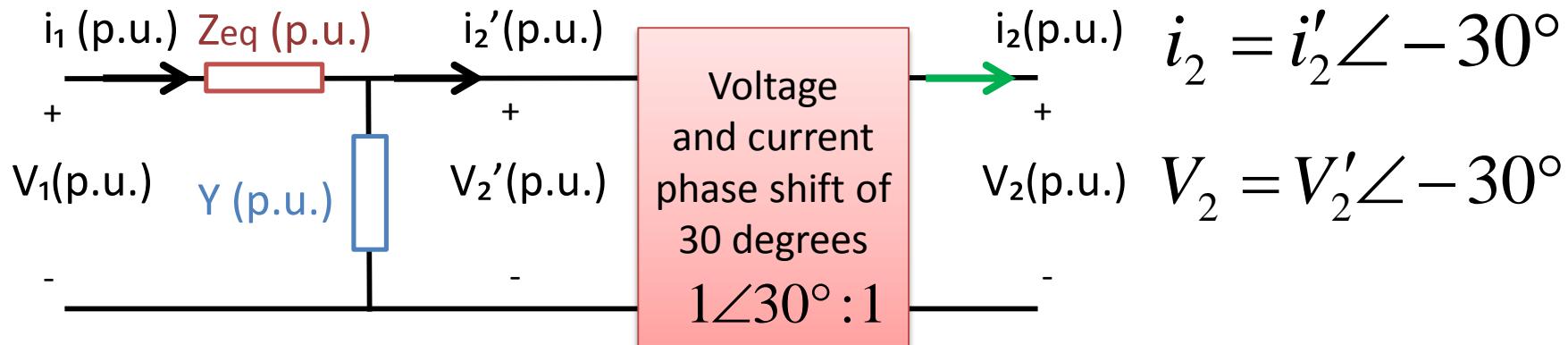
$$V_{A1-n} = \left(\frac{N_1}{N_2} \right) \sqrt{3} V_{A2-n} \angle 30^\circ \quad \Rightarrow \quad \angle V_{A1-n} : \angle V_{A2-n} = 1\angle 30^\circ : 1$$



3Φ Transformer Per Unit Model

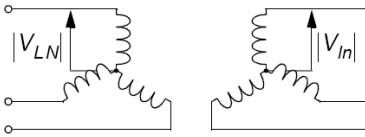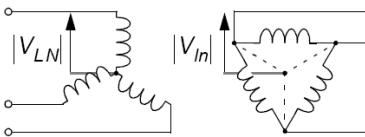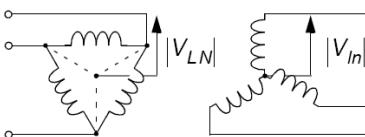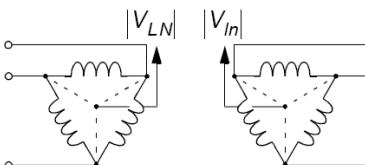designation	winding connection
Yy	
Yd	
Dy	
Dd	

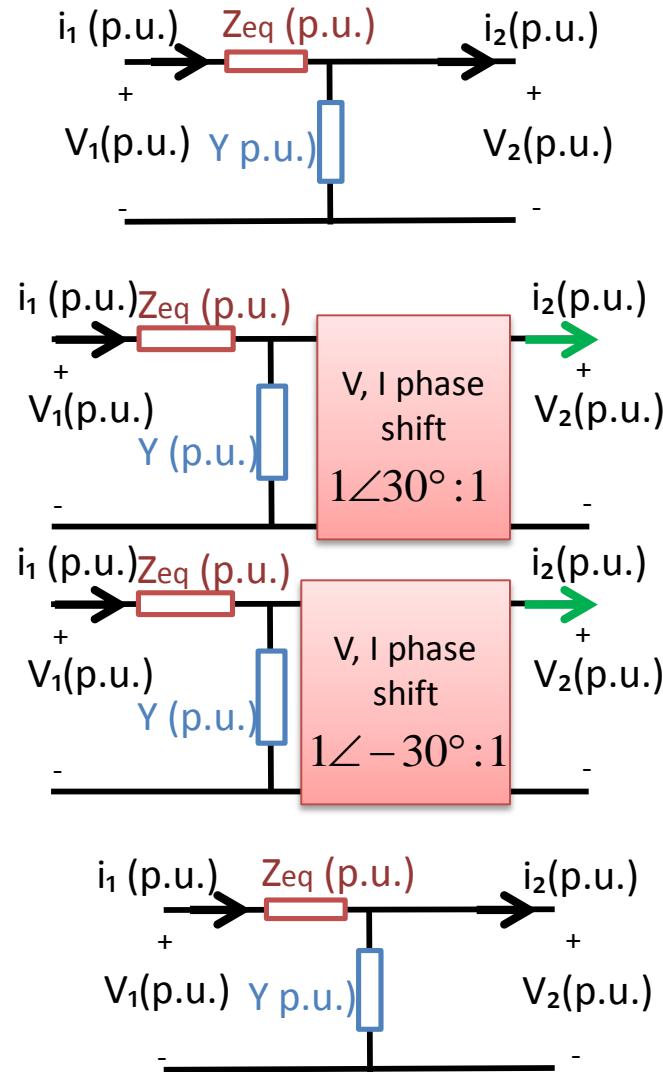

Three-Phase Transformer Nameplate


High voltage 13.2kV
(line-to-line)

Low voltage 480V
(line-to-line) or
277V(line-to-
neutral)

Circuit connection,
 Δ -connected at high
voltage and Y-
connected at low
voltage

KVA rating, 1000 KVA

Impedance = 5.75%

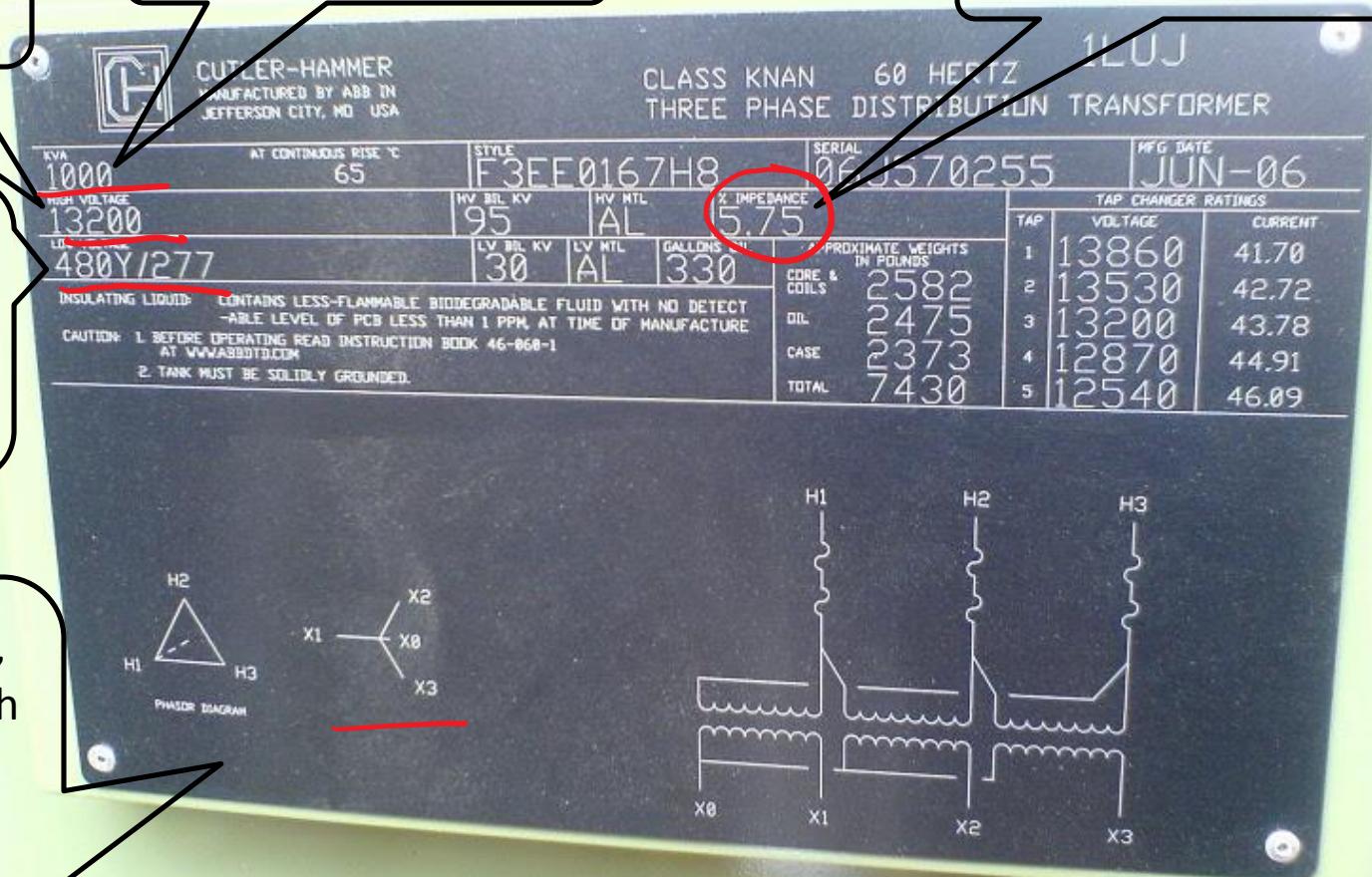

Per Unit Quantity: 3Φ

Base Value: 3Φ

Steps of Calculation: 3Φ

THREE PHASE PER UNIT ANALYSIS

Recall: Per Unit Quantity


- The per unit quantity of voltage, current, power and impedance is found from dividing the actual quantity by a base value of that quantity.

$$\text{per - unit quantity} = \frac{\text{actual quantity}}{\text{base value of quantity}}$$

- Per unit value is denoted by ‘p.u.’.
- The base value quantity typically follows transformer rating.
- The per unit values are the same irrespective of the sides of the transformer.

Per Unit Analysis in 3Φ Circuit

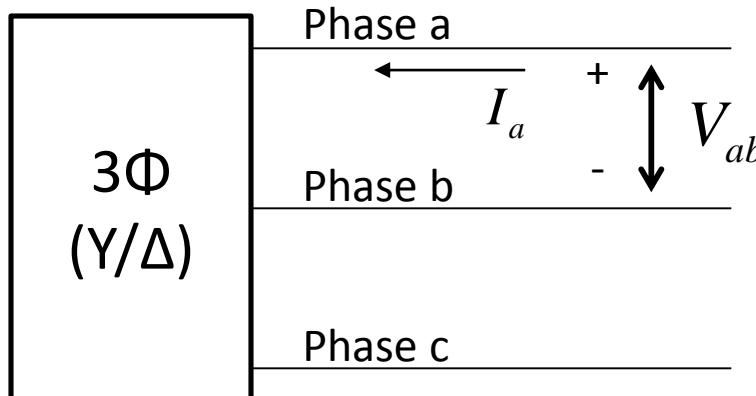- Recall that in three phase circuit:
 - Voltage is given as line-to-line voltage.
 - Current is given as line current.
 - Apparent power is given as three-phase power.



$$|S_{3\Phi}| = \sqrt{3} |V_{\text{Line-To-Line}}| |I_{\text{Line}}|$$

Base Value for Voltage: 3Φ Case

- Base values are **real numbers**, denote by subscript '*B*'.
- Voltage base values follow transformer voltage ratings.

$$V_B^{\text{line-to-neutral}} = \frac{V_B^{\text{line-to-line}}}{\sqrt{3}}$$

- Note that the voltage ratios are given as line-to-line voltage at both ends. This means that it already incorporates the factor of $\sqrt{3}$ term in Y or Δ configurations. (see slide 17 again)

Base Value for Power: 3Φ Case

- Only **single** base complex power $S_B^{3\Phi}$ in the system.
- The base value of power is used to normalize the quantity. Thus, the base values of real power, reactive power, and complex power are all the same real number.

$$S_B^{3\Phi} = P_B^{3\Phi} = Q_B^{3\Phi}$$

Base Value for Current and Impedance: 3Φ Case

- Current base values are calculated from the base power and base voltage.

$$I_B^{3\Phi} = \frac{S_B^{3\Phi}}{\sqrt{3} V_B^{L-L}}$$

- Impedance base values (same value for impedance, resistance, or reactance) are calculated from voltage and current.

$$Z_B = \frac{V_B^{L-N}}{I_B^{L-N}} = \frac{(V_B^{L-N})^2}{S_B^{3\Phi}}$$

Change of Base Value

- Manufacturers usually specify equipment impedances in per unit values together with voltage ratings (V) and apparent power rating (VA).
- The impedance base values can be found from the ratings of the equipment.
- Different equipment has different ratings.
- We may need to calculate per unit values on the new basis.
- Note that this process is exactly the same as in single-phase case.

Per Unit Value for Impedance

$$Z_{\text{ACTUAL}}^{3\phi} = Z_{\text{OLD}}^{3\phi \text{ pu}} Z_{\text{BOTH}}^{3\phi} = Z_{\text{NEW}}^{3\phi \text{ pu}} Z_{\text{BNEW}}^{3\phi}$$

$$\Rightarrow Z_{\text{pu}}^{3\phi \text{ NEW}} = \frac{Z_{\text{BOLD}}^{3\phi}}{\frac{Z_{\text{BNEW}}^{3\phi}}{S_{\text{BOLD}}^{3\phi}}} \cdot Z_{\text{pu}}^{3\phi \text{ OLD}}$$

$$= \frac{(V_{\text{BOLD}}^{L-L})^2}{S_{\text{BOLD}}^{3\phi}} \times \frac{S_{\text{BNEW}}^{3\phi}}{(V_{\text{BNEW}}^{L-L})^2} \cdot Z_{\text{pu}}^{3\phi \text{ OLD}}$$

$$Z_{\text{pu}}^{3\phi \text{ NEW}} = \left(\frac{V_{\text{BOLD}}^{L-L}}{V_{\text{BNEW}}^{L-L}} \right)^2 \times \left(\frac{S_{\text{BNEW}}^{3\phi}}{S_{\text{BOLD}}^{3\phi}} \right) \times Z_{\text{pu}}^{3\phi \text{ OLD}}$$


Steps of Calculation: 3Φ Case

1. Choose $S_B^{3\Phi}$ for the system.
2. Select $V_B^{\text{line-to-neutral}}$ or $V_B^{\text{line-to-line}}$ for different zones.
3. Calculate Z_B for different zones.
4. Express all quantities in p.u.
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.

Note that the **per unit circuit** is the circuit in **per-phase analysis** with normalization of the voltage magnitude at different locations. This means that **the phase of voltage** in per unit analysis **refers to the line-to-neutral voltage**.

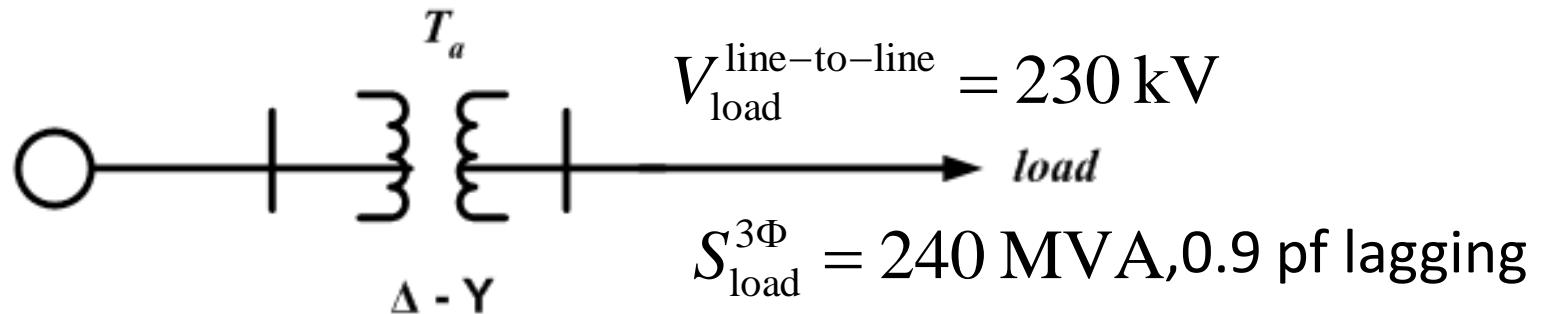Example : Δ -Y 3Φ Transformer

- Three-phase generator rated 300 MVA, 23 kV supplying a system Y-connected load of 240 MVA, 0.9 power factor lagging at 230 kV through a 330 MVA 23 Δ / 230Y kV **step-up** transformer of leakage reactance 11%.
- Use **base values at the load of 100 MVA and 230 kV**, find the current supplied by the generator. Use *load voltage for an angle reference*.




Example : Base Values

330 MVA
 $23\Delta / 230Y$ kV

$$S_B^{3P} = 100 \text{ MVA}$$

$$X_{T_1} = 0.11 \text{ p.u.}$$

T_a

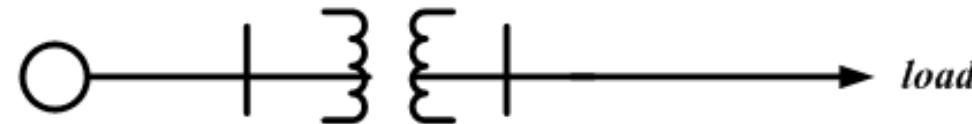

$$V_{B1}^{L-L} = \frac{23}{230} \times 230 = 23 \text{ kV}$$

$$V_{B2}^{L-L} = 230 \text{ kV}$$

$$Z_{B1} = \frac{(V_{B1}^{L-L})^2}{S_B^{3P}} = \frac{(23 \times 10^3)^2}{100 \times 10^6} = 5.29 \Omega$$

$$Z_{B2} = \frac{(V_{B2}^{L-L})^2}{S_B^{3P}} = \frac{(230 \times 10^3)^2}{100 \times 10^6} = 529 \Omega$$

$$I_{B1} = \frac{S_B^{3P}}{\sqrt{3} V_{B1}^{L-L}} = \frac{100 \times 10^6}{\sqrt{3} \times 23 \times 10^3} = 2510.2 \text{ A}$$


$$I_{B2} = \frac{S_B^{3P}}{\sqrt{3} V_{B2}^{L-L}} = \frac{100 \times 10^6}{\sqrt{3} \times 230 \times 10^3} = 251.02 \text{ A}$$

Example : Transformer Reactance

$$S_B^{3\Phi} = 100 \text{ MVA}$$

$$330 \text{ MVA } X_{T1} = 0.11 \text{ p.u.}$$

23Δ / 23Y kV

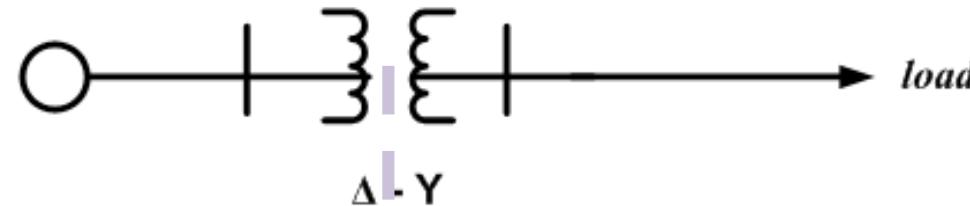


$$X_{pu}^{\text{new}} = \left(\frac{V_{BOLD}^{L-L}}{V_{BNEW}^{L-L}} \right)^2 \times \left(\frac{S_B^{3\Phi}}{S_B^{3\Phi \text{ new}}} \right) \times X_{pu}^{\text{old}} = \left(\frac{23 \times 10^3}{23 \times 10^3} \right)^2 \times \left(\frac{100 \times 10^6}{330 \times 10^6} \right) \times 0.11$$

$$= 0.0333 \text{ pu}$$

$$X_{pu}^{\text{new}} = \left(\frac{230 \times 10^3}{230 \times 10^3} \right)^2 \times \left(\frac{100 \times 10^6}{330 \times 10^6} \right) \times 0.11 = 0.0333 \text{ pu.}$$

Example : Load Voltage and Current

$$S_B^{3\Phi} = 100 \text{ MVA}$$


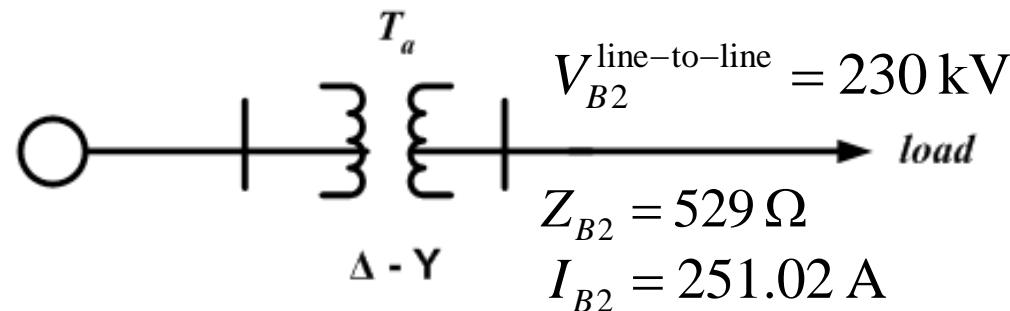


$$S_L = \sqrt{3} V_{L-L} I_L \Rightarrow I_L = \frac{S_L}{\sqrt{3} V_{L-L}}$$

$$\Rightarrow I_L = \frac{240 \times 10^6}{\sqrt{3} \times 230 \times 10^3} = 602.45 \text{ A}$$

$$\angle I_L = \cos^{-1} 0.9 = 25.85^\circ \Rightarrow I_L = 602.45 \angle -25.85^\circ$$

Example : Per Unit Values

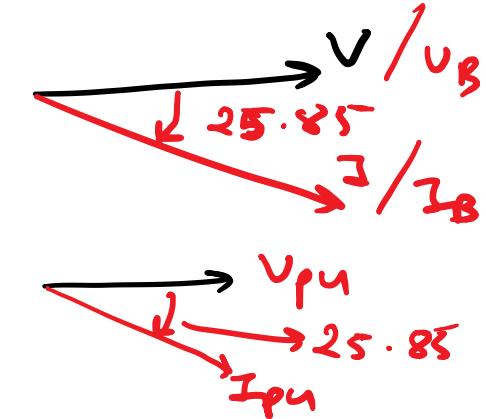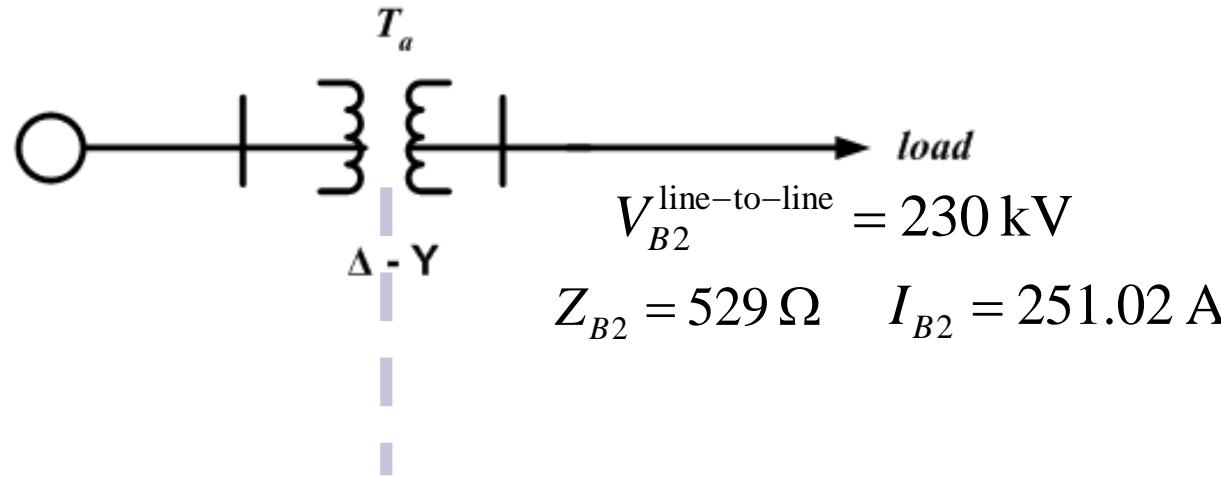


$$V_{LOAD,pu} = \frac{V_{LOAD}^{L-L}}{V_B^{L-L}} \quad L_0 = \frac{230 \times 10^3}{230 \times 10^3} L_0 = 120 \text{ pu}$$

$$I_{LOAD,pu} = \frac{I_{LOAD}}{I_B} = \frac{602.45 L - 25.85}{251.02} = 2.4 L - 25.85 \text{ pu}$$

Example : Per Unit Circuit

$$I_{B1} = 2510.2 \text{ A}$$

$$I_{B2} = 251.02 \text{ A}$$

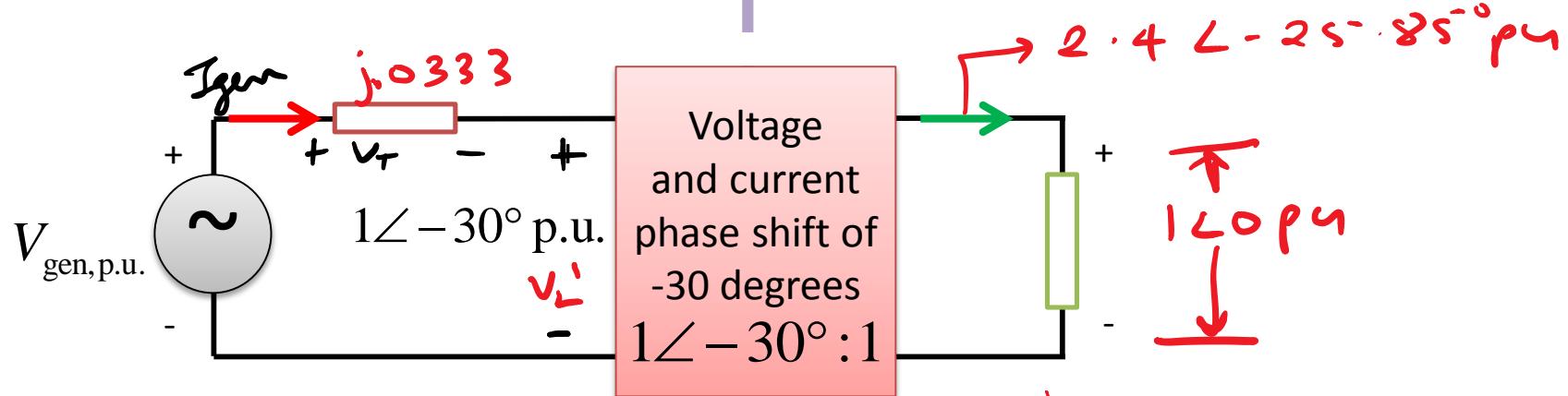

$$\frac{I_{gen\text{ p.u.}}}{I_L \text{ p.u.}} = \frac{1L - 30}{1}$$

$$\Rightarrow I_{gen\text{ p.u.}} = 2 \cdot 4L - 25 \cdot 85 \times 1L - 30$$

$$= 2 \cdot 4L - 55 \cdot 85^\circ \text{ p.u.}$$

$$I_{gen} = (2 \cdot 4L - 55 \cdot 85) \times 2510.2 \Rightarrow I_{gen} = 6024.5 L - 35 \cdot 85 \text{ A}$$

Summary

- Revision of 1-Φ per unit analysis
- 3Φ transformers $\xrightarrow{\Delta Y}$ $\xrightarrow{Y\Delta}$ { Phase Shift
- 3Φ - per unit analysis

	1 Φ	3Φ
1)	$S_B^{1\Phi}$	$S_B^{3\Phi}$
2)	V_{B1}, V_{B2}, \dots each zone	$V_{B1}^{L-L}, V_{B2}^{L-L}, \dots$ each zone
3)	$Z_B^{sp} = \frac{V_{B1}^2}{S_B^{1\Phi}}$... each zone	$Z_B^{sp} = \frac{(V_{B1}^{L-L})^2}{S_B^{3\Phi}}$ each zone
4)	$I_{B1} = \frac{S_B^{1\Phi}}{V_{B1}}, \text{ each zone}$	$I_{B1}^{3\Phi} = \frac{S_B^{3\Phi}}{\sqrt{3} V_{B1}^{L-L}}$ each zone