

is larger ~~than~~ than the complex power value obtained in 6.1c by ~~1.1~~ \Rightarrow Var as the transmission line also consumes real and reactive power.

d The ratings of some electrical apparatus are represented in VA ~~be~~ instead of watts because they may not be purely resistive and will consume reactive power ^{in addition to real power consumed}. Such apparatus are computers and other electronics. It is also possible to calculate the real and reactive power consumed by the ^{apparatus power} rating given in VA of the electrical apparatus.

e From 6.1c,

$$P = 15.1 \text{ W}$$

$$Q = 10.7 \text{ var}$$

$$Q_{\text{old}} = Q_{\text{new}} = 0$$

$$10.7 = Q_c = 0$$

$$Q_c = 10.7 \text{ var}$$

$$Q_c = IV$$

$$j10.7 = I_c(19.22)$$

$$I_c = j0.55671 \text{ A}$$

$$Z_c = \frac{j19.22}{j0.55671}$$

$$-j \frac{1}{\omega C} = -j34.524$$

$$\frac{1}{2\pi(50)C} = 34.524$$

$$C = 92.2 \mu\text{F}$$

~~theoretically~~

$$\begin{aligned} f \quad Z_c &= -j \frac{1}{\omega C} \\ &= -j \frac{1}{2\pi(50)(30 \times 10^{-6})} \\ &= -j106.10 \end{aligned}$$

$$\begin{aligned} Z_{\text{total}} &= \left(\frac{1}{16 + j(89.1 \times 10^{-3})(2\pi(50))} + \frac{1}{33 + j(2\pi(50))(26 \times 10^{-3})} + \frac{1}{-j \frac{1}{2\pi(50)(30 \times 10^{-6})}} \right)^{-1} \\ &= (32.24 \angle -60.25^\circ + 34.00 \angle -13.90^\circ + 0.009425 \angle 90^\circ)^{-1} \\ &= (j0.02457 + 0.04394)^{-1} \\ &= 19.86 \angle 29.213^\circ \end{aligned}$$

$$I = \frac{V}{Z}$$