

EE2022

Electrical Energy Systems

Lecture 10: Summary



EE2022 Syllabus – Part 1

1. Introduction

✓ Energy and its various forms; Importance of Electrical Energy in secondary form

2. Introduction to Electrical Power

✓ Active, Reactive and Apparent Power; Concept of Power factor, lagging, leading and unity power factor operation

3. Three phase systems

Single- and three-phase power system; Star and Delta connection; Relationship between phase and line quantities; per-unit representation.

4. Generation, Transmission and Distribution Network

✓ Transmission line modelling; Calculation of transmission line parameters;

Why...?

Why AC and not DC ?

Why a **sinusoidal alternating voltage ?**

Why 50 Hz (or 60 Hz) ?

http://en.wikipedia.org/wiki/Utility_frequency

The choice of Frequency

50 Hz and 60 Hz

- Between 1885 and 1890 in the U.S.A.:
 - 140, 133 $\frac{1}{3}$, 125, 83 $\frac{1}{3}$, 66 $\frac{2}{3}$, 50, 40, 33 $\frac{1}{3}$, 30, 25, 16 $\frac{2}{3}$ Hz
- Nowadays:
 - 60 Hz in North America, Brazil and Japan (has also 50 Hz!)
 - 50 Hz in most other countries
- Exceptions:
 - 25 Hz Railways (Amtrak)
 - 16 $\frac{2}{3}$ Hz Railways
 - 400 Hz Oil rigs, ships and airplanes

The choice of Frequency

50 Hz and 60 Hz

- A too low frequency, like 10 or 20 Hz causes flicker
- A too high frequency
 - Increases the hysteresis losses:

$$P_{hys} :: f\psi^{1.5-2.5}$$


- Increases the eddy current losses:

$$P_{eddy} :: f^2\psi^2$$

- Increases the cable and line impedance


$$\frac{j\omega L}{j2\pi f L}$$

Sinusoidal Currents And Voltages

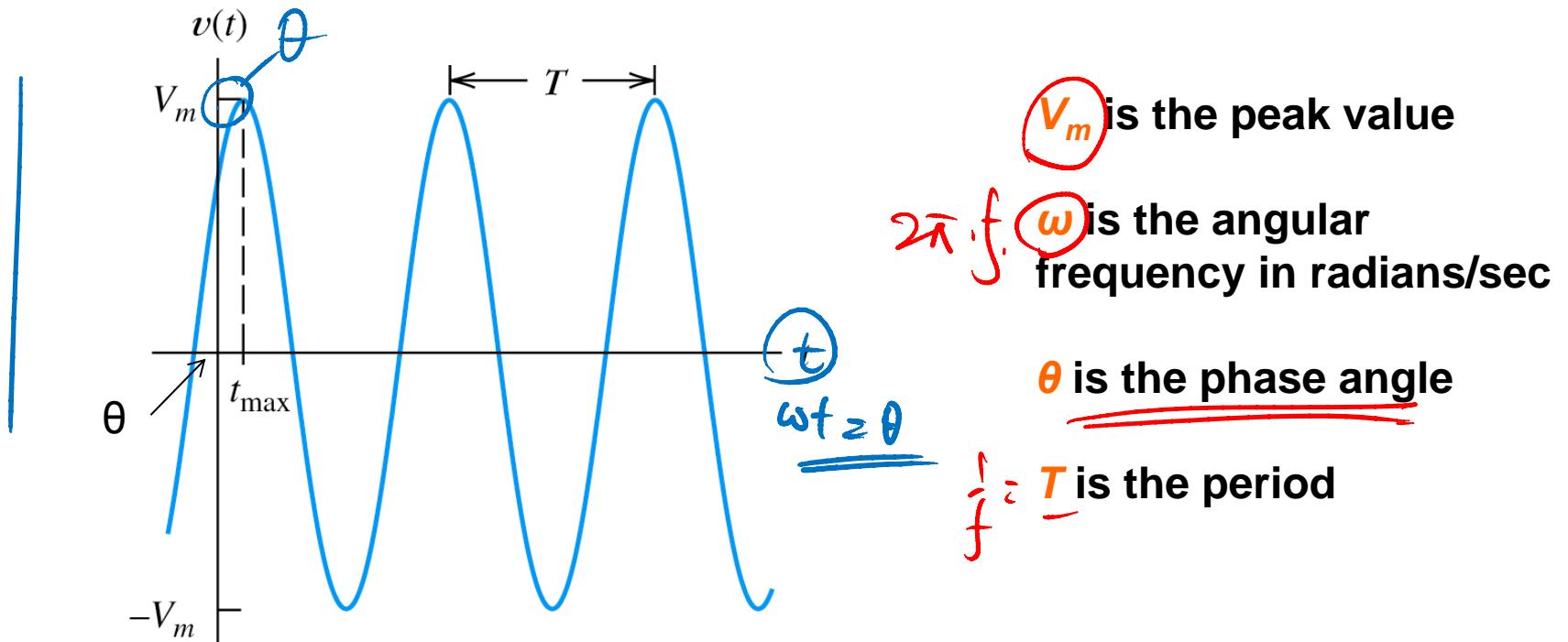

A sinusoidal voltage waveform given by $v(t) = V_m \cos(\omega t + \theta)$.
Note: Assuming that θ is in degrees, we have $t_{\max} = \frac{-\theta}{360} \times T$.
For the waveform shown, θ is -45° .

Root-Mean-Square Values

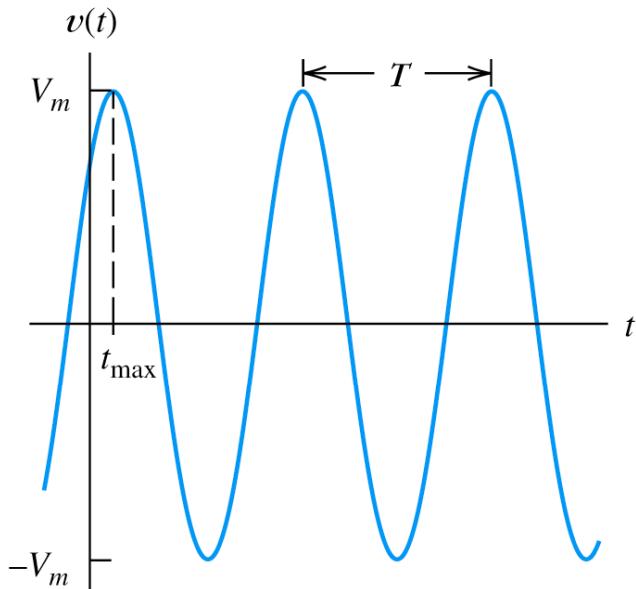

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$


$= \frac{V_m}{\sqrt{2}}$

power calculations.

Figure 5.1 A sinusoidal voltage waveform given by $v(t) = V_m \cos(\omega t + \theta)$.

Note: Assuming that θ is in degrees, we have $t_{\max} = \frac{-\theta}{360} \times T$.

For the waveform shown, θ is -45° .

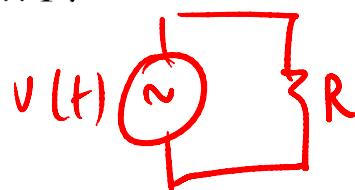

Avg power = $\frac{(V_{\text{rms}})^2}{R}$

$$= \frac{V_{dc}^2}{R}$$

V_{rms}



Phasor Representation of a Sinusoidal waveform

Time function : $v_1(t) = V_m \cos(\omega t + \theta_1)$

$\frac{d}{dt}, \int dt$, Phasor : $\underline{V}_1 = V_1 \angle \theta_1$

Where V_1 is the RMS value of voltage

① Phase ② Impedance

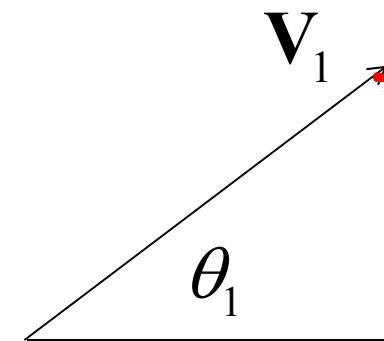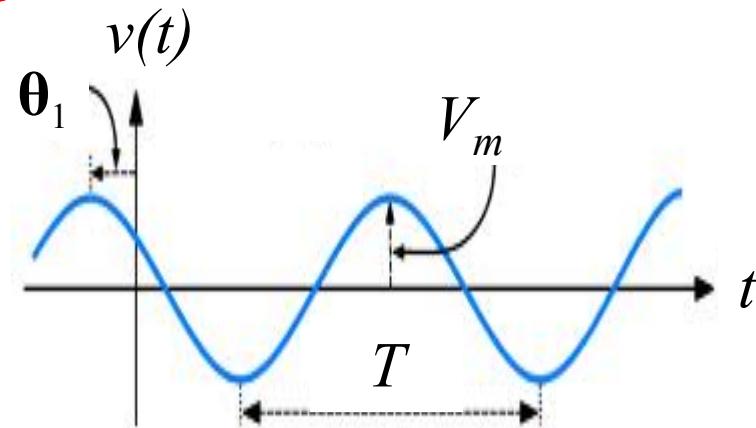

Example - Phasors

$$\begin{aligned}
 & 10 \sin(2\pi t + 45^\circ) + 20 \cos(2\pi t - 60^\circ) + 15 \sin(2\pi t + 90^\circ) \\
 = & \quad \quad \quad " \quad + 20 \sin(2\pi t - 60^\circ + 90^\circ) + \pi
 \end{aligned}$$

Phasors - . (same frequency)

$$\begin{aligned}
 & \frac{10}{r_2} \cdot [45^\circ] + \frac{20}{r_2} \cdot [30^\circ] + \frac{15}{r_2} [90^\circ] = \\
 & = \frac{1}{r_2} \cdot [10 \angle 45^\circ + 20 \angle 30^\circ + 15 \angle 90^\circ] = \left(\frac{40 \cdot 29}{r_2}\right) \angle 52.75^\circ.
 \end{aligned}$$

$$\text{Result} : 40.29 \cdot \sin(2\pi t + 52.75^\circ).$$

R Example
Impedance = Resistance + j Reactance

R $\text{---} \text{H}$

$$\frac{Z}{R}$$

$$Z = \underline{\underline{R + jX}}$$

L $\text{---} \text{m}$

$$j\omega L$$

C $\text{---} \text{H}$


$$-j\frac{1}{\omega C}$$

$$I = \frac{V}{Z} = \angle I = V - Z$$


Current will lag voltage by θ (if θ +ve)
 " " lead " by θ (if θ -ve)

$$X = \omega L$$

$$C = -\frac{1}{\omega C}$$

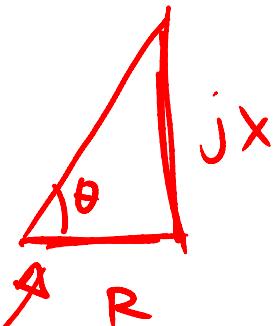


Impedance angle:
 Power factor angle

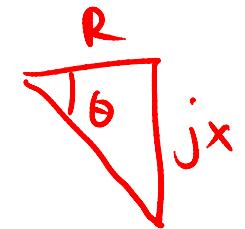

Series Resonance

Series circuit comprising inductor, capacitor and resistance has some interesting behavior.

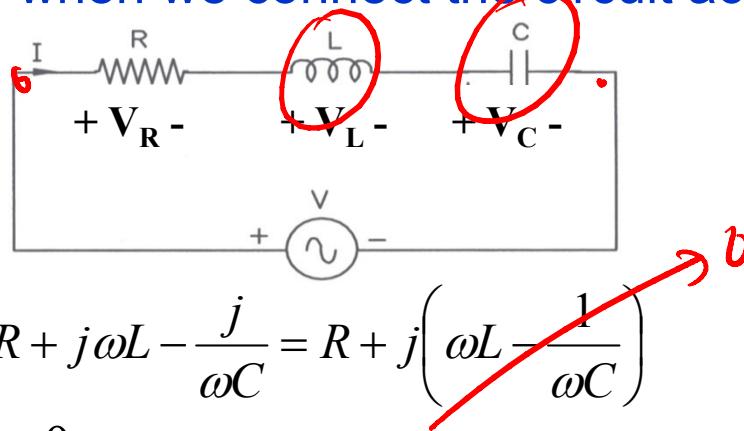This can be analyzed when we connect the circuit across variable frequency source.



Impedance:


$$Z = R + j\omega L - \frac{j}{\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$= |Z| \angle \theta$$

Magnitude and phase angle:

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

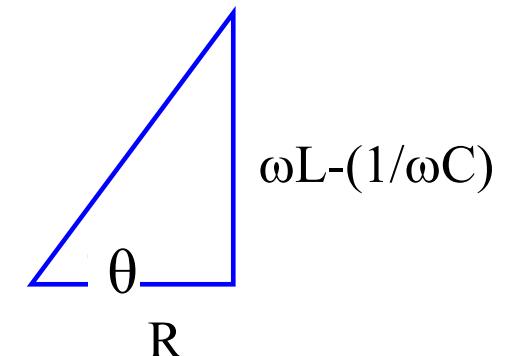
$$\tan \theta = \frac{\omega L - \frac{1}{\omega C}}{R}$$



Current flow in the circuit

$$I = \frac{V}{R + j\omega L - \frac{j}{\omega C}}$$

Parallel RLC Circuits

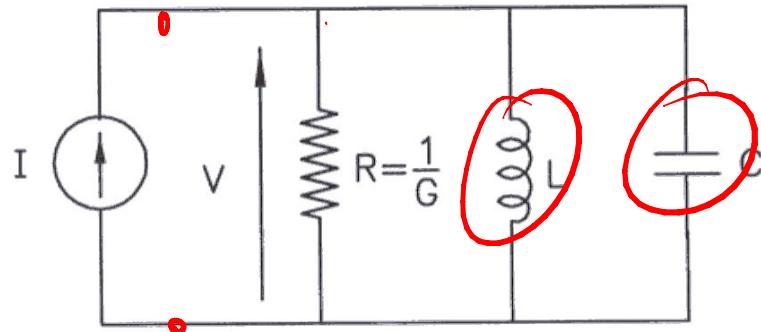

Similar behavior is observed when R, L and C are connected in parallel.


The admittance of the circuit is

$$Y = G + j\omega C - \frac{j}{\omega L}$$

$$|V| = \frac{|I|}{|Y|} = \frac{|I|}{\sqrt{G^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}}$$


$$\omega_0 = \frac{1}{\sqrt{L \cdot C}}$$

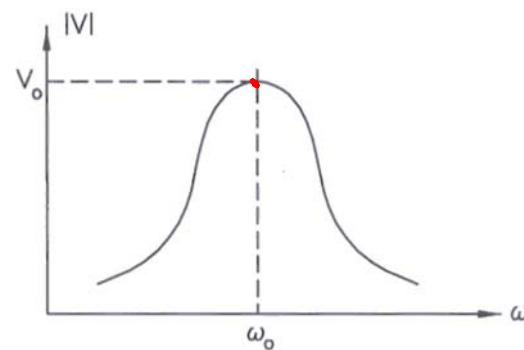At resonance: $\omega_0 L = \frac{1}{\omega_0 C}$



- What is power in AC circuits for R, L, C?
- Power in Generic AC Load \rightarrow $R+jX$
- Real, Reactive and Apparent Power
- Power Triangle (Complex Power)
- Power Factor / Power Factor Compensation

Power in R, L, C

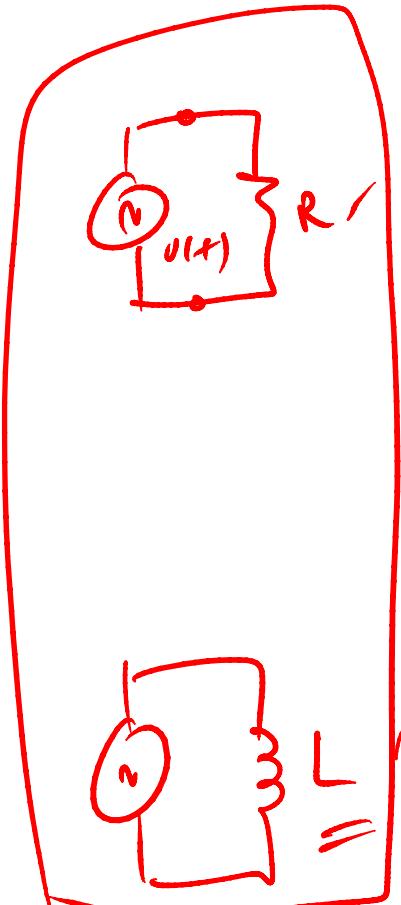

$$V(t) = V_m \cdot \sin(\omega t)$$

$$i(t) = \frac{V_m}{R} \cdot \sin \omega t$$

$$P(t) = \frac{V_m^2}{R} \cdot \underline{\sin^2 \omega t} = \frac{V_m^2}{R} \cdot [1 - \cos(2\omega t)]$$

\uparrow Instantaneous power.

\rightarrow twice

Frequency ω

oscillation ω

$$= \frac{1}{2} \cdot \frac{V_m^2}{\omega L} \cdot \sin(2\omega t)$$


$$P(t) = \frac{V_m^2}{\omega L} \cdot \underline{\sin \omega t \cdot \cos \omega t}$$

$$= \frac{V_m^2}{2} \cdot \omega C \cdot \sin \omega t \cdot \cos \omega t$$

$$= \frac{V_m^2}{2} \cdot \omega C \cdot \underline{\sin(2\omega t)}$$



Power in Generic AC Load

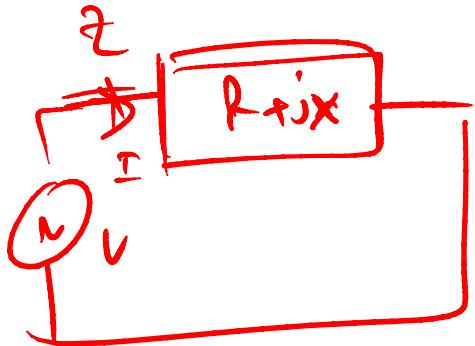


$$I = \frac{V}{Z}$$

$$\text{power} = I^2 \cdot Z = I^2 \cdot (R + jX)$$

$$= \underbrace{I^2 R}_{P} + j \underbrace{I^2 X}_{Q}$$

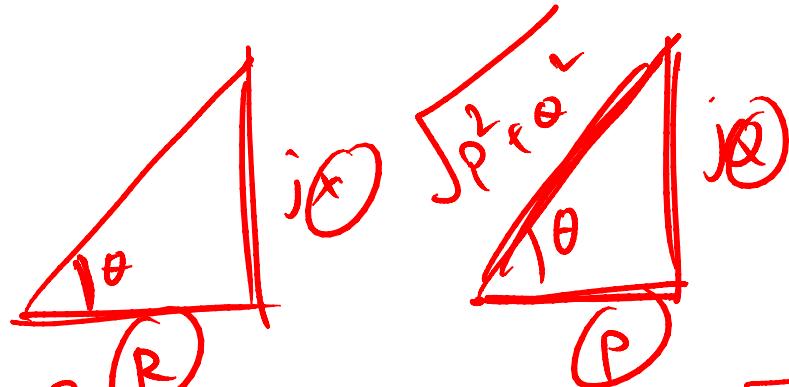P Q
Real power Reactive
(Average pr) power.



$$\cos\left[\tan^{-1}\frac{X}{R}\right] \quad \text{Apparent power } |S| = \sqrt{P^2 + Q^2} \quad \left. \begin{array}{l} P = |S| \cdot \cos \theta \\ Q = |S| \cdot \sin \theta \end{array} \right\}$$

$$\cos\left(\tan^{-1}\frac{Q}{P}\right) - \quad |S| = V_{rms} I_{rms} \quad \left. \begin{array}{l} P = |S| \cdot \cos \theta \\ Q = |S| \cdot \sin \theta \end{array} \right\}$$

$\cos \theta = \text{Power factor}$


Complex Power

We can show that,

$$\text{Complex power } S = V \cdot I^*$$

$$\text{Complex power, } S = V_{\text{rms}} I_{\text{rms}} \cos \theta + j V_{\text{rms}} I_{\text{rms}} \sin \theta$$

$$\text{Or, } S = |S| \cos \theta + j |S| \sin \theta = P + jQ$$

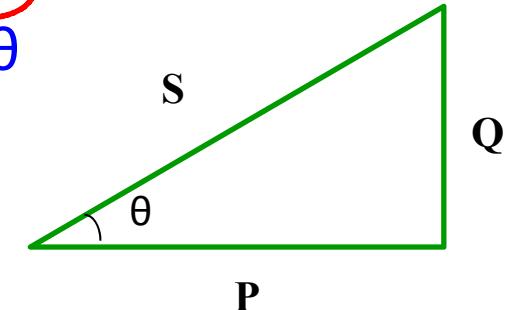


S	Complex power	VA	$S = S \angle \theta = P + jQ = VI^* = \\ = V I \angle \theta = V I (\cos \theta + j \sin \theta)$
$ S $	Apparent power	VA	$ S = V I = \sqrt{P^2 + Q^2}$
P	Active power Average power, Real power	W	$P = \text{Re}(S) = S \cos(\theta) = V I \cos(\theta)$
Q	Reactive power	var	$Q = \text{Im}(S) = S \sin(\theta) = V I \sin(\theta)$



Power Factor of an a.c. circuit

Now, we will define Power Factor of an a.c. circuit as the ratio of real power to the apparent power.


$$\text{Power Factor} = \frac{P}{|S|} = \frac{P}{|V| |I|} = \cos \theta$$

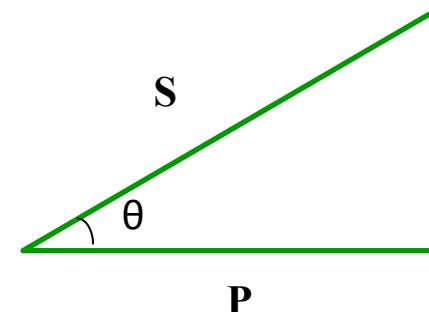

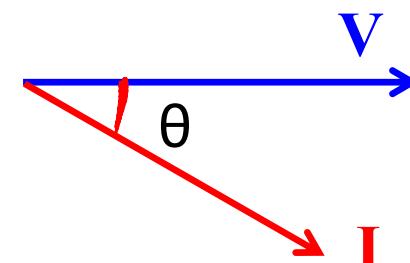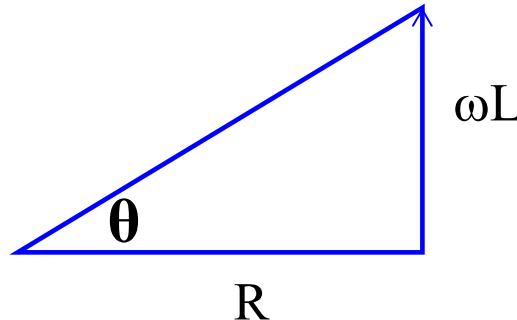Power factor angle (θ) is the same in power triangle, impedance triangle, and the angle between voltage and current.



Power Factor

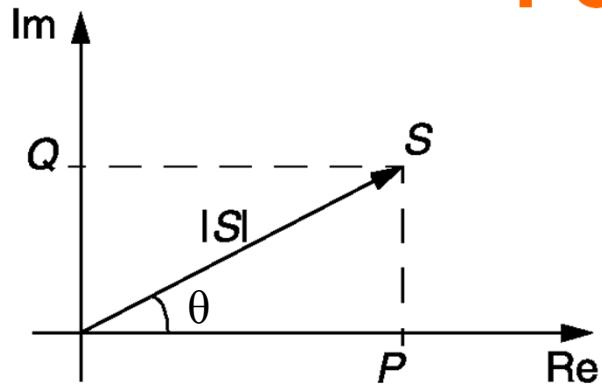

$$P = |S| \cos(\theta) = |V| |I| \cos(\theta)$$

$$\cos(\theta) = \frac{P}{|S|} = \frac{P}{\sqrt{P^2 + Q^2}}$$


$$\cos(\theta) = \cos\left(\tan^{-1}\left(\frac{Q}{P}\right)\right)$$
✓

Example – Different types of power

① Load draws 10 kW at 230V P.f. \neq 0.8 lag

② 15 kVA at 230V P.f. \neq 0.9 lead.

①

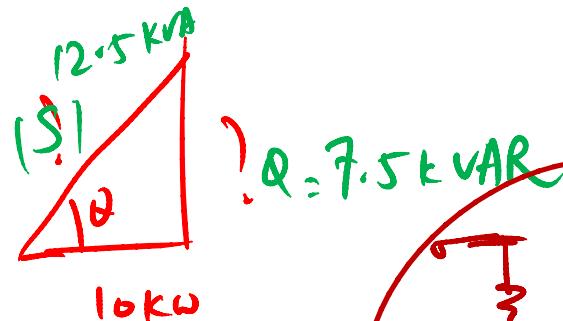

$$\theta = \cos^{-1}(0.8) \\ = 36.87^\circ$$

$$|S| = \frac{P}{\text{P.f.}} = 12.5$$

$$Q = |S| \cdot \sin(36.87^\circ) = 7.5 \text{ kVAR}$$

$R+jX$



②

$R+jX$

P ? = 13.5 kW

Q ? = 6.54 kVAR
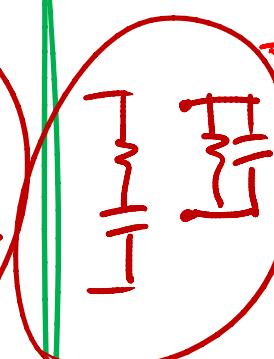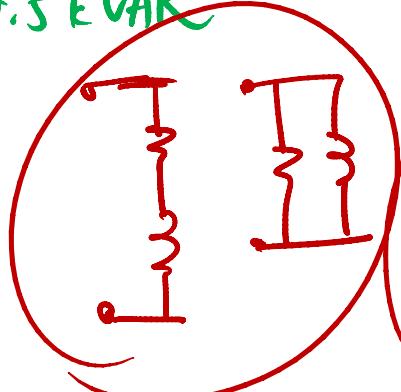
$$\theta' = -\cos^{-1}(0.9) \\ = -25.84^\circ$$




Power Factor

$$P = |S| \cos(\theta) = |V||I| \cos(\theta)$$

$$0 \leq \theta \leq 90^\circ$$

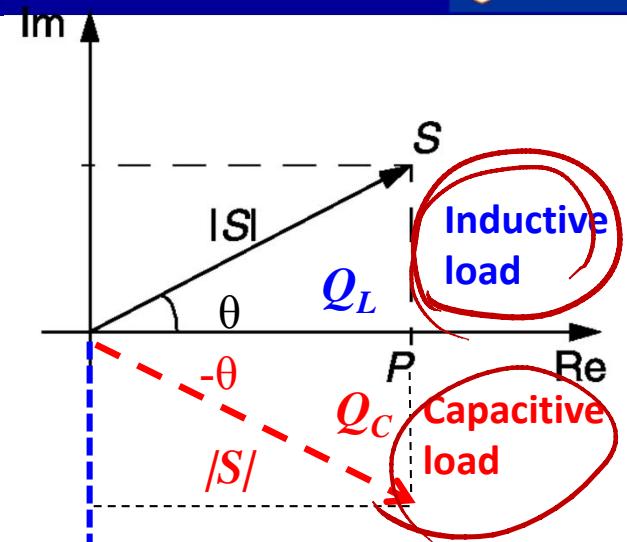Hence, power factor lies between: $0 \leq \text{p.f.} \leq 1$



Since $\cos (+\theta) = \cos (-\theta)$, we identify the power factor as leading or lagging.

For inductive load: Current lags behind voltage (Reactive power +ve)


Hence, power factor is lagging p.f.

For capacitive load: Current leads the voltage (Reactive power -ve)

Hence, power factor is leading p.f.





For example: If the load is $10\angle 25^\circ$ the power factor is 0.906 lagging
If the load is $20\angle -30^\circ$ the power factor is 0.87 leading

Power Factor Correction

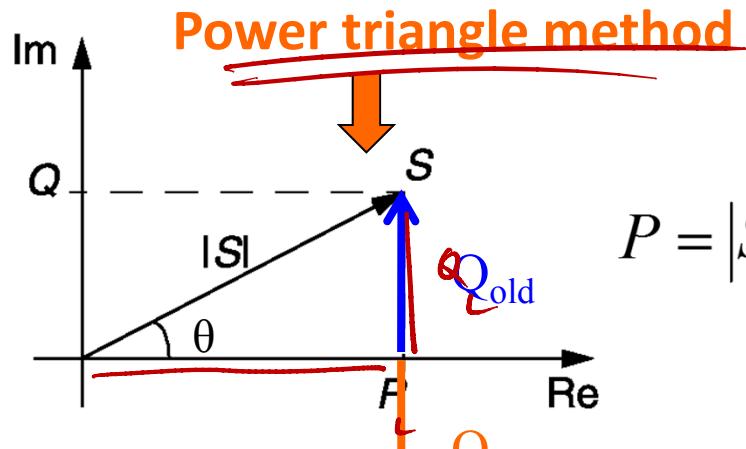

$$P = |S| \cos(\theta) = |V||I| \cos(\theta)$$

$$|I| = P / |V| \cos(\theta)$$

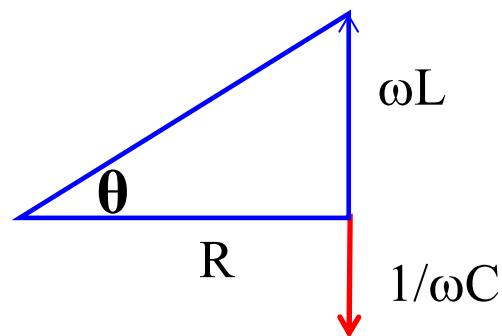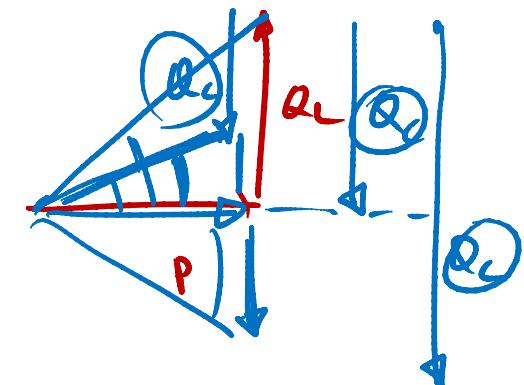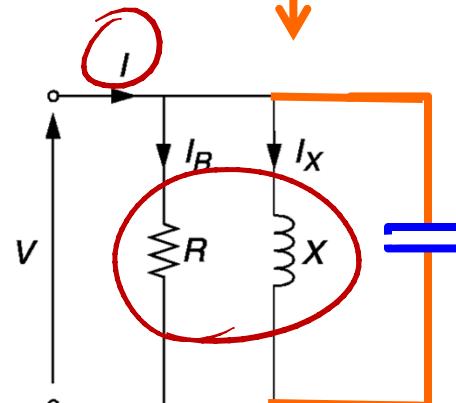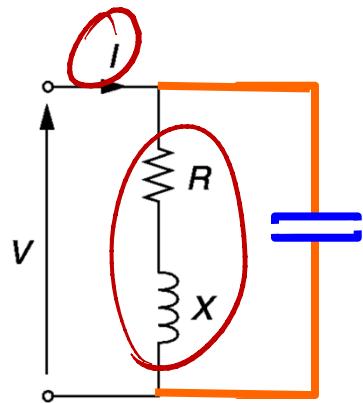


Load is $\frac{20+j10}{10\text{kW}}$
 Load draws 10kW , at 0.8 lagging


Example

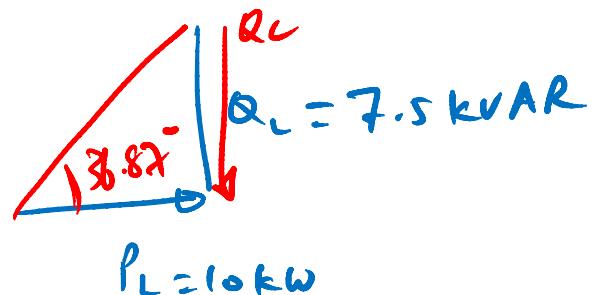0.8 to 0.9

Pf. from a $230\text{V}/50\text{Hz}$ source.



$$P_L + jQ_L + jQ_C$$

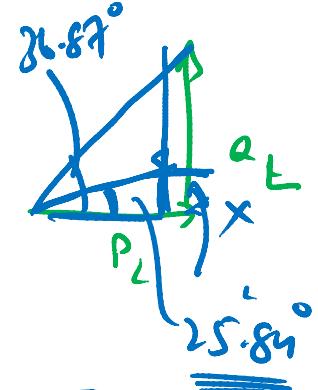


① Unity P.f.

$$Q_L + Q_C = 0$$

$$Q_C = -Q_L = -7.5 \text{ kVAR}$$


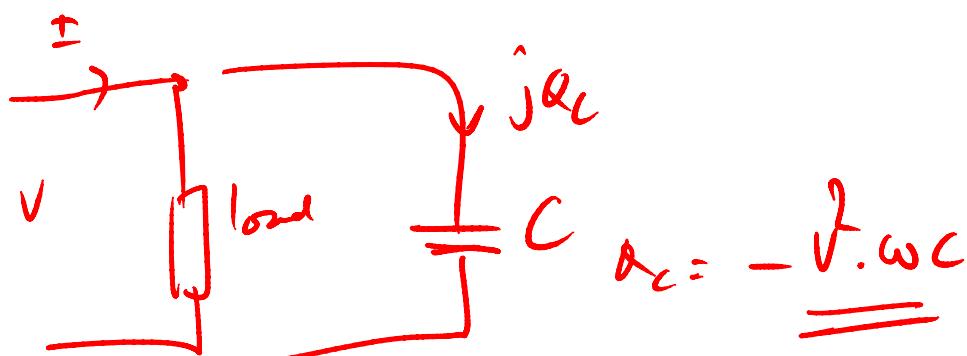
$$C = \frac{-Q_C}{V \cdot 2\pi \cdot 50} \\ = \frac{+7.5 \times 10^3}{230^2 \times 2\pi \times 50} \text{ F}$$



$$Q_C + Q_L = 4.84$$

$$Q_C = 4.84 - 7.5 = -2.66 \text{ kVAR}$$
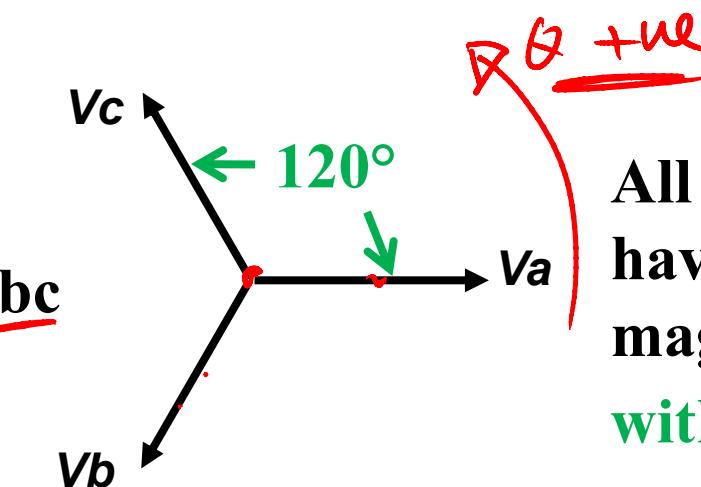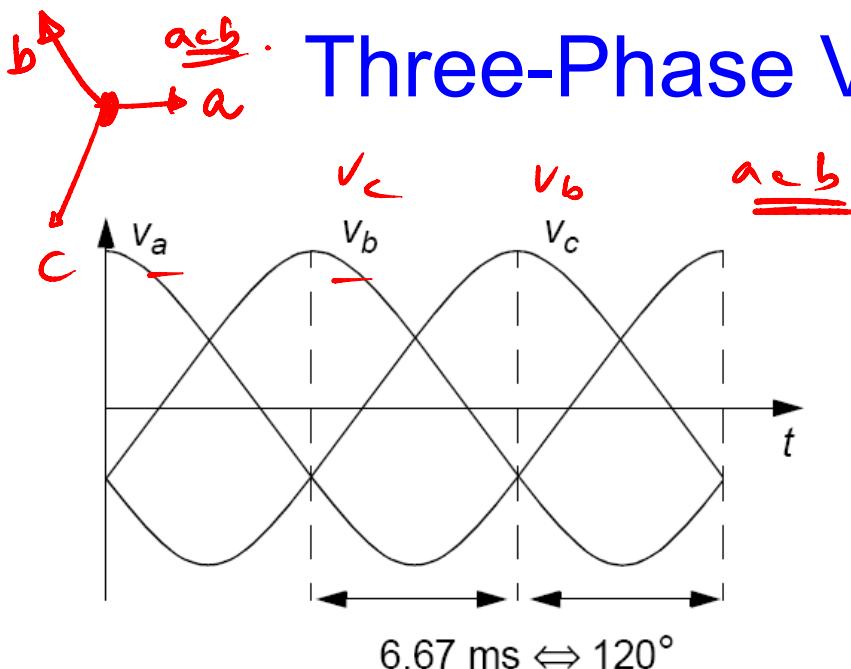
$$\left. \begin{aligned} X &= P_L \cdot \tan 25.84^\circ \\ &= 4.84 \text{ kVAR} \end{aligned} \right\}$$



Phase sequence: abc (positive)

$$v_a = \sqrt{2}|V| \cos(\omega t)$$

$$v_b = \sqrt{2}|V| \cos\left(\omega t - \frac{2\pi}{3}\right)$$

$$v_c = \sqrt{2}|V| \cos\left(\omega t - \frac{4\pi}{3}\right)$$

All three voltage sources have the same voltage magnitude, with 120 degrees apart.

Line-To-Line Voltage


 \underline{abc}
 $\underline{ab}, \underline{bc}, \underline{ca} \parallel \underline{ba}, \underline{cb}, \underline{ac}$
 $V_{ab} > V_{an} - V_{bn}$

Voltage is given as line-to-line voltage by convention.


KVL:

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3}V_{an} \angle 30^\circ$$


$$|V_{\text{Line-Line}}| = \sqrt{3}|V_{\text{Line-neutral}}|$$

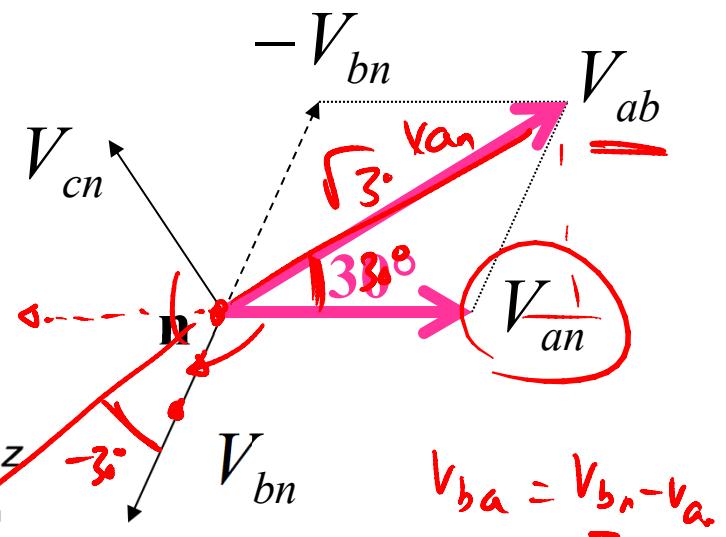

$$V_{ba} = V_{bn} - V_a$$

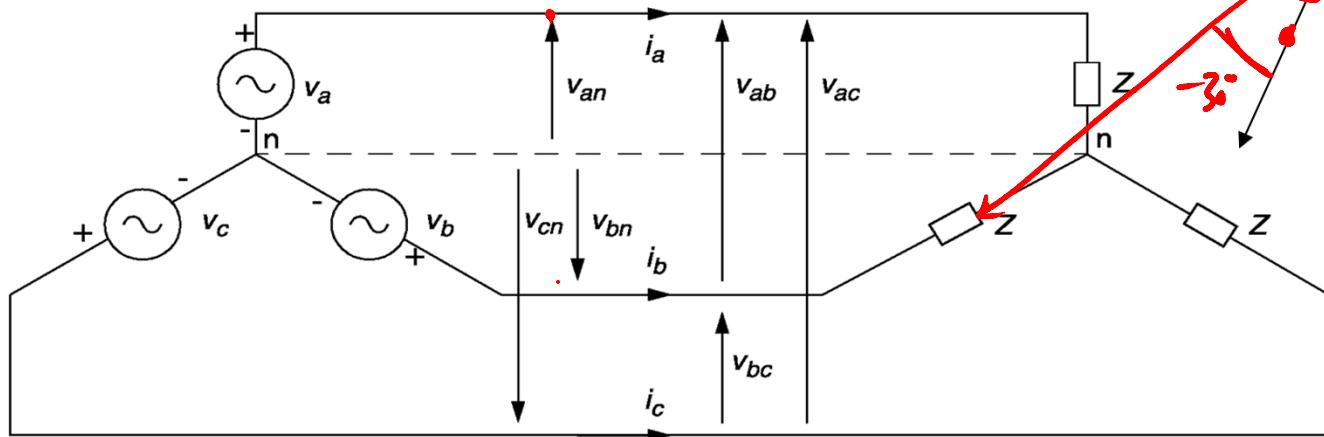

Delta/Wye Connected 3-Phase Load

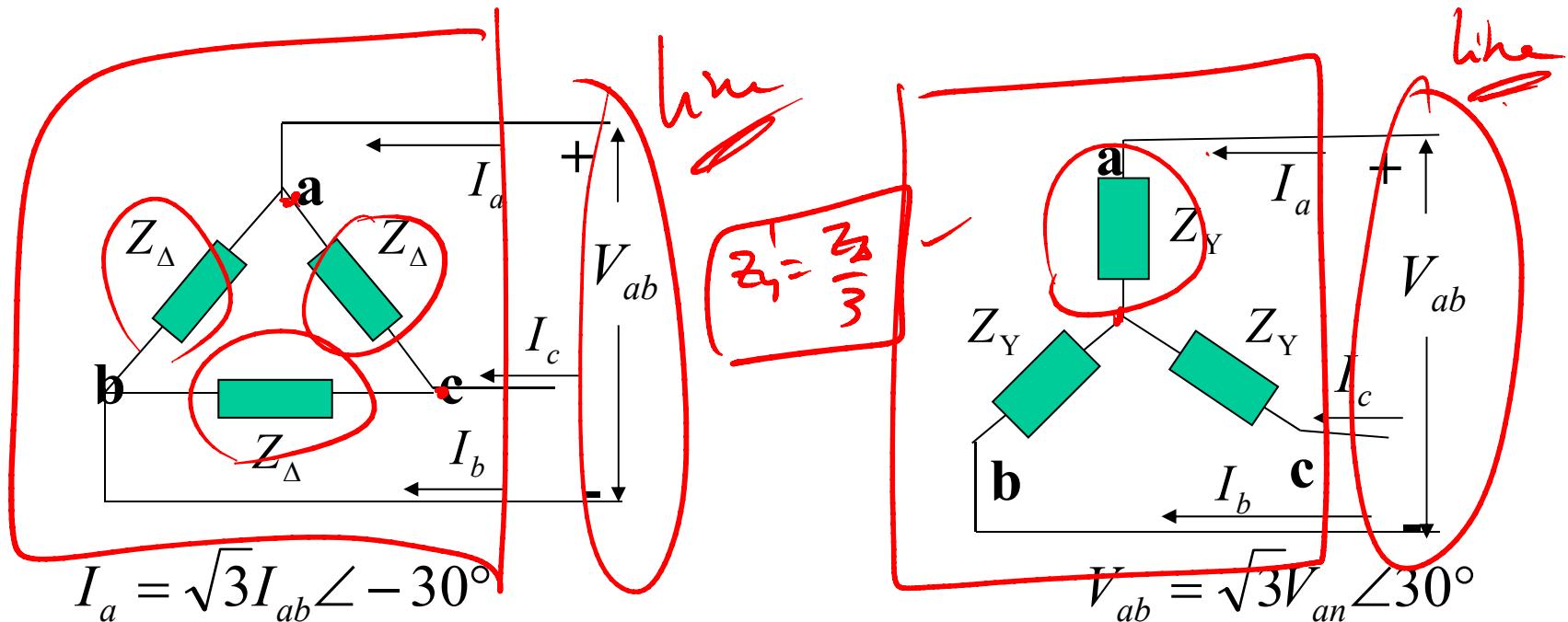

$$|S_{3\Phi}| = 3|V_{ab} I_{ab}^*| = \sqrt{3}|V_{ab} \| I_a|$$

$$|S_{3\Phi}| = 3|V_{an} I_a^*| = \sqrt{3}|V_{ab} \| I_a|$$

$|S_{3\Phi}| = \sqrt{3} |V_{\text{Line-To-Line}} \| I_{\text{Line}}|$

($\sqrt{3} \cdot V_{\text{phase}}$)



$\sqrt{3}, V \sim I$

~~$S = 3 \cdot V \cdot I$~~

Per-Phase Analysis: Assumption

It must be
balanced three-
phase circuit.

$$I_n = I_a + I_b + I_c = 0$$

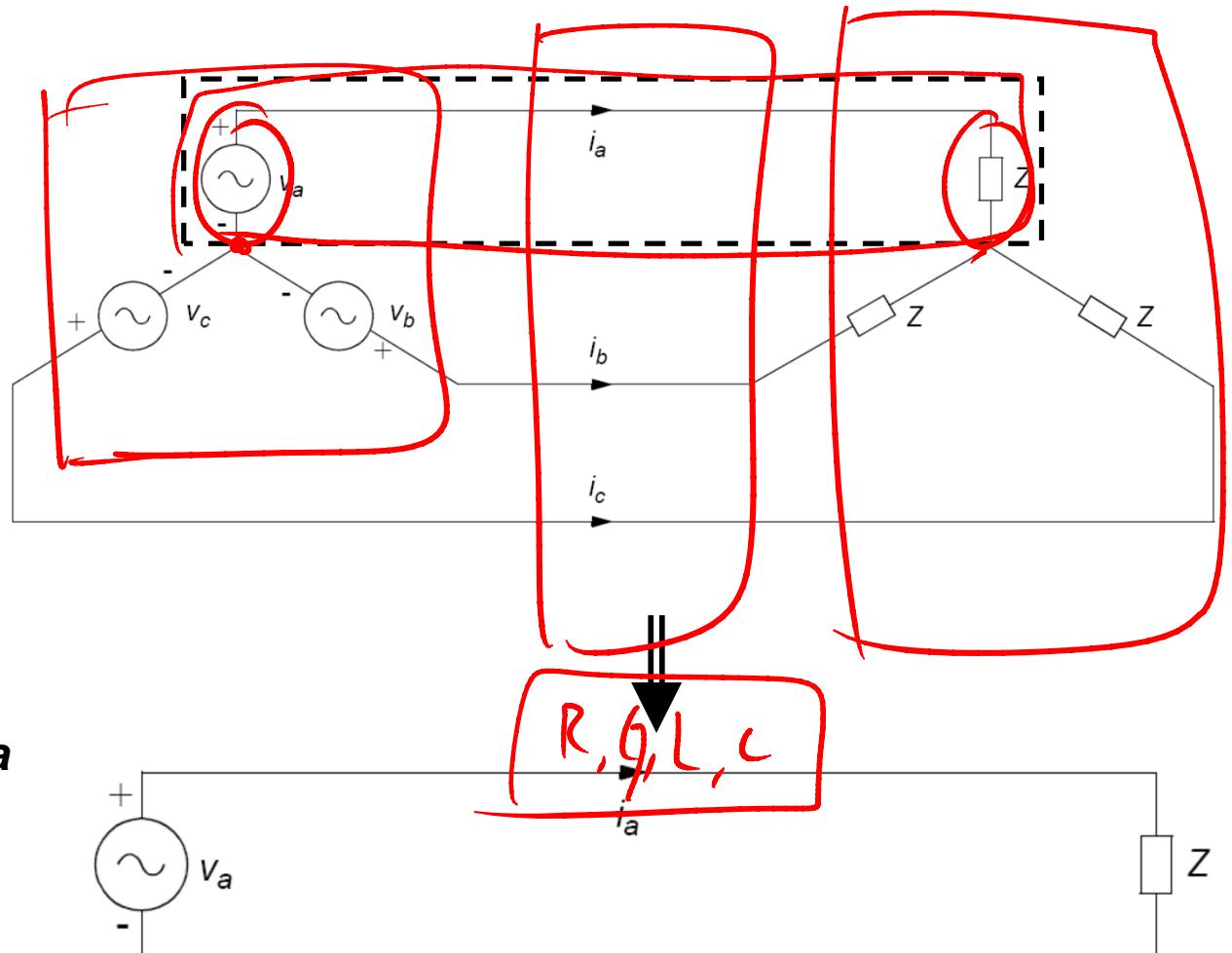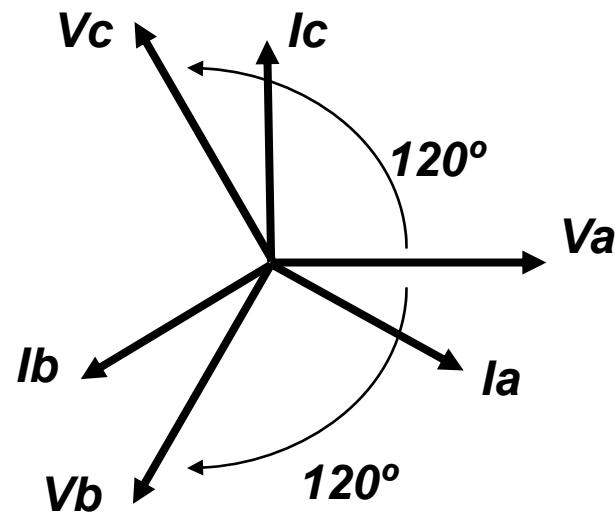

Steps of Per Phase Analysis

Make sure that the three-phase system is balanced.


- The three-phase sources need to have the same magnitude with 120 degree phase difference.
- The three-phase impedances must be of the same value (both phase and magnitude).

Convert all Delta-connected sources/loads to Wye-connected sources/loads.

Per phase analysis reduce three-phase circuit to single-phase circuit. We can apply the same concept used in single-phase.


$$V_{LL} \rightarrow V_{LN} = \frac{V_{LL}}{\sqrt{3}}$$
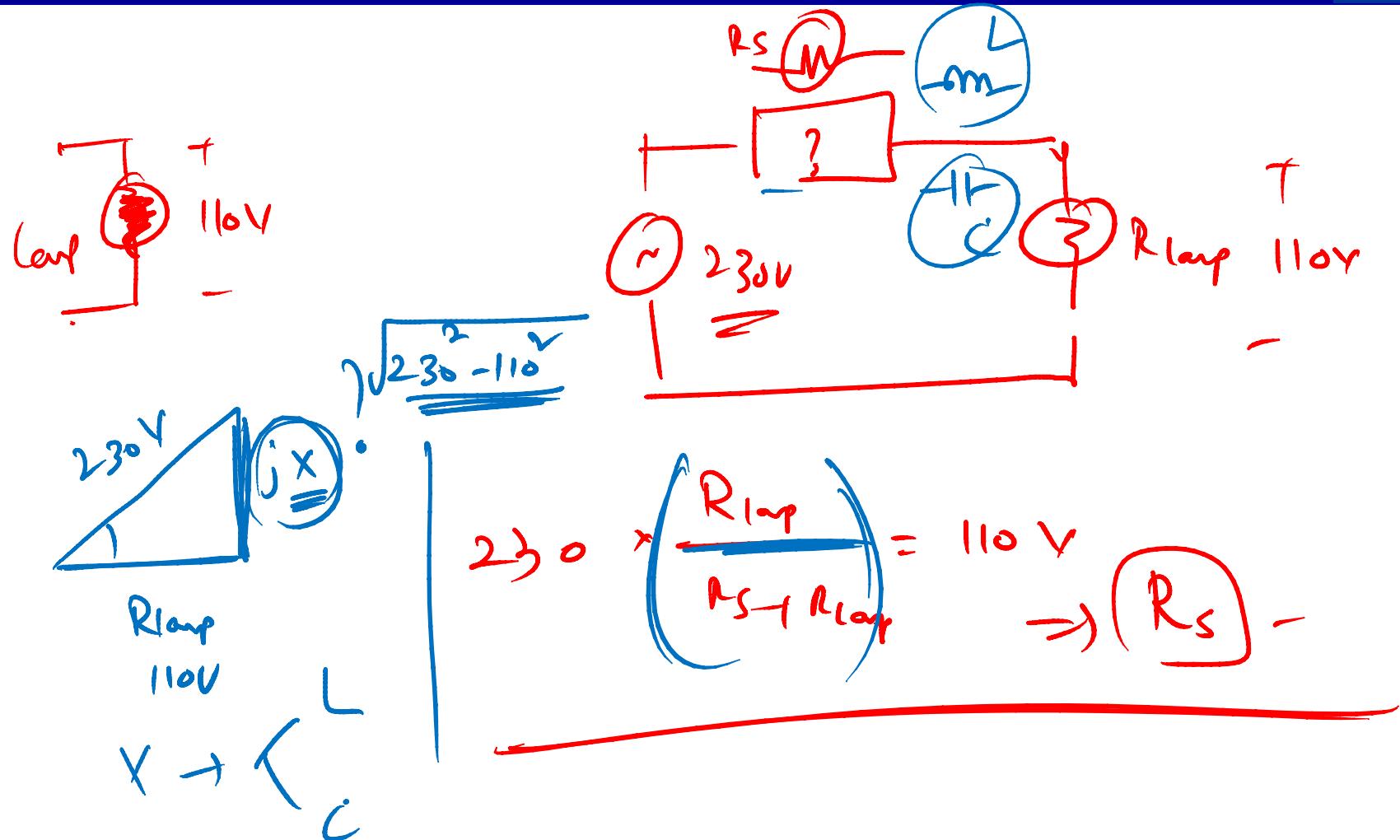
$$Z_\Delta \rightarrow \overline{Z_Y} = \frac{Z_\Delta}{3}$$



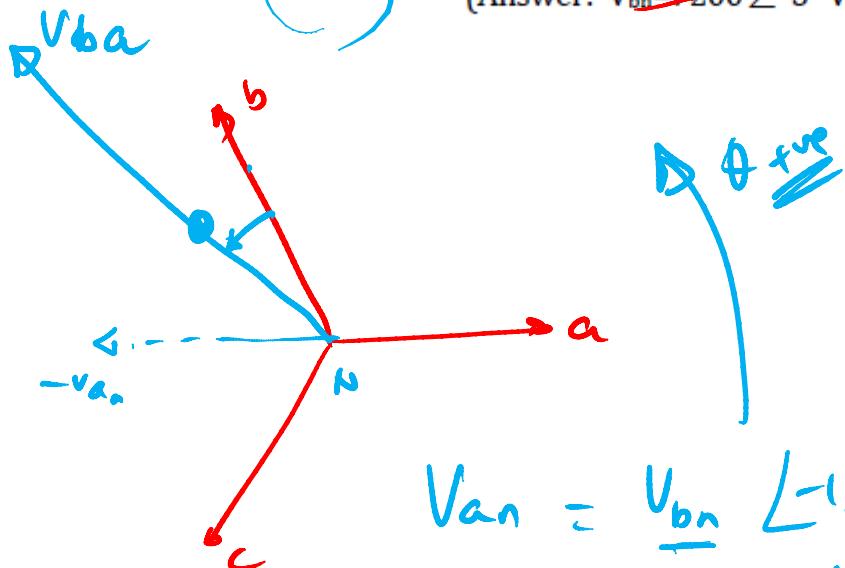2. What are the phase voltages for a balanced three-phase Y load, if $V_{ba} = 12470 \angle -35^\circ$ V? The phase sequence is positive sequence i.e. ~~abc~~ ~~acb~~ ~~bca~~

(Answer: $V_{bn} = 7200 \angle -5^\circ$ V, $V_{an} = 7200 \angle 115^\circ$ V, and $V_{cn} = 7200 \angle -125^\circ$ V)



$$Van = \underline{V_{bn}} \angle -12^\circ$$

$$V_{cn} = \underline{V_{bn}} \angle +240^\circ$$

$$\underline{V_{ba}} = \underline{V_{bn}} - \underline{V_{an}}$$

$$= \underline{\sqrt{3}V_{bn}} \angle +30^\circ$$

$$V_{bn} = \frac{V_{ba}}{\sqrt{3}} \angle -30^\circ$$


$$= \frac{12470}{\sqrt{3}} \angle -35 - 30^\circ$$

$$= \underline{12470} \angle -65^\circ$$

$$V_{a'n} \checkmark$$

$$\underline{V_{a'n}} = 100 \angle 0^\circ$$

$$V_{ab} ?$$

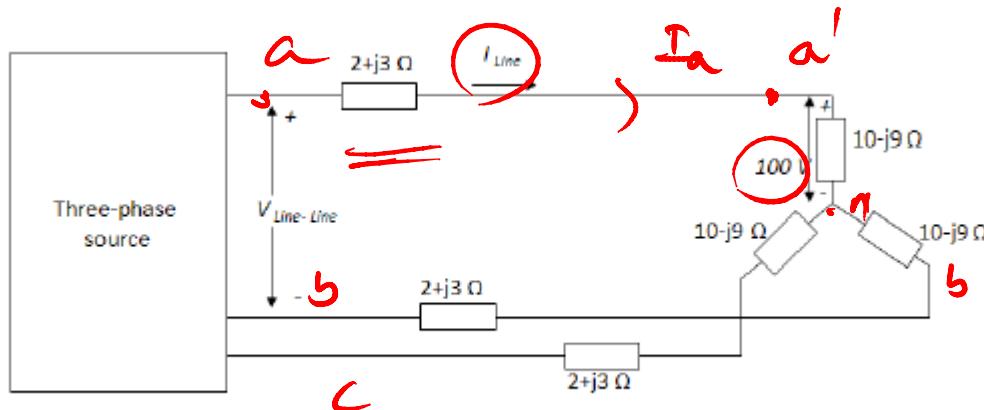

$$I_a = \frac{100 \angle 0^\circ}{10 - j9} = 7.43 \angle 41.98^\circ \text{ A}$$



$$V_{an} = V_{a'n} + I_a \times (2 - j3) = 99.72 \angle 15.41^\circ$$

$$V_{ab} = \sqrt{3} \cdot V_{an} \angle 30^\circ \quad . \quad V_{LL} = \sqrt{3} \cdot V_{an}$$

\equiv

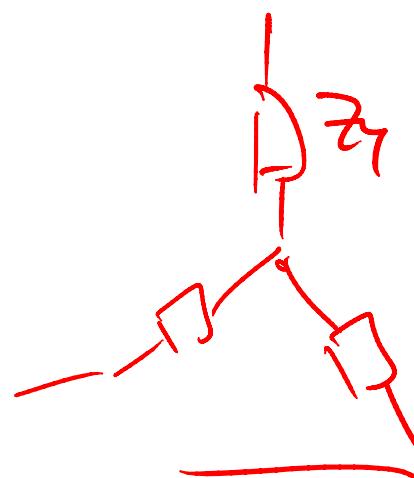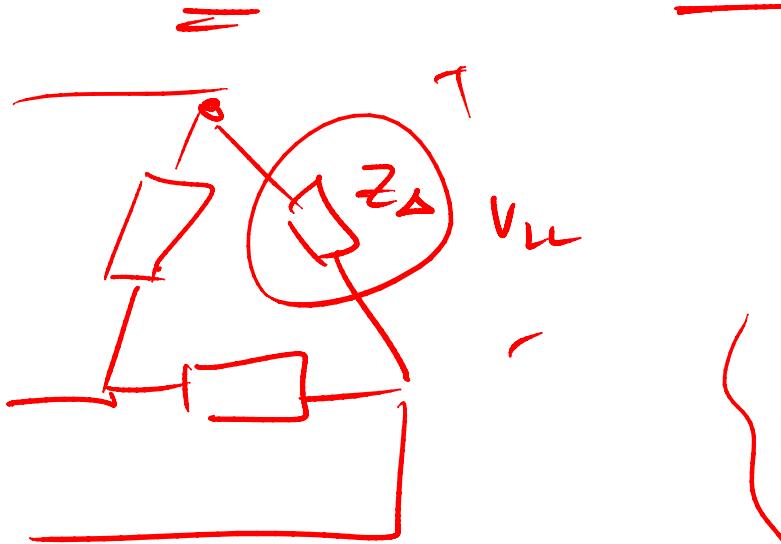8. In a 208-V three-phase circuit a balanced Δ load absorbs 2 kW at a 0.8 leading power factor. Find Z_Δ .

(Answer: $51.9 \angle -36.87^\circ \Omega$)



$$V = 208 \text{ V}$$

$$P = \frac{2000}{\sqrt{3}}. \quad \text{P. f.} = 0.8 \quad \text{leading}$$

$$P = \frac{V^2}{|Z_\Delta|} \cdot (\text{P. f.})$$

$$Z_\Delta = \frac{V^2}{P} \cdot \text{P-f.}$$

$$Z_Y = \frac{V^2}{P} \cdot \text{P.f.}$$

$$= \frac{(208/\sqrt{3})^2}{2000/3} \times 0.8$$