

EE2022

Electrical Energy Systems

Lecture 5: AC Power Problem Solving



Instantaneous power:

$$p(t) = V_m I_m \cos^2 \omega t = \frac{1}{2} [1 + \cos 2\omega t] \times V_m I_m$$

Average of this function is equal to half of the peak amplitude :



$$P_{R,avg} = \frac{V_m I_m}{2}$$

$$P_{R,avg} = \frac{V_m I_m}{\sqrt{2} \sqrt{2}} = \underline{V_{rms} I_{rms}}$$

$$V_{rms} = R I_{rms}$$

$$P_R = \frac{V_{rms} \cdot I_{rms}}{(avg)} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

Average Power in a Resistor

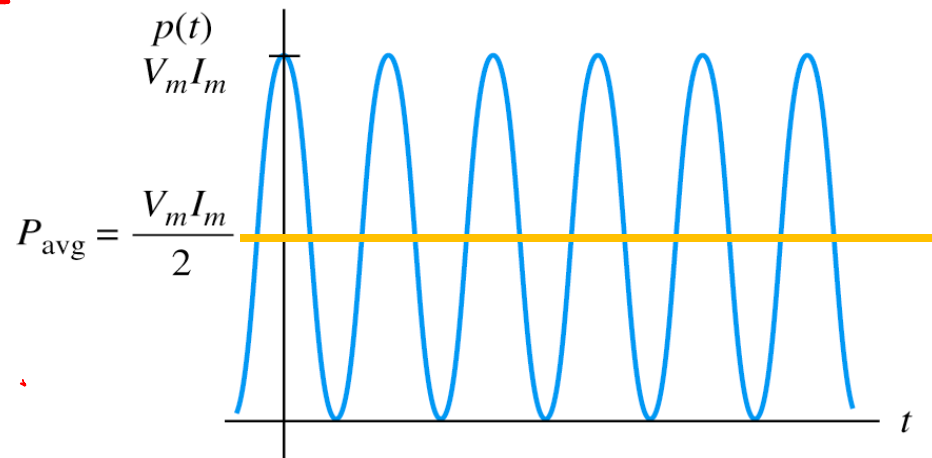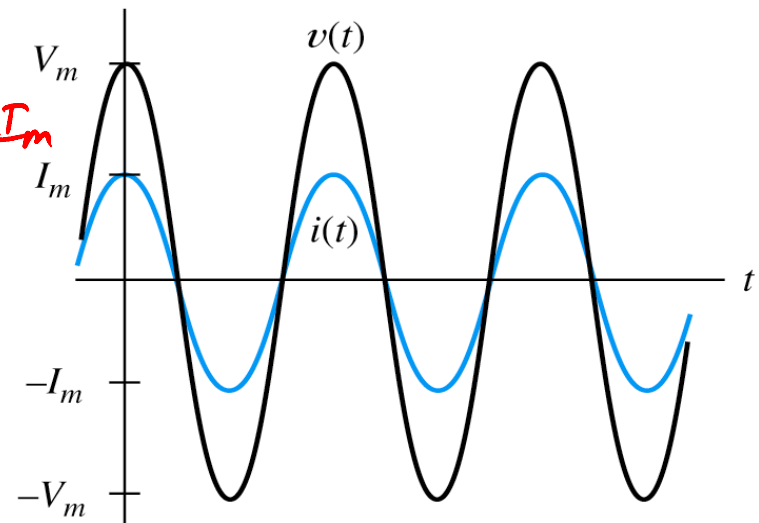



Current, voltage, and power versus time for a purely resistive load

Average Power in an Inductor

$$p(t) = \underline{V_{rms} I_{rms} \sin(2\omega t)}$$

Average power, $P_{avg} = 0$
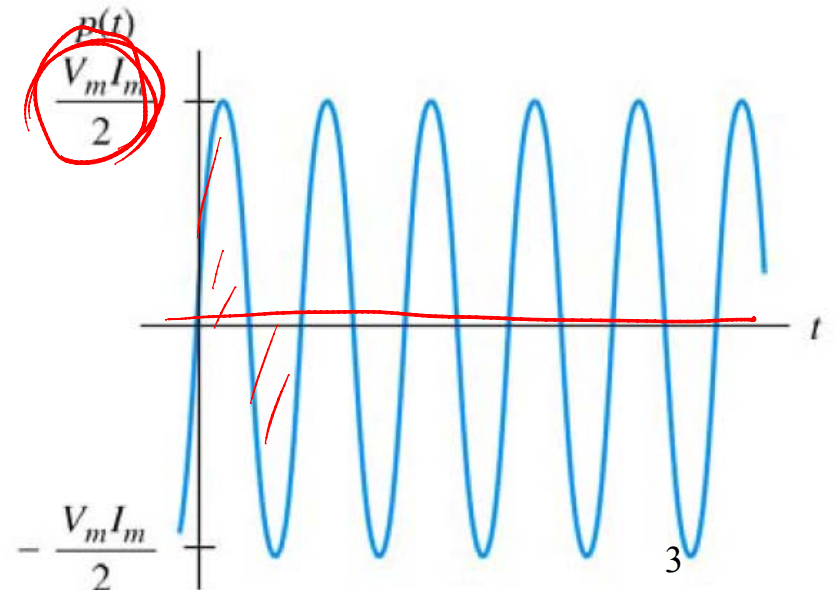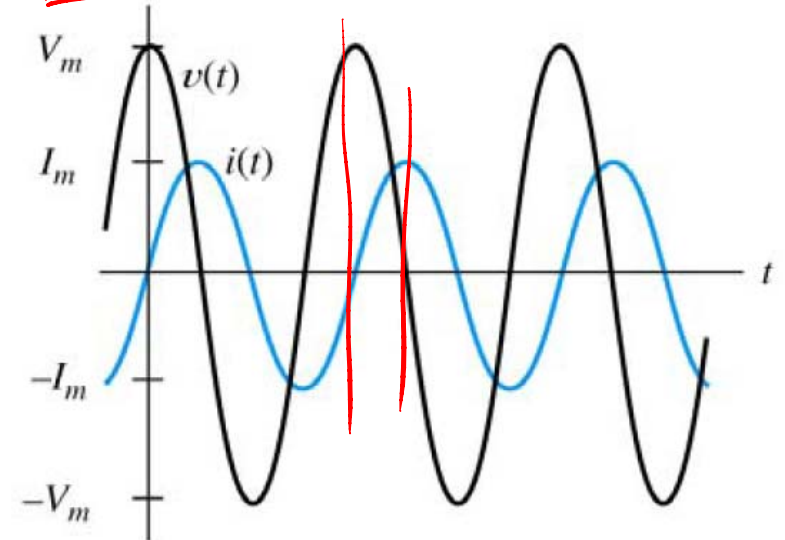
$$\begin{aligned}
 P_L(t) &= \underline{V_{rms}} \cdot \underline{I_{rms}} \cdot \sin 2\omega t \\
 &= \frac{V_{rms}^2}{\omega L} \cdot \sin 2\omega t \\
 &= I_{rms}^2 \times \omega L \sin 2\omega t.
 \end{aligned}$$



Average Power in a Capacitor

$$p(t) = -V_{rms} I_{rms} \sin(2\omega t)$$



Average power, $P_{avg} = 0$

$$\begin{aligned}
 p(t) &= - \frac{V_{rms}^2}{Y_{\omega C}} \sin 2\omega t \\
 &= - I_{rms}^2 \left(\frac{1}{\omega C} \right) \sin 2\omega t
 \end{aligned}$$

$R \rightarrow P_{avg} \quad I_{rms}^2 \cdot R \rightarrow \textcircled{P}$


$\underline{L} \rightarrow P_{peak} \quad I_{rms}^2 \cdot \omega L \quad \left. \vphantom{I_{rms}^2 \cdot \omega L} \right\} Q$

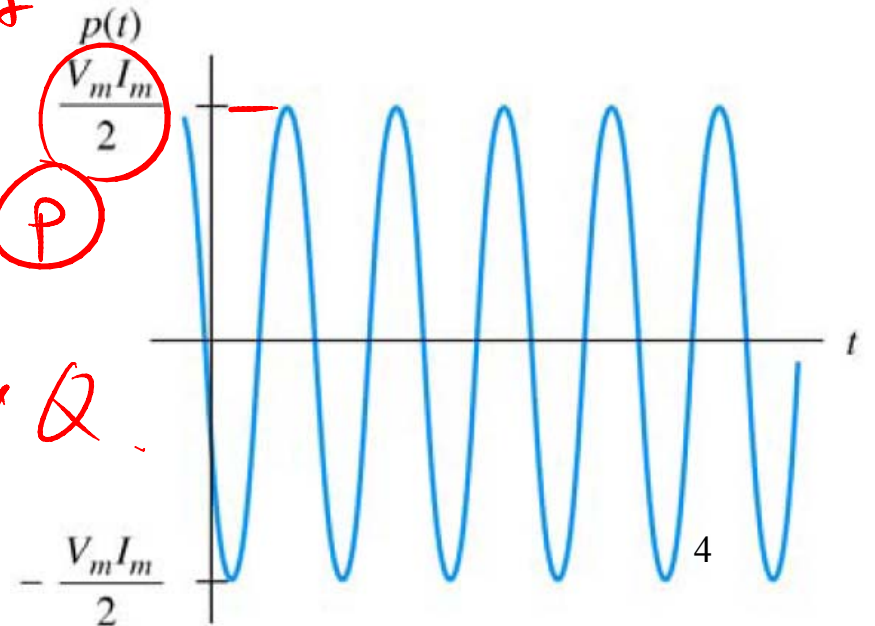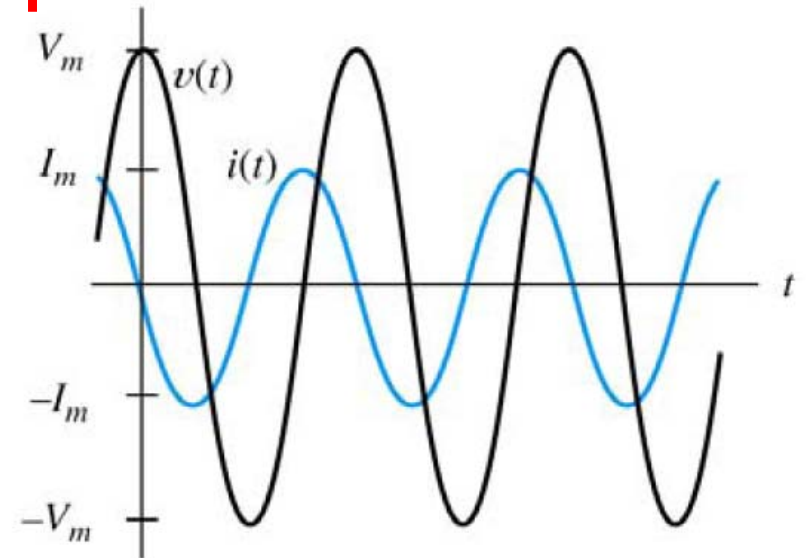$\underline{C} \rightarrow P_{peak} \quad I_{rms}^2 \cdot \frac{1}{\omega C} \quad \left. \vphantom{I_{rms}^2 \cdot \frac{1}{\omega C}} \right\} Q$



Real, Reactive and Apparent Power



Generic Load

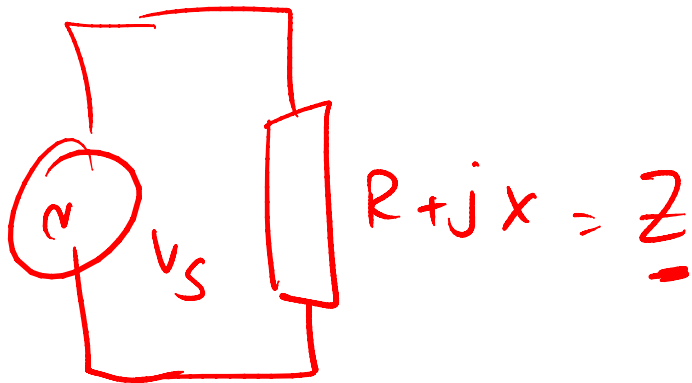

$$P = V_{rms} \cdot I_{rms} \cdot \cos \theta$$

$$= |S| \cdot \cos \theta$$

↑ Apparent power.

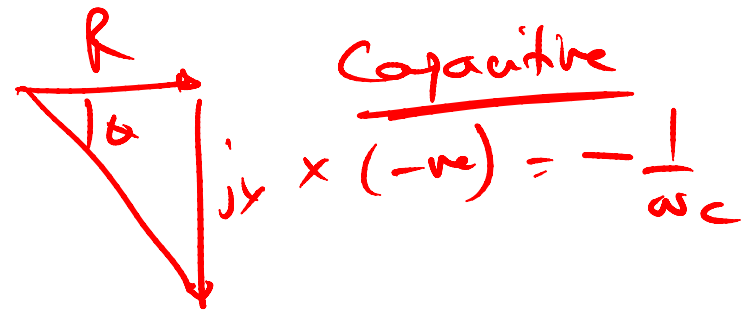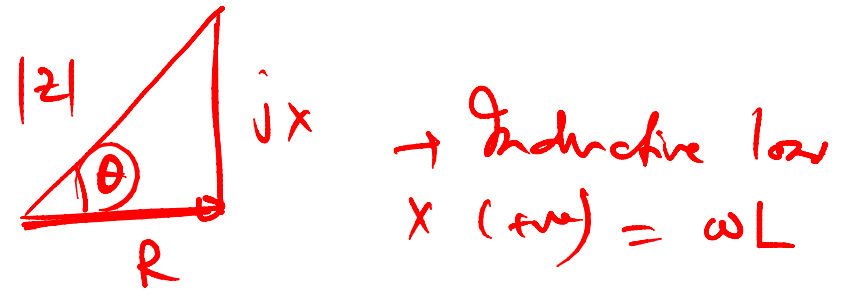

Apparent Power

We express power in d.c. and a.c. circuits as follows:



$$P_{dc} = V_{dc} I_{dc} \text{ Watts}$$

$$P_{ac} = V_{rms} I_{rms} \cos \theta \text{ Watts}$$


Apparent Power $|S| = V_{rms} I_{rms}$ VA (volt-amperes)

So, the power in a.c. circuit may also be expressed in terms of apparent power as follows:

$$\underline{P = |S| \cos \theta}$$

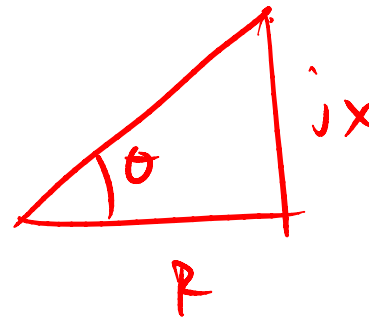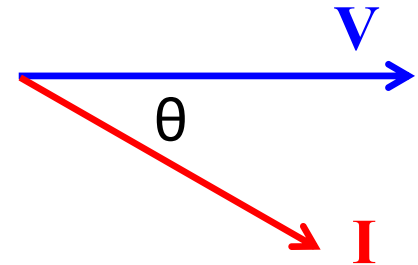


Impedance
triangle

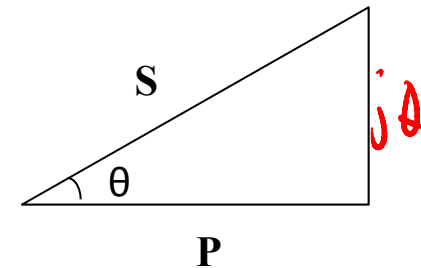

power triangle

Power Triangle

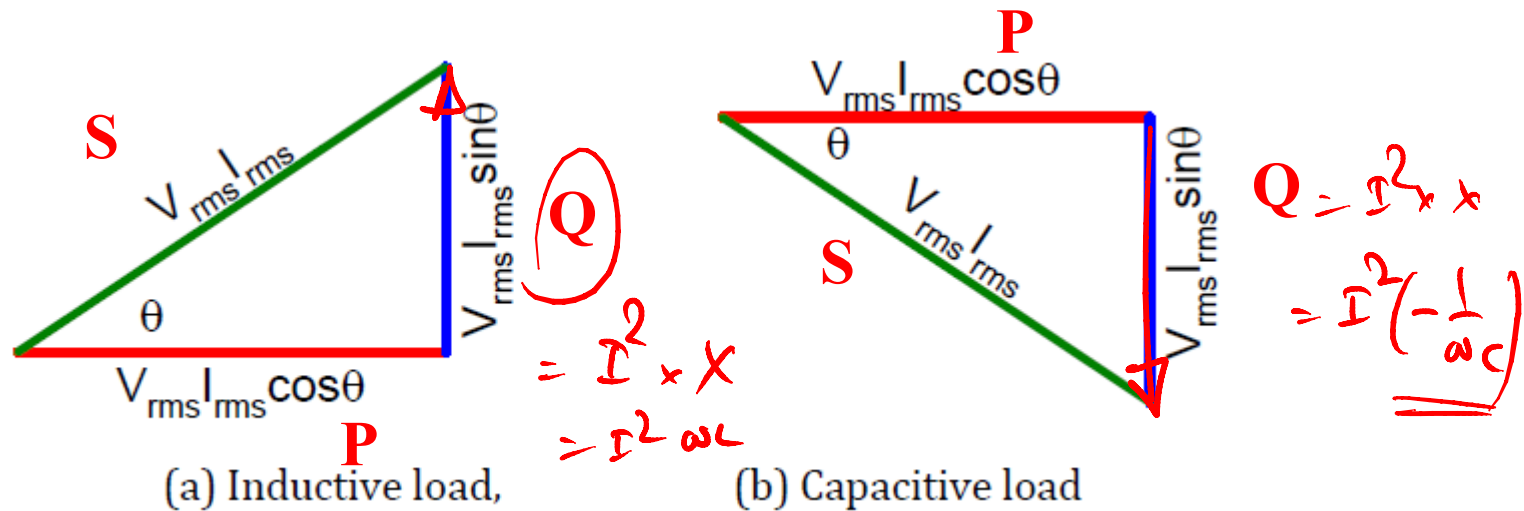

P – Real (or active) power; power consumed in the resistive part of the circuit


Q – Reactive power consumed by the device, due to inductor or capacitor

Example 2: Compute the instantaneous, (average, real) and reactive powers in the following circuit if $v(t) = 14.14 \sin(377t)$ $V = \frac{14.14}{\sqrt{2}} \angle 0^\circ$

$$R = 4 \Omega, \quad L = 8 \text{ mH} \quad X_L = \omega \times L = 377 \times 8 \times 10^{-3} = 3 \Omega$$


$$Z = R + jX = \underline{4 + j3}$$
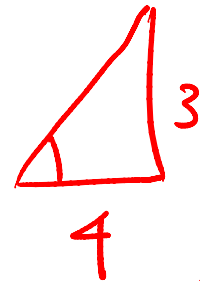
$$I = \frac{V}{Z} = 2.0 \angle -36.87^\circ \text{ A}$$



$$\theta = \tan^{-1}\left(\frac{3}{4}\right) = 36.87^\circ$$
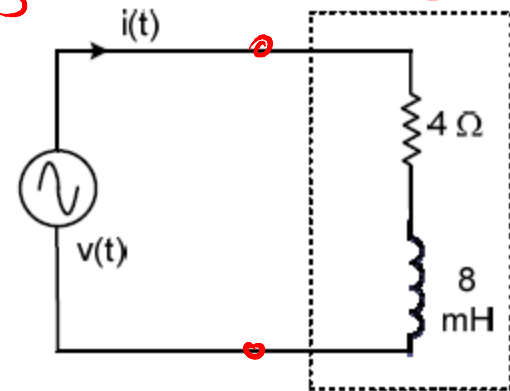
$$i(t) = 2.0\sqrt{2} \sin(377t - 36.87^\circ) \text{ A}$$




$$p(t) = v(t) \cdot i(t) = 14.14 \times 2.0 \times \sqrt{2} \cdot \sin(377t) \cdot \sin(377t - 36.87^\circ)$$

$$P_{\text{avg}} = P_s = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos \theta = \frac{14.14}{\sqrt{2}} \times 2.0 \times \cos(36.87^\circ) \text{ W}$$

$$Q = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \sin \theta = \frac{14.14}{\sqrt{2}} \times 2.0 \cdot \sin(36.87^\circ) \text{ VAR}$$

Complex Power


Apparent power, $|S| = V_{\text{rms}} I_{\text{rms}}$

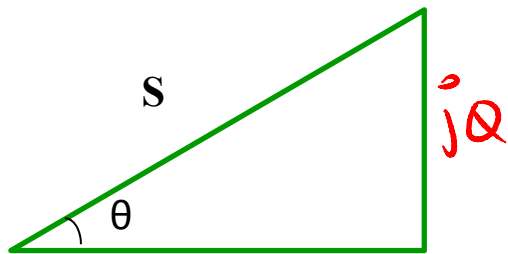

P

$$S = P + jQ$$

↑

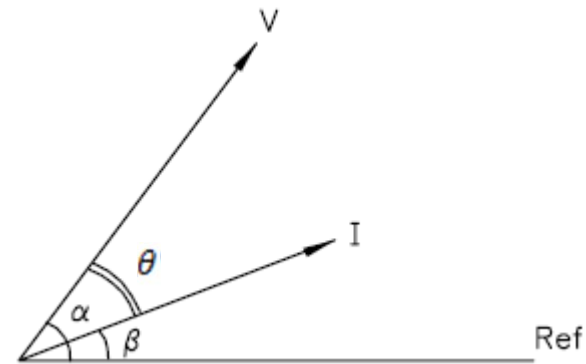


Complex Power

① **Complex power $S = \underline{V} \cdot \underline{I}^*$**

Complex power, $S = V_{\text{rms}} I_{\text{rms}} \cos \theta + j V_{\text{rms}} I_{\text{rms}} \sin \theta$

$$S = |S| \cos \theta + j |S| \sin \theta$$

② $= P + jQ$

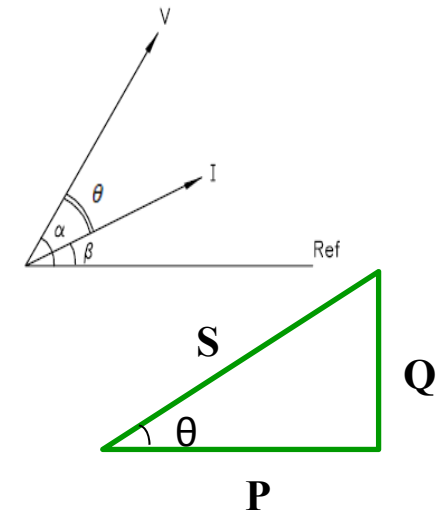

S	Complex power	VA	$S = S \angle \theta = P + jQ = VI^* =$ $= V I \angle \theta = V I (\cos \theta + j \sin \theta)$
$ S $	Apparent power	VA	$ S = V I = \sqrt{P^2 + Q^2}$
P	Active power Average power, Real power	W	$P = \text{Re}(S) = S \cos(\theta) = V I \cos(\theta)$
Q	Reactive power	var	$Q = \text{Im}(S) = S \sin(\theta) = V I \sin(\theta)$

Example 1: A voltage source with series resistor is connected to a parallel combination of inductor and resistor. Find the complex power, and hence real power and reactive power delivered to the load.

$$S = V_L \cdot I_L^* = P + jQ$$

$$V_L = V_S \times \frac{Z_L}{4 + Z_L} = 110 \angle 0^\circ \times \frac{5.14 \angle 59^\circ}{4 + 5.14 \angle 59^\circ}$$

$$= 70.9 \angle 25.46^\circ$$


$$I_L = \frac{V_L}{Z_L} = \frac{70.9 \angle 25.46^\circ}{5.14 \angle 59^\circ} = 13.79 \angle -33.54^\circ$$

$$Z_L = \frac{10 \times (j6)}{10 + j6} = 5.14 \angle 59^\circ$$

$$S = V_L \cdot I_L^* = 70.9 \angle 25.46^\circ \times 13.79 \angle 33.54^\circ$$

$$= 977.71 \angle 59^\circ = \underline{\underline{503.56 + j838}}$$

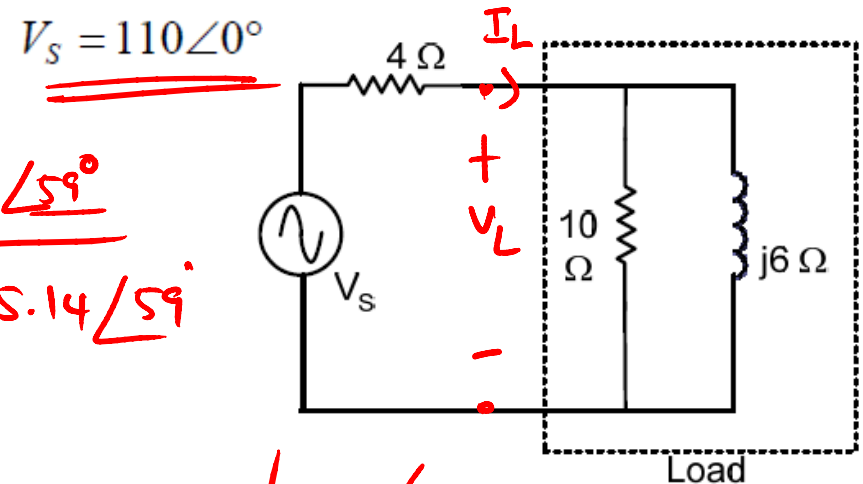
$\underbrace{\hspace{1cm}}_P \quad \underbrace{\hspace{1cm}}_Q$





Power Factor of an a.c. circuit

Now, we will define Power Factor of an a.c. circuit as the ratio of real power to the apparent power.

$$\text{Power Factor} = \frac{P}{|S|} = \frac{P}{|V||I|} = \cos(\theta)$$

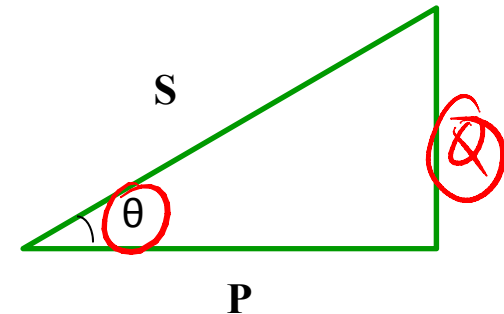



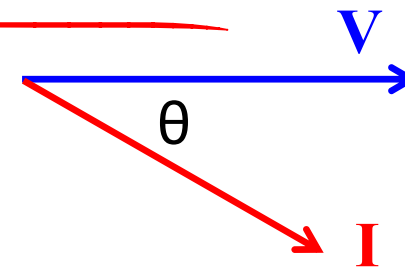
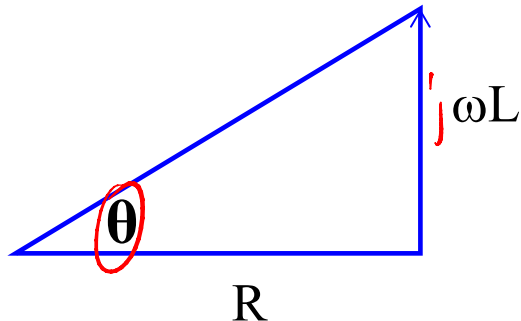
Power factor angle (θ) is the same in power triangle, impedance triangle, and the angle between voltage and current.



Leading \ Lagging Power Factor



Lagging

Inductive

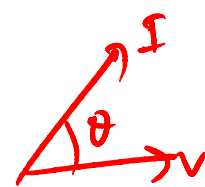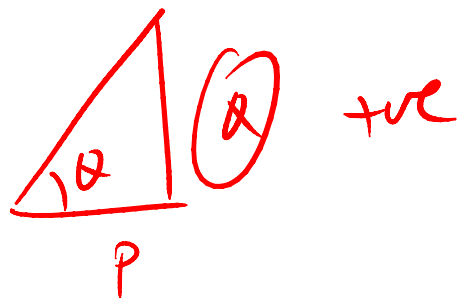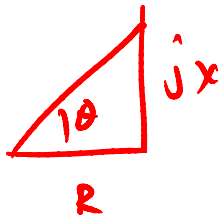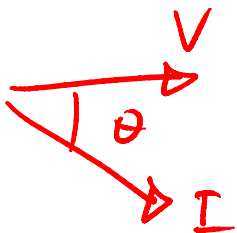


(Leading)

Capacitive

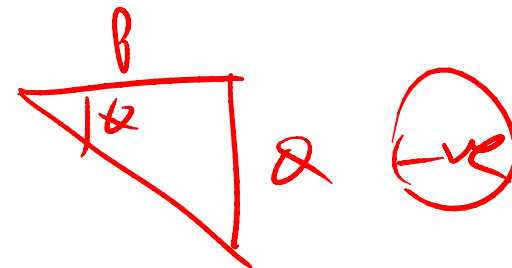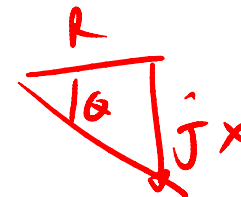

Power Factor

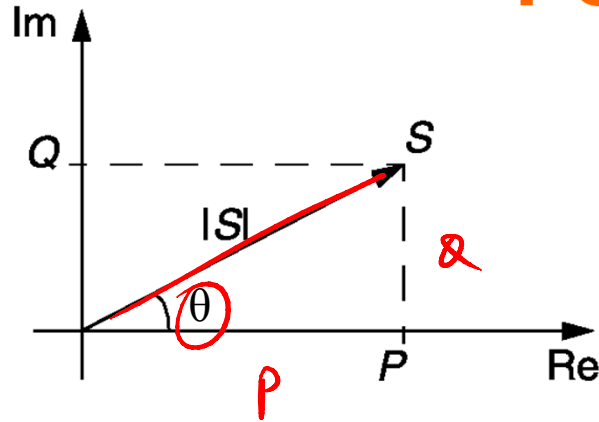

$$P = |S| \cos(\theta) = |V||I| \cos(\theta)$$

$$|S| = \sqrt{P^2 + Q^2}$$

$$\text{P.f.} = \cos(\theta) = \frac{P}{|S|} = \frac{P}{\sqrt{P^2 + Q^2}} \quad (1)$$

$$\underline{\underline{\cos(\theta)}} = \cos\left(\tan^{-1}\left(\frac{Q}{P}\right)\right) \quad (2)$$

Power Factor Correction

Loads are usually connected to a fixed voltage supply, e.g. 220V, 50 Hz in Singapore, hence V_{rms} is given.


$$\underline{p.f.} = \frac{P}{V_{rms} I_{rms}}$$

$$\text{Or } I_{rms} = \frac{P}{V_{rms} \times \cos\theta}$$


To deliver a certain amount of power to the load, current will be larger if power factor is smaller.

Hence it is desirable that power factor be as close to 1 as possible.
i.e. θ should be as small as possible.

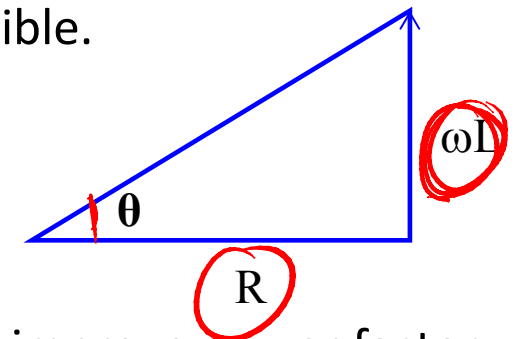Once the load is connected, its θ cannot be changed.



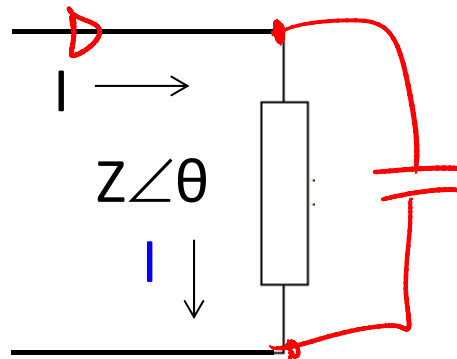Another reactive element can be added parallel to the load to improve power factor.




If the load is originally inductive, choose a capacitor

If the load is originally capacitive, choose an inductor as correcting device

Power Factor Correction

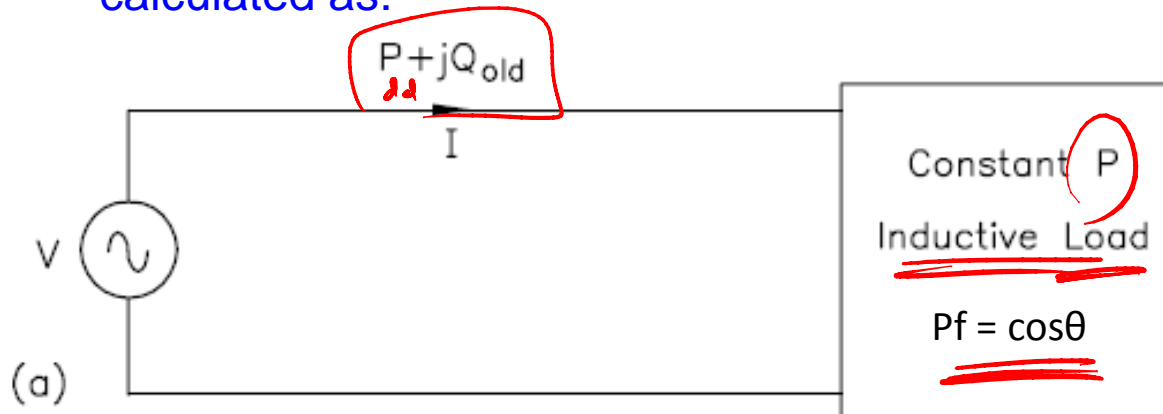If P is the active power consumption of the load, the current drawn by the load can be calculated as:




$$\checkmark \underline{P} = 1000 \text{ W} = |S| \cos \theta$$

$$\checkmark P.f. = 0.8 \text{ lagging} = \cos \theta$$

$$\rightarrow Q = |S| \sin \theta$$

$$= \frac{P}{P.f.} \times \sin(\cos^{-1}(P.f.))$$

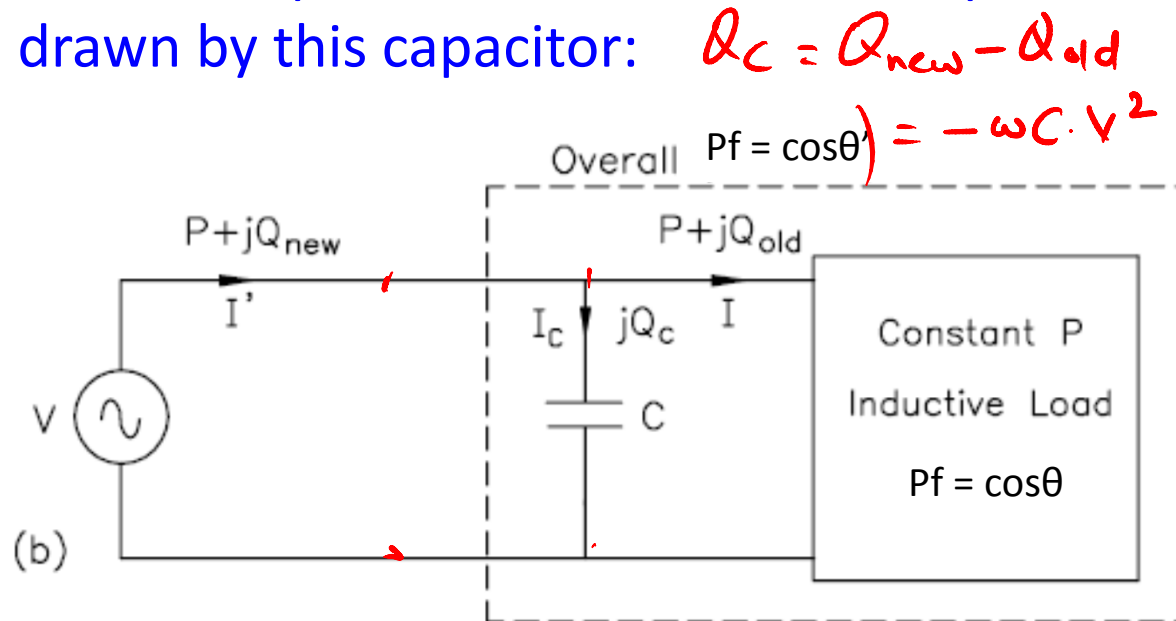When a capacitor is connected to improve the power factor, the current drawn by this capacitor:




$$P + jQ_{new} = P_{old} + j(Q_{old} + Q_c)$$

$$P.f. \text{ new} = \cos \theta'$$

$$Q_{new} = \frac{P_{old}}{\cos \theta'} \sin \theta'$$


Power Factor Correction

Power triangle method

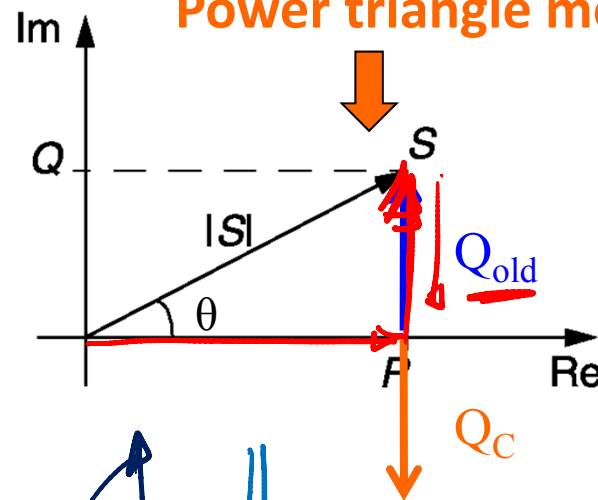

$$P = |S| \cos(\theta) = |V| |I| \cos(\theta)$$

$$|I| = P / |V| \cos(\theta)$$

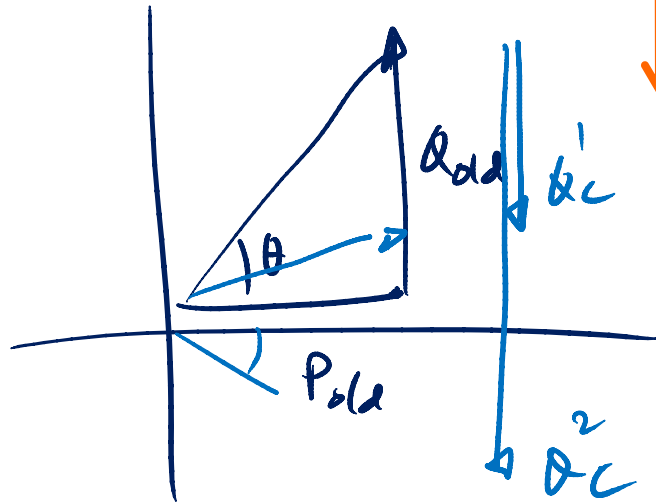

Example 2 - Power Factor Correction

A load connected across a 200 V, 50Hz line draws 10 kW at 0.5 power factor lagging. A capacitor C is now connected in parallel with the load to improve the power factor. What must be the value of C to make the overall power factor


(i) 0.9 lagging, (ii) unity and (iii) 0.8 leading?


Solution: Take source voltage as reference. So, current drawn at 0.5 p.f. lagging is

$$P = 10 \text{ kW}$$

$$\text{P.f.} = 0.5 \text{ lag}$$
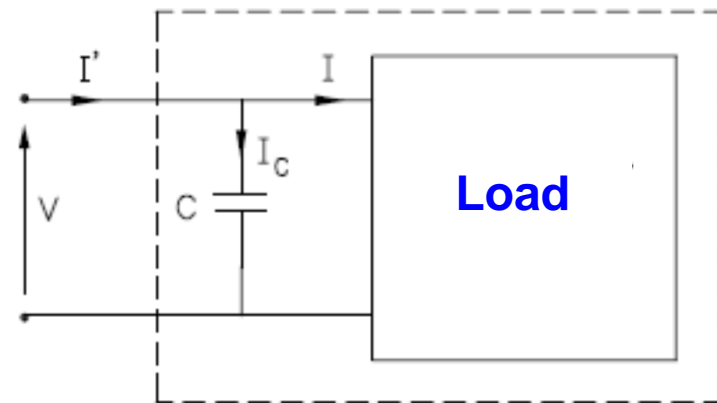
$$Q_{dd} = \frac{P}{\text{P.f.}} \times \sin(\cos^{-1} \text{P.f.}) = \frac{10000}{0.5} \times \sin(\cos^{-1} 0.5) = 17320 \text{ VAR.}$$



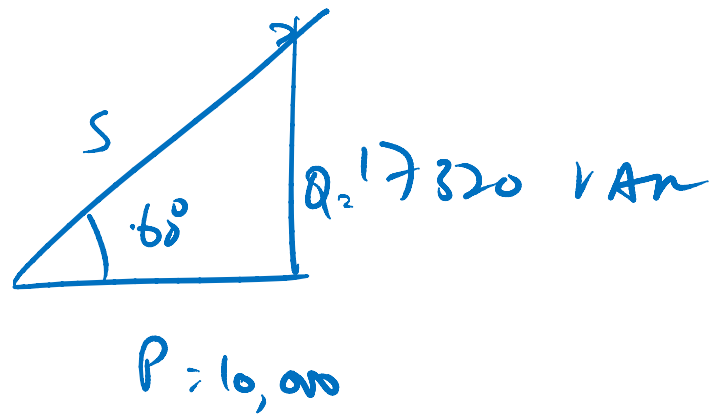


17320 VAn

$P = 10,000$

Old. (one)

Case 1: 0.9 lagging

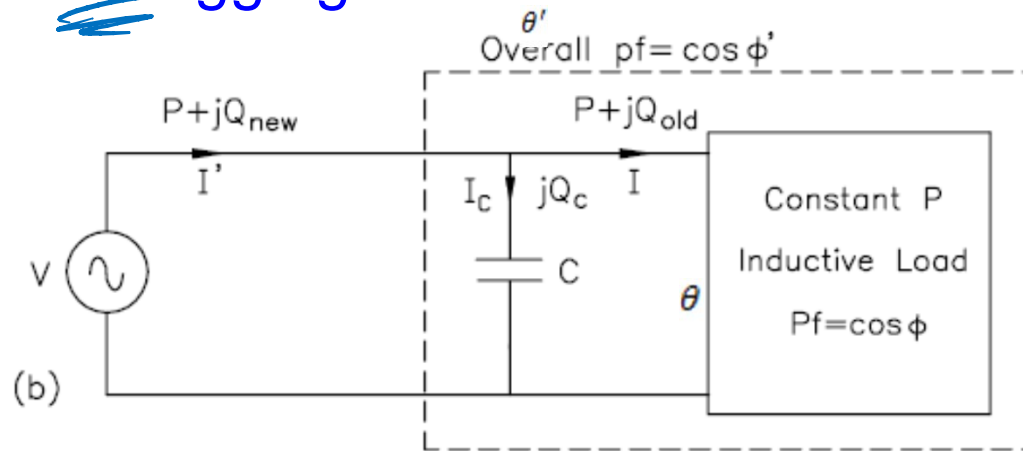


$$\begin{aligned}
 Q_c &= Q_{new} - Q_{old} \\
 &= 4843 - 17320 \\
 &= -12477 \\
 &= -\omega \cdot C \cdot V^2
 \end{aligned}$$

$$\begin{aligned}
 \underline{P_{new}} + j Q_{new} &= P_{old} + j Q_{new} \\
 &= 10520 + j Q_{new}
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow C &= \frac{12477}{2\pi \cdot 50} \\
 &\times \frac{1}{200} \\
 &\text{F.}
 \end{aligned}$$

$$\begin{aligned}
 Q_{new} &= \frac{P}{P.f.} \times \sin(\cos^{-1}(P.f. \text{ new})) \\
 &= \frac{10520}{0.9} \cdot \sin(\cos^{-1}(0.9)) = 4843 \text{ VAR}
 \end{aligned}$$


Case 2: Unity p.f.

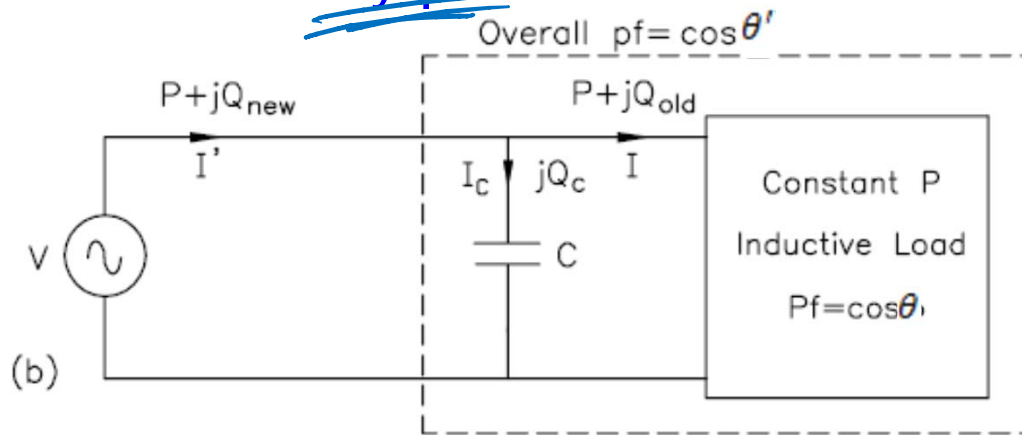

$$Q_{\text{new}} = 0 \quad Q_c = Q_{\text{new}} - Q_{\text{old}} = -17320$$

$$C = \frac{Q_c}{\omega V^2} = \frac{17320}{2\pi \times 50 \times 200} \text{ F}$$

Case 3: 0.8 leading

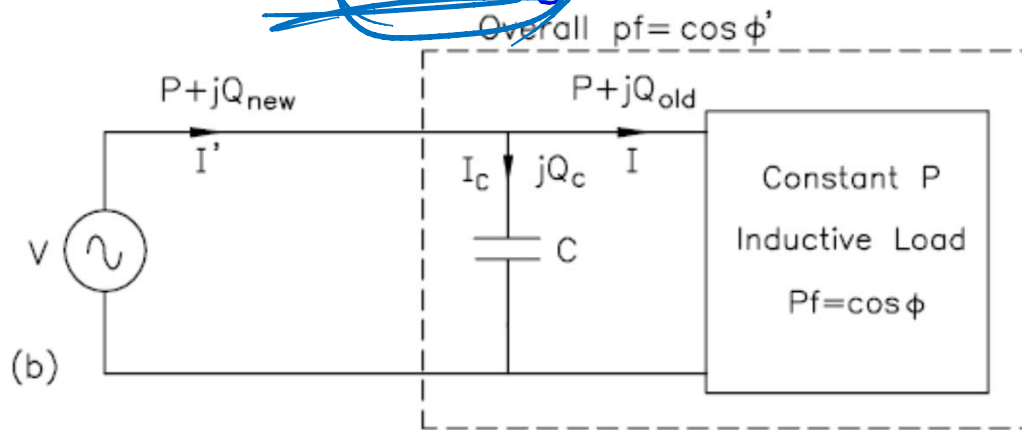

$$Q_{new} = \frac{P}{P.f.} \cdot \sin (\cos^{-1} 0.8)$$

$$= \frac{10000}{0.8} \cdot \sin (-36.87^\circ) = -7500 \text{ VAR.}$$

$$Q_c = Q_{new} - Q_{old} = -7500 - 17320 \text{ VAR}$$

$$\Rightarrow C.$$

Transmission Line Loss

Industrial load connected to a substation

V_s = Substation or sending end voltage.


V_L = Voltage at the load.

I = Current drawn by the load.

R = Resistance of the transmission line.

X = Reactance of the transmission line.

The transmission line loss is given by: $P_{\text{loss}} = |I|^2 R$

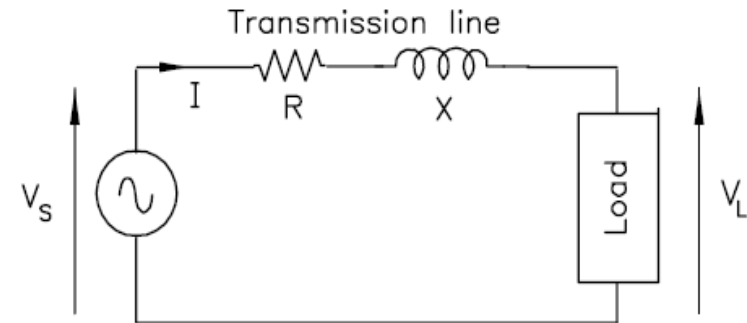


For the same real power demand, if the power factor of the load decreases, then $|I|$ increases as shown by the following equation. This results in heavy line losses.

$$|I| = \frac{P}{|V| \cos \theta}$$

A poor power factor results in higher current and hence higher power loss.

Capital Cost of Power Plants

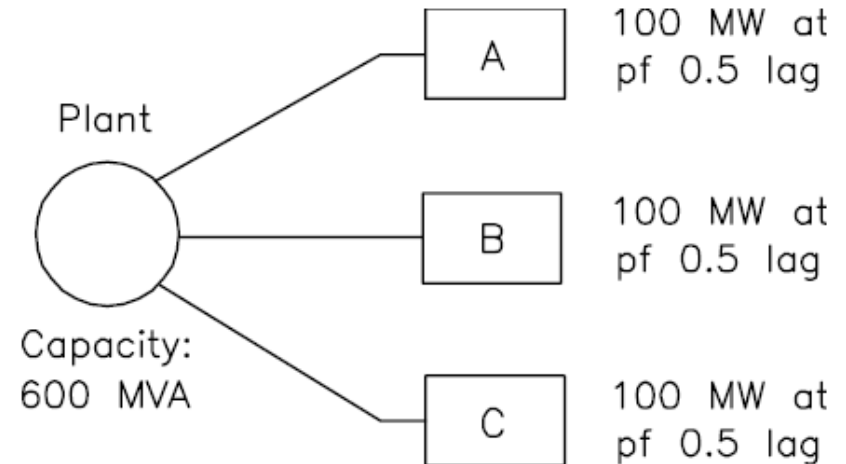Three industrial customers A, B and C are drawing power from the Power Plant. Let the load at each of the three industries be 100 MW at a p.f. of 0.5 lagging. The maximum demand of each consumer is



$$\text{Max. Demand} = |V||I| = \frac{P}{\cos \theta} = \frac{100}{0.5} = 200 \text{ MVA}$$

So the installed capacity of the plant should be

$$\sum \text{Max. Demand} = 600 \text{ MVA}$$


If \$X is the capital cost per annum per MVA of the plant, the total annual capital cost is

$$\text{Capital cost} = \$600X$$

The three consumers will share the capital cost equally in this case and each will pay \$200X.

If the load at each of the three industries is 100 MW at unity p.f., the maximum demand of each consumer is

$$\text{Max. Demand} = |V||I| = \frac{P}{\cos \theta} = \frac{100}{1.0} = 100 \text{ MVA}$$

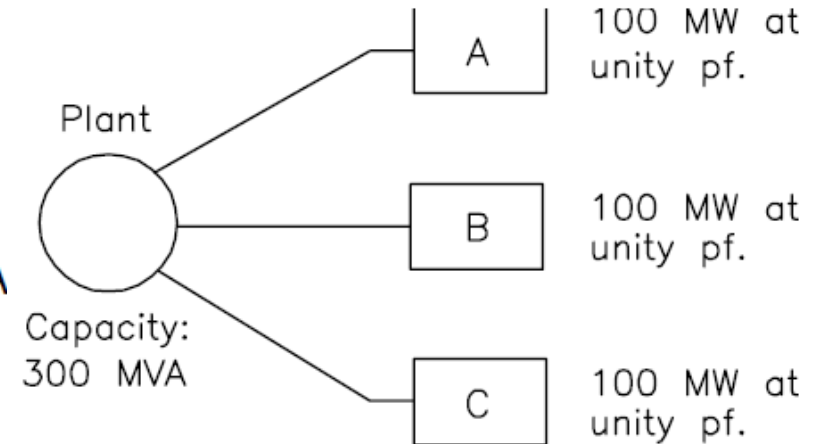

So the installed capacity of the plant should be

$$\sum \text{Max. Demand} = 300 \text{ MVA}$$

As the plant capacity is only 300 MVA, the total annual capital cost in this case is

$$\text{Capital cost} = \$300X$$

The three consumers will share the capital cost equally in this case also and each will pay \$100X.

Two points become evident from this example:

- Plant capacity gets affected by the maximum demand of each consumer.
- Annual capital cost gets affected by the power factor of the load.

A poor power factor results in higher capital cost.