

# EE2022 Electrical Energy Systems

## Lecture 7: Three-Phase Circuit Analysis Summary and Problem Solving

# Advantages of Balanced 3-Phase Systems

$$\underline{|S_{3\phi}| = \sqrt{3} \cdot V \cdot I} \quad ||| \quad \text{vs.} \quad \underline{|S_{1\phi}| = V \cdot I} \quad ||$$

- When compared to three single-phase circuits, three-phase circuits have better use of equipment and materials
  - More power can be transmitted per conductor
  - Lesser power losses in the conductors
- This implies reduced capital and operating costs of transmission and distribution.
- We can calculate voltage and current for only one phase and refer to other phases easily.


②

## An Additional Advantage of Balanced 3-Phase Circuit


- Constant power transfer to load.
  - This also implies constant mechanical power input for a generator.
  - When mechanical power input is constant, mechanical shaft torque is also constant.
  - This helps to reduce shaft vibration and noise, extending the machine's lifetime.

1.4. Real power has double-frequency  
( $2\omega$ )

# Three-Phase Voltage Sources

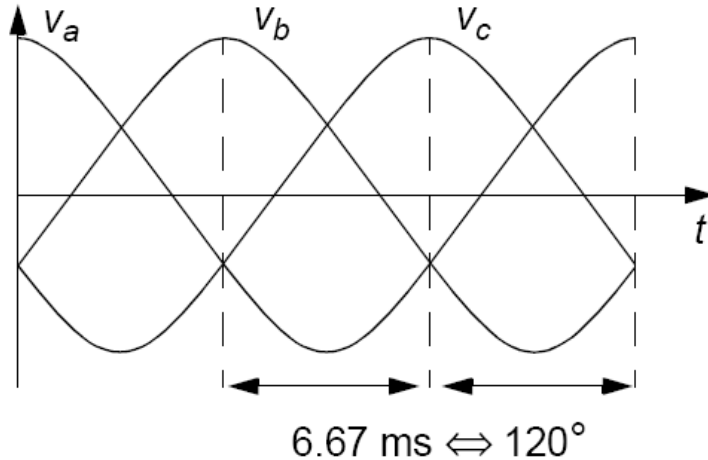


$$\begin{aligned} v_a &= \sqrt{2}|V| \cos(\omega t) \\ v_b &= \sqrt{2}|V| \cos\left(\omega t - \frac{2\pi}{3}\right) \\ v_c &= \sqrt{2}|V| \cos\left(\omega t - \frac{4\pi}{3}\right) \end{aligned}$$

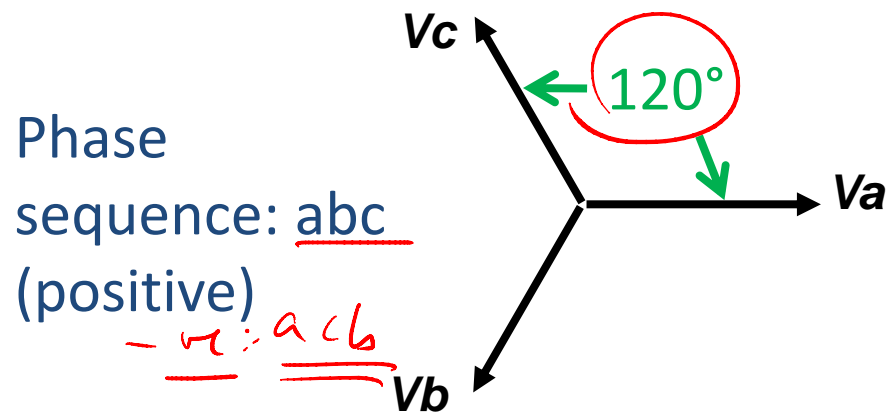


All three voltage sources have the same voltage magnitude, with **120 degrees** apart.

# Balanced Three-Phase Circuit

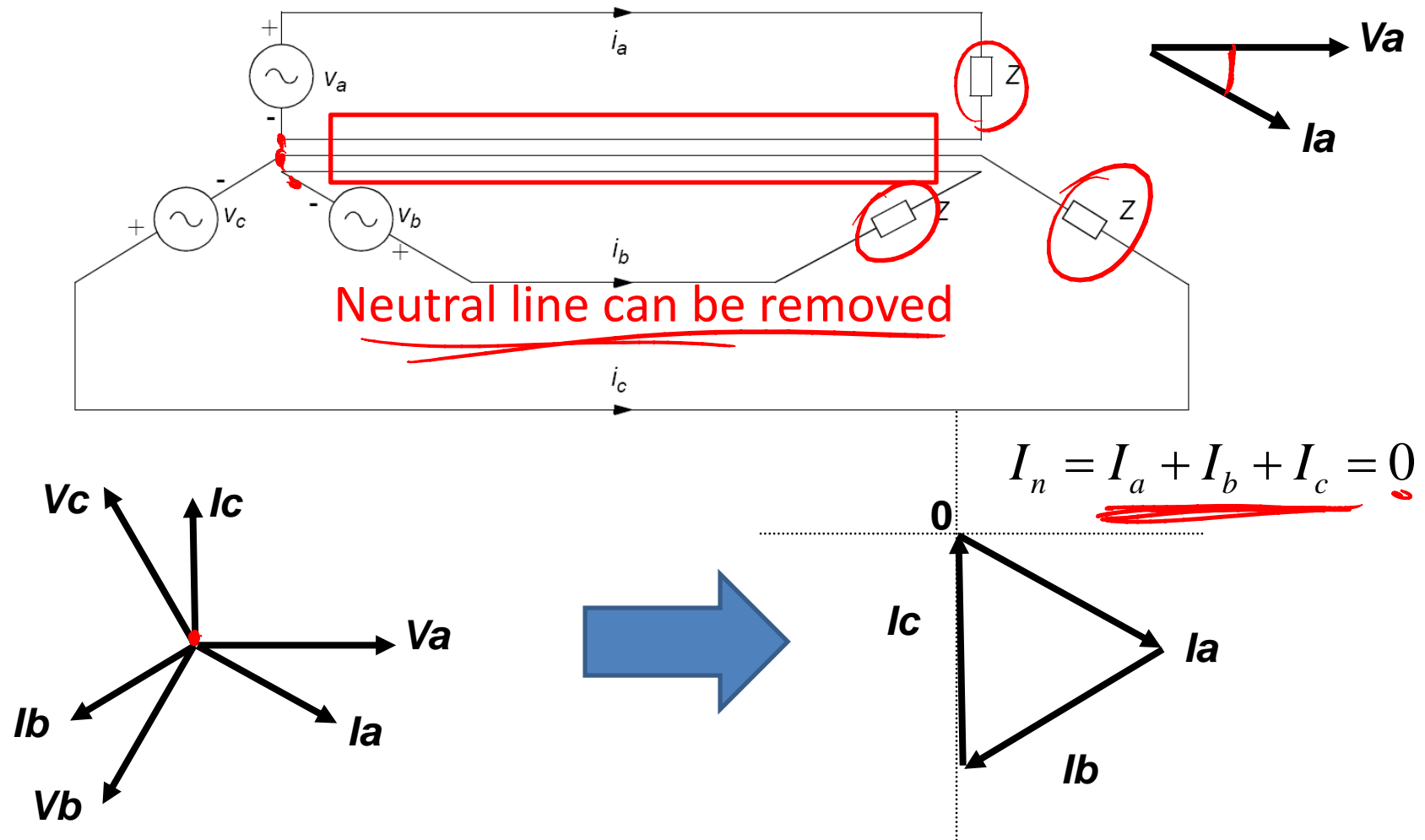


# Positive and Negative sequence

abc

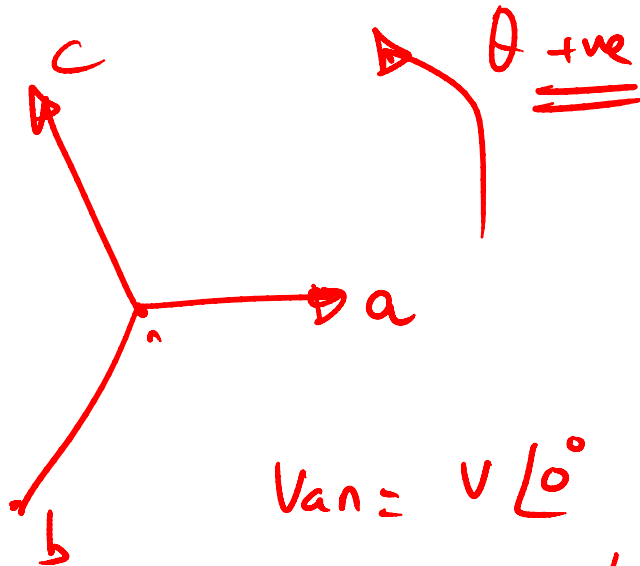


$$\begin{aligned}
 V_{an} &= V \angle 0^\circ \\
 V_{bn} &= V_{an} \angle -120^\circ \\
 V_{cn} &= V_{bn} \angle -120^\circ \\
 &= V_{an} \angle +120^\circ
 \end{aligned}$$

acb

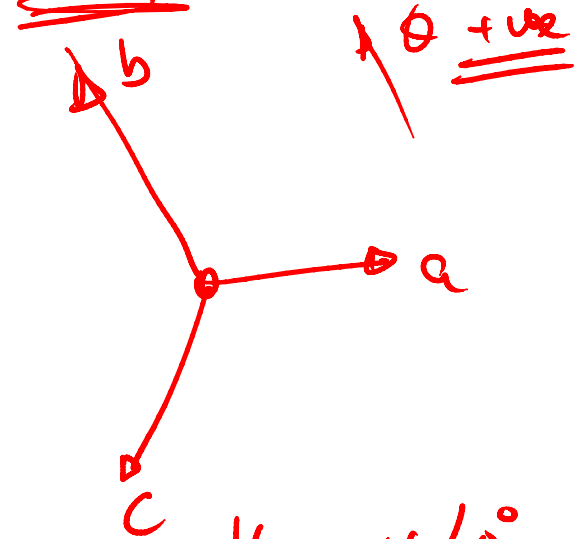

$$\begin{aligned}
 V_{an} &= V \angle 0^\circ \\
 V_{cn} &= V_{an} \angle -120^\circ \\
 V_{bn} &= V_{an} \angle +120^\circ
 \end{aligned}$$

# Line-To-Neutral (Phase) Voltage


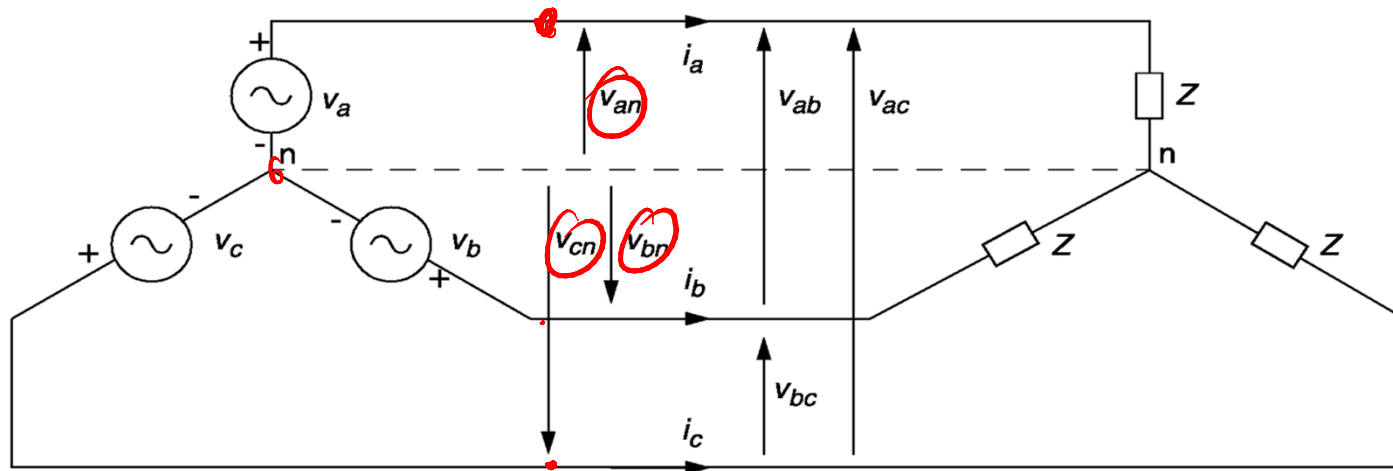


$V_{an}$ ,  $V_{bn}$ ,  $V_{cn}$  are called line-to-neutral voltage or phase voltage.

# Line-To-Line Voltage


- Voltage is given as line-to-line voltage by convention.
- KVL:  $V_{ab} = V_{an} - V_{bn} = \sqrt{3}V_{an} \angle 30^\circ$

$$|V_{\text{Line-Line}}| = \sqrt{3}|V_{\text{Line-neutral}}|$$

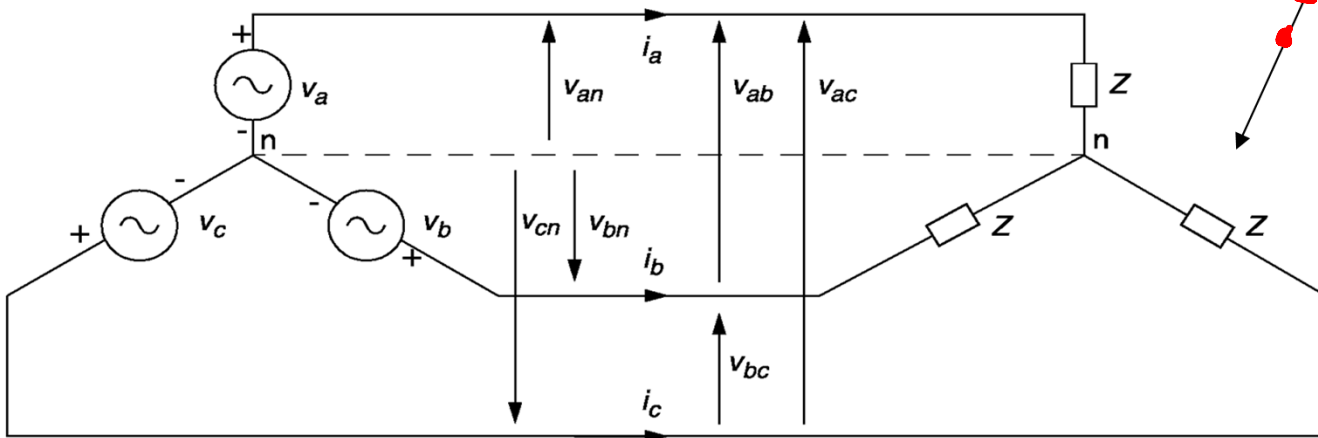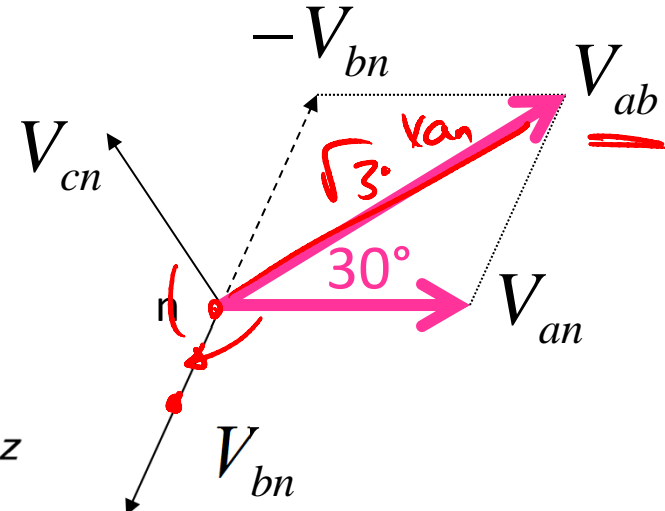



# Example

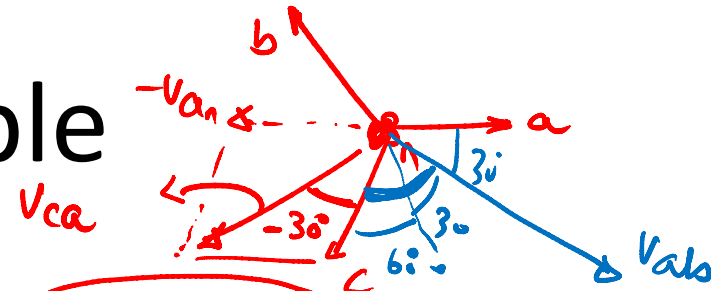


1. A balanced three-phase Y load has one phase voltage of  $V_{cn}=277 \angle 45^\circ$  V. If the phase sequence is negative sequence i.e. acb, find the line voltages  $V_{ca}$ ,  $V_{ab}$ , and  $V_{bc}$ .

(Answer:  $V_{ca}=480 \angle 15^\circ$  V,  $V_{ab}=480 \angle 135^\circ$  V, and  $V_{bc}=480 \angle -105^\circ$  V)

$$\begin{aligned}
 V_{ca} &= V_{cn} - V_{an} \\
 &= \sqrt{3} \cdot V_{cn} \angle -30^\circ \\
 &= \sqrt{3} \times 277 \angle 45^\circ \angle -30^\circ \\
 &= \sqrt{3} \cdot 277 \angle 15^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_{ab} &= \sqrt{3} \cdot V_{cn} \angle 90^\circ \\
 &= \sqrt{3} \times 277 \angle 45^\circ \angle 90^\circ \\
 &= \sqrt{3} \times 277 \angle 135^\circ
 \end{aligned}$$

# Line Current

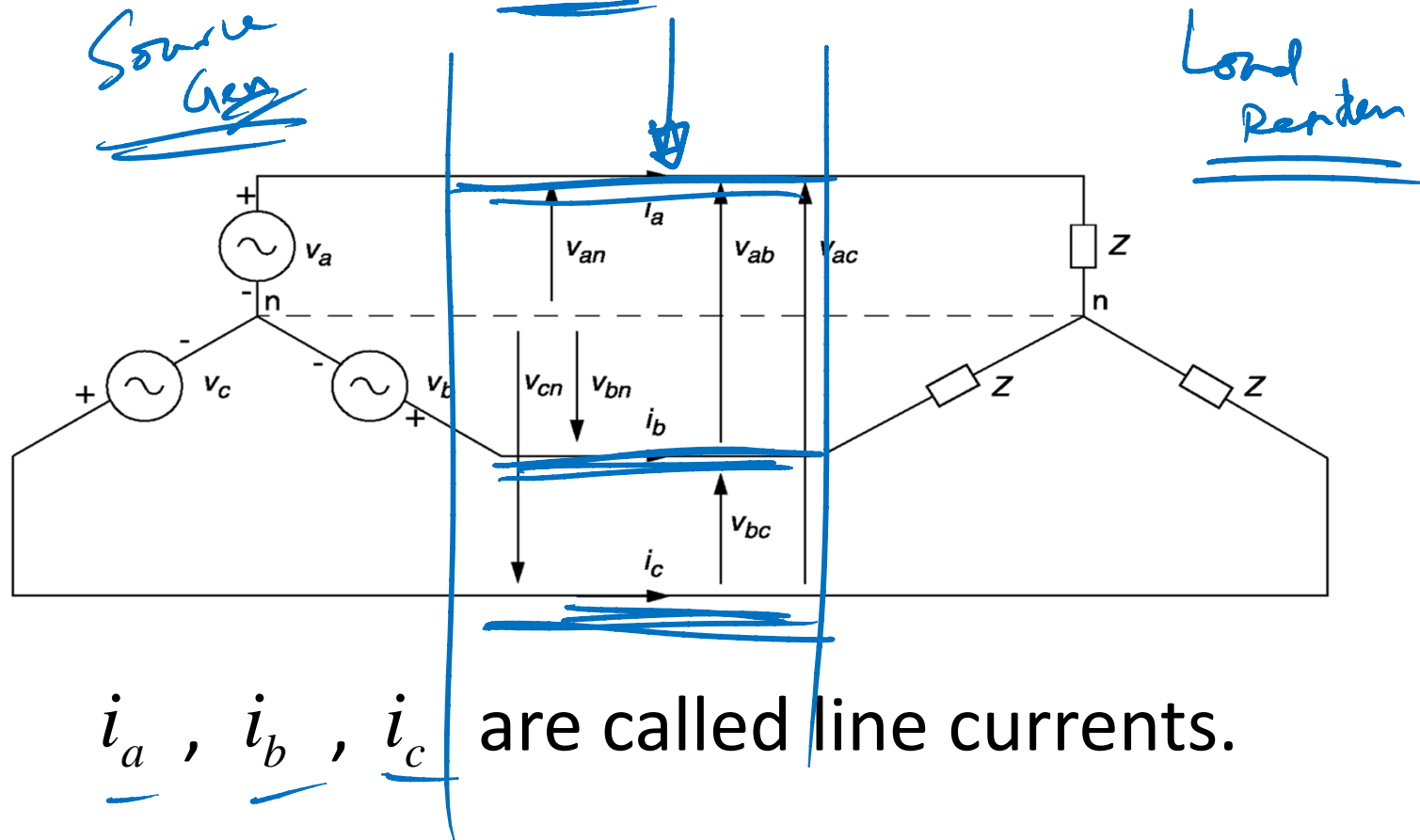


# Line Current VS Phase Current


$$\sqrt{3}, /30^\circ$$

$$I_a = I_{ab} - I_{ca}$$

## Wye Connection

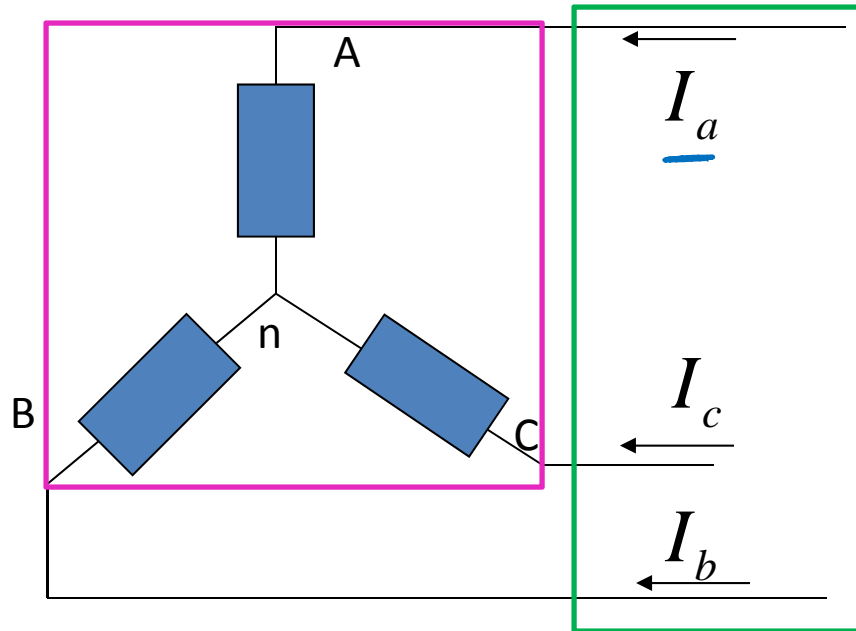


## Delta Connection

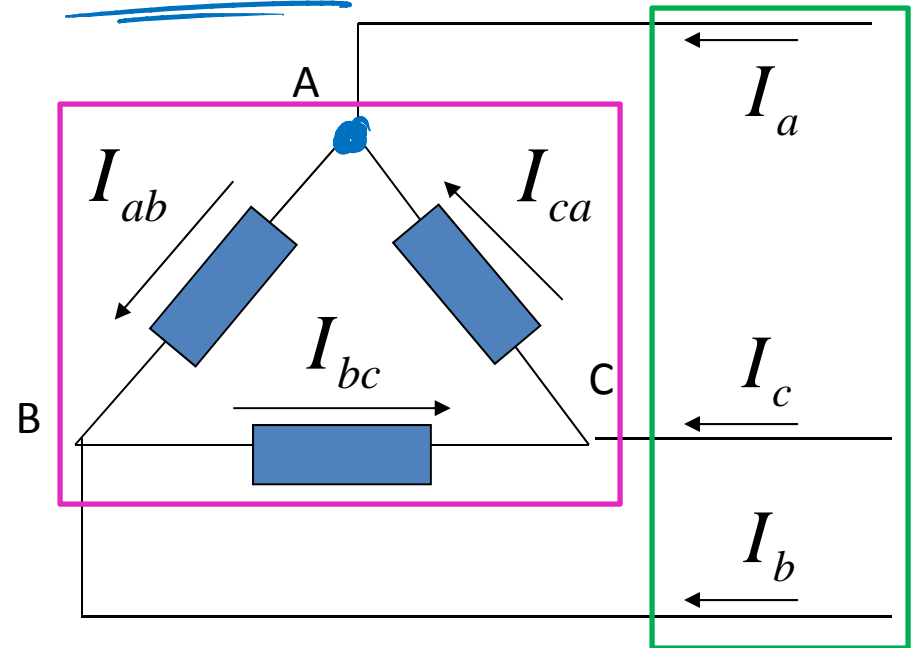

Currents through the three-phase conductor lines are called 'Line currents'.

Currents carried by the load impedance are called 'Phase currents' or 'Load Current'.

# Delta-Wye Load Transformation

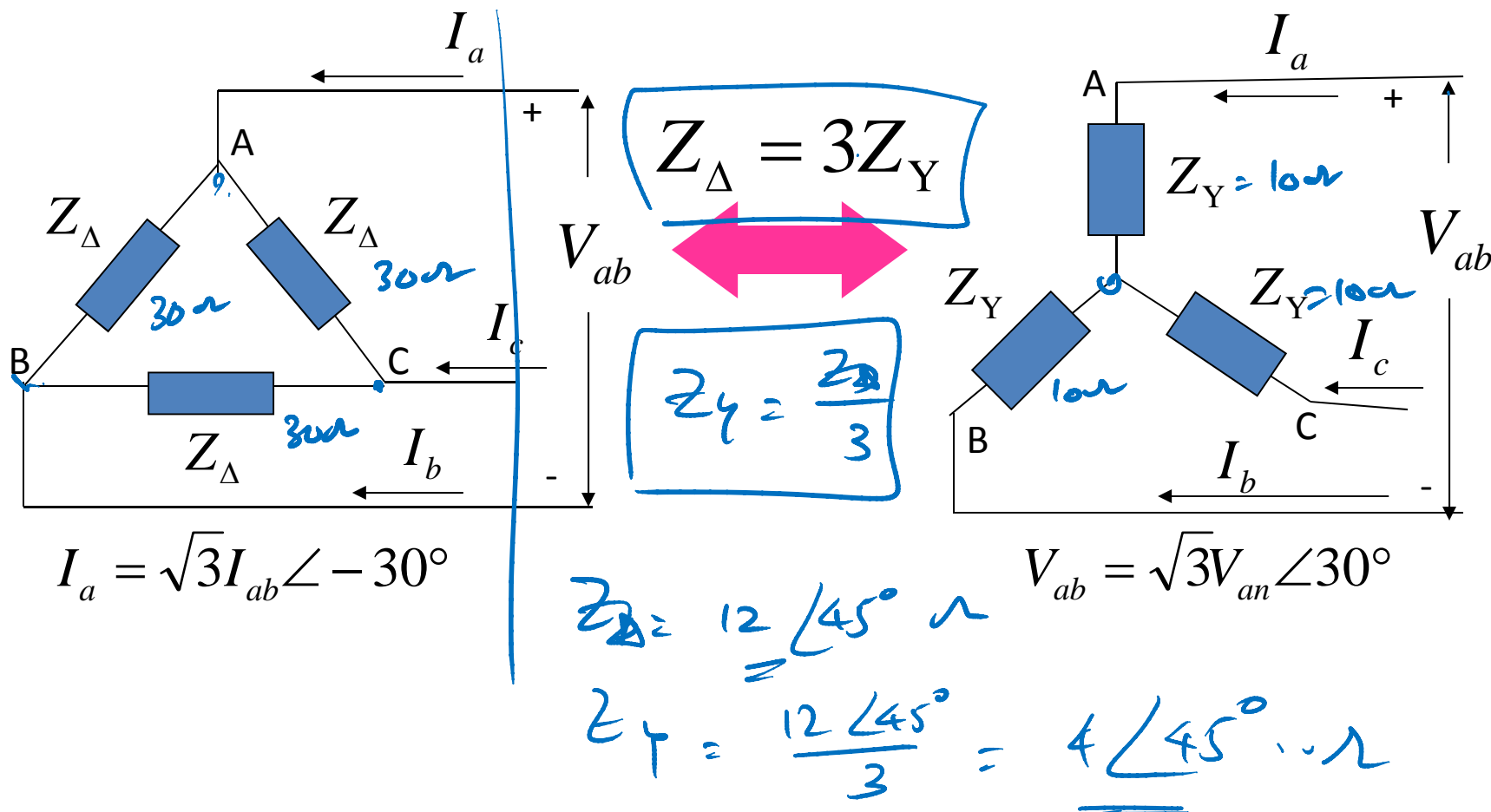

# Summary

- Three-phase voltage sources
  - Positive and negative sequences
- Balanced three-phase circuit
  - Conditions
  - Advantages
- Balanced three-phase circuit
  - Line-to-neutral (phase) voltage
  - Line-to-line (line) voltage
  - Line current
- Wye-Delta connection
- Delta-Wye load transformation

$$|V_{\text{Line-Line}}| = \sqrt{3} |V_{\text{Line-neutral}}|$$


$$\sqrt{3} = 1.732$$

$$Z_{\Delta} = 3Z_Y$$
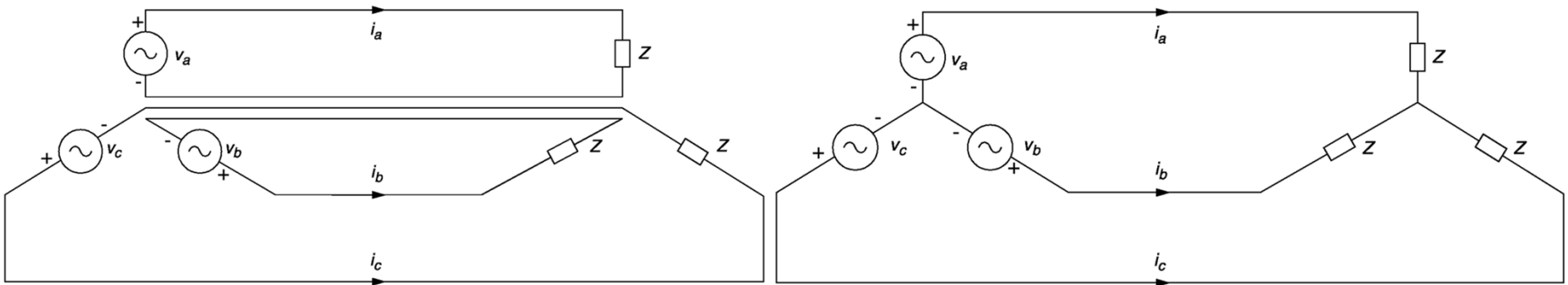
# Three Phase Power Calculation

- Three phase power is found from summation of each phase power.

$$S_{3\Phi} = \underline{V_{an}} \cdot \underline{I_a^*} + \underline{V_{bn}} \cdot \underline{I_b^*} + \underline{V_{cn}} \cdot \underline{I_c^*}$$




# Balanced Three-Phase Power

- From three phase power,

$$S_{3\Phi} = V_{an} I_a^* + V_{bn} I_b^* + V_{cn} I_c^*$$


- When the system is balanced, (assume positive sequence) we can write,
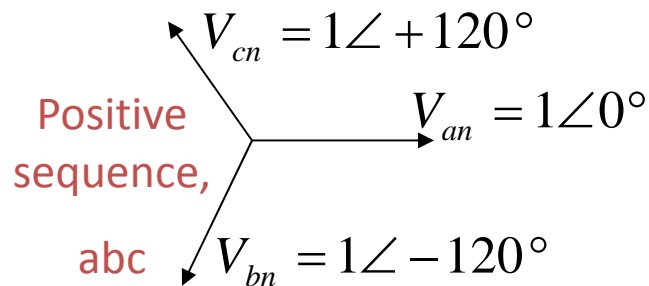
$$S_{3\Phi} = V_{an} I_a^* + V_{an} \angle -120^\circ (I_a \angle -120^\circ)^* + V_{an} \angle 120^\circ (I_a \angle 120^\circ)^*$$




$$S_{3\Phi} = 3V_{an} I_a^*$$

# Delta/Wye Connected 3-Phase Load

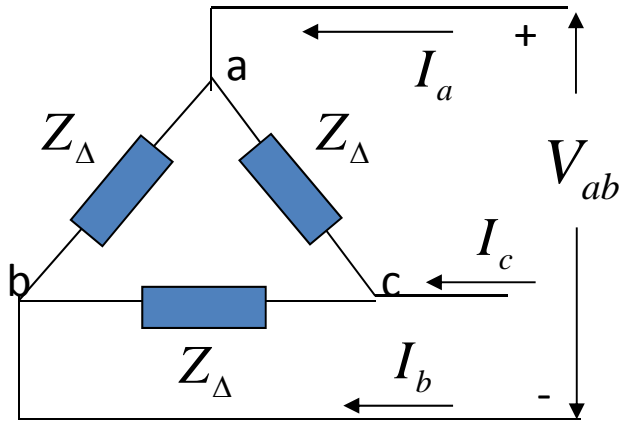

$$I_a = \sqrt{3}I_{ab} \angle -30^\circ$$

$$|S_{3\Phi}| = 3|V_{ab}I_{ab}^*| = \sqrt{3}|V_{ab}||I_a|$$

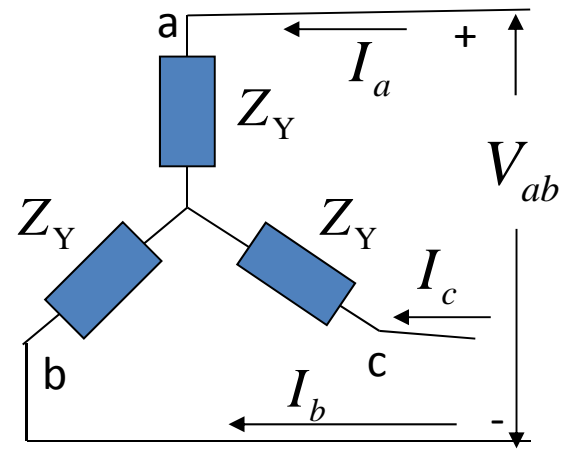

$$V_{ab} = \sqrt{3}V_{an} \angle 30^\circ$$

$$|S_{3\Phi}| = 3|V_{an}I_a^*| = \sqrt{3}|V_{ab}||I_a|$$

$$|S_{3\Phi}| = \sqrt{3}|V_{\text{Line-To-Line}}||I_{\text{Line}}|$$

( $3 \cdot V_{\text{phase}}$ )

$S_{3\Phi} \neq 3 \cdot V \cdot I$

$\sqrt{3} \cdot V \cdot I$



Assumption

Single-line diagram




Example example example...

# **PER PHASE ANALYSIS**

# Per Phase Analysis: Assumption

It must be  
balanced three-  
phase circuit.

$$I_n = I_a + I_b + I_c = 0$$

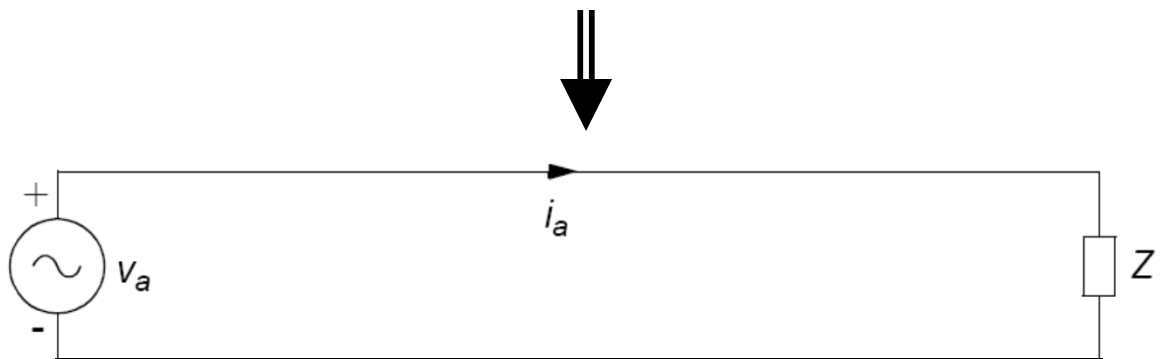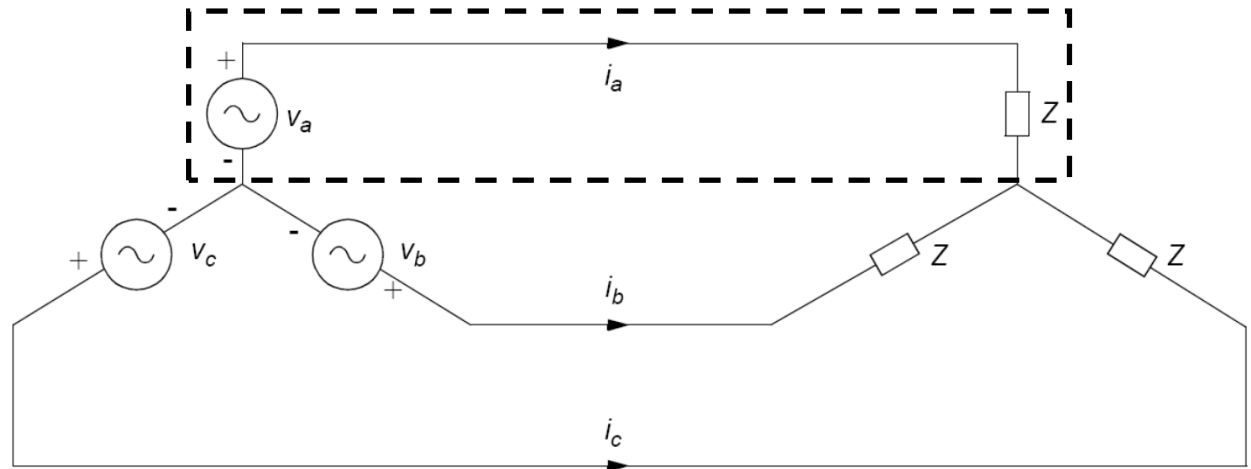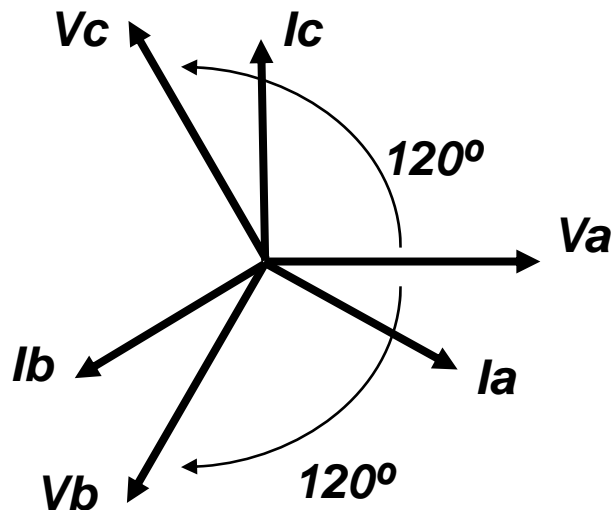


# Steps of Per Phase Analysis

- Make sure that the three-phase system is balanced.
  - The three-phase sources need to have the same ✓ magnitude with 120 degree phase difference.
  - ✓ The three-phase impedances must be of the same value (both phase and magnitude).
- **Convert** all Delta-connected sources/loads to Wye-connected sources/loads.  $\left. \begin{array}{l} \cdot V_u \rightarrow V_{LN} \\ \cdot Z_\Delta \rightarrow Z_Y \end{array} \right\}$
- Per phase analysis reduce three-phase circuit to ✓ single-phase circuit. We can apply the same concept used in single-phase.

# Example


- Given a one-line diagram,

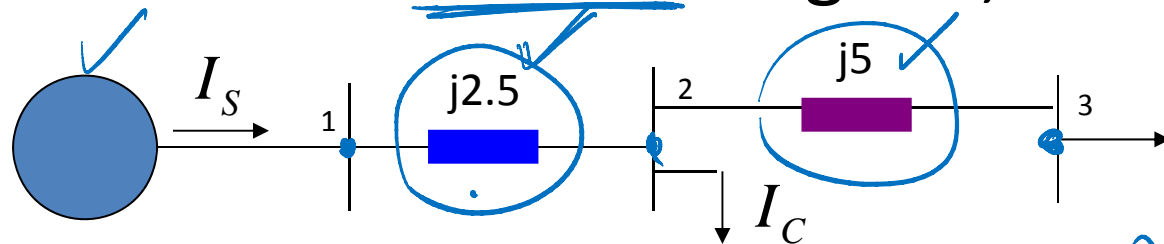


Source,  $\Delta$ -Connected  
Positive sequence

Load 1,  $\Delta$ -Connected  
Capacitor:  $Z_C = -j15$

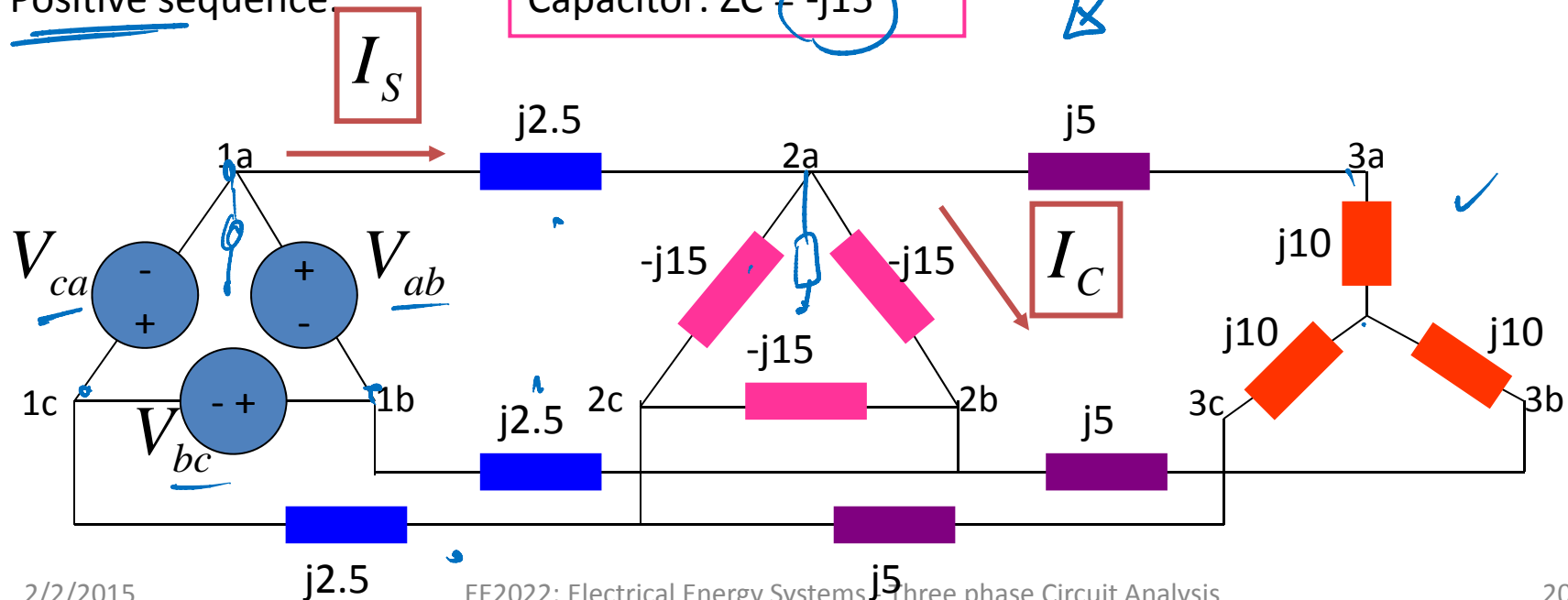
Load 2, Y-Connected  
Inductive:  $Z_L = j10$



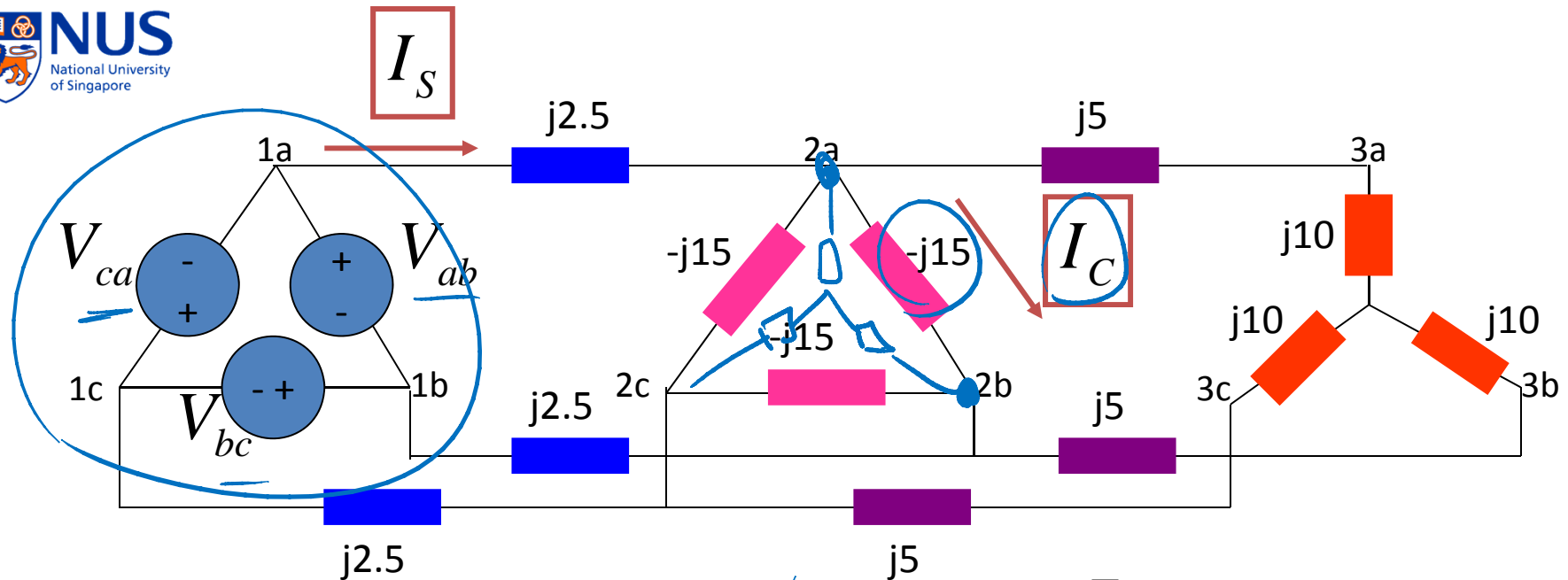


$$Z_Y = \frac{Z_{\Delta}}{3} = \frac{-j15}{3} = -j5$$


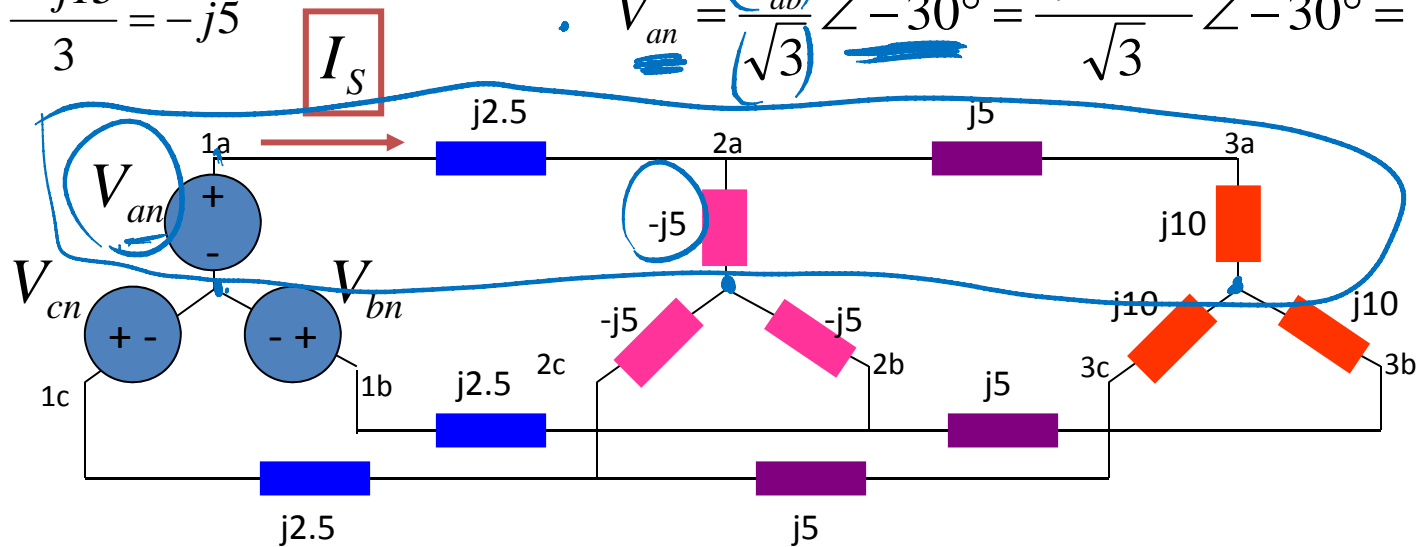
$$V_{an} = \frac{(V_{ab})}{(\sqrt{3})} \angle -30^\circ = \frac{\sqrt{3} \angle 0^\circ}{\sqrt{3}} \angle -30^\circ = 1 \angle -30^\circ$$



# Example 2: 1-Phase diagram

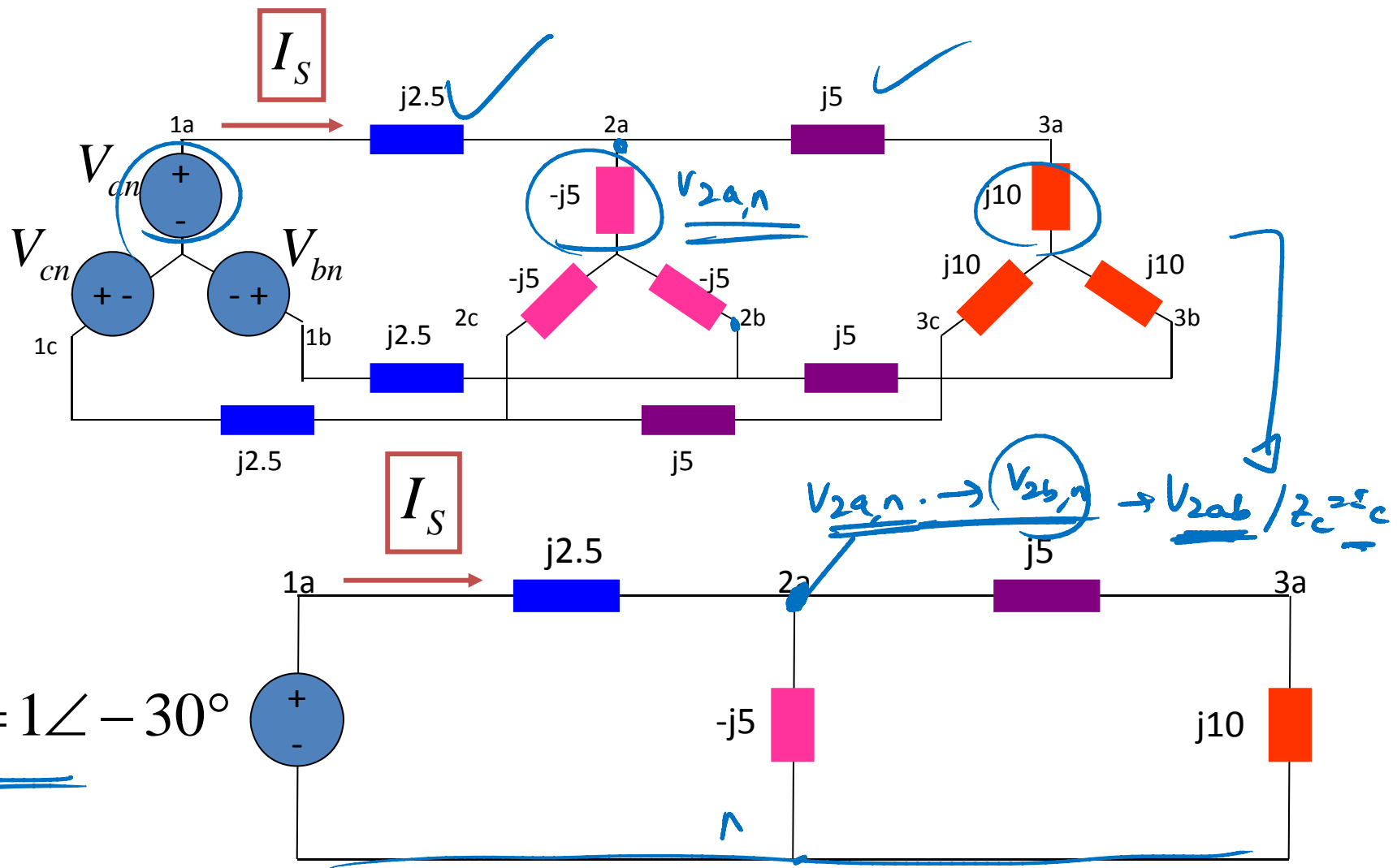

## Example 2: 1-Phase diagram

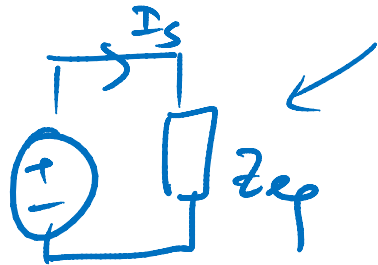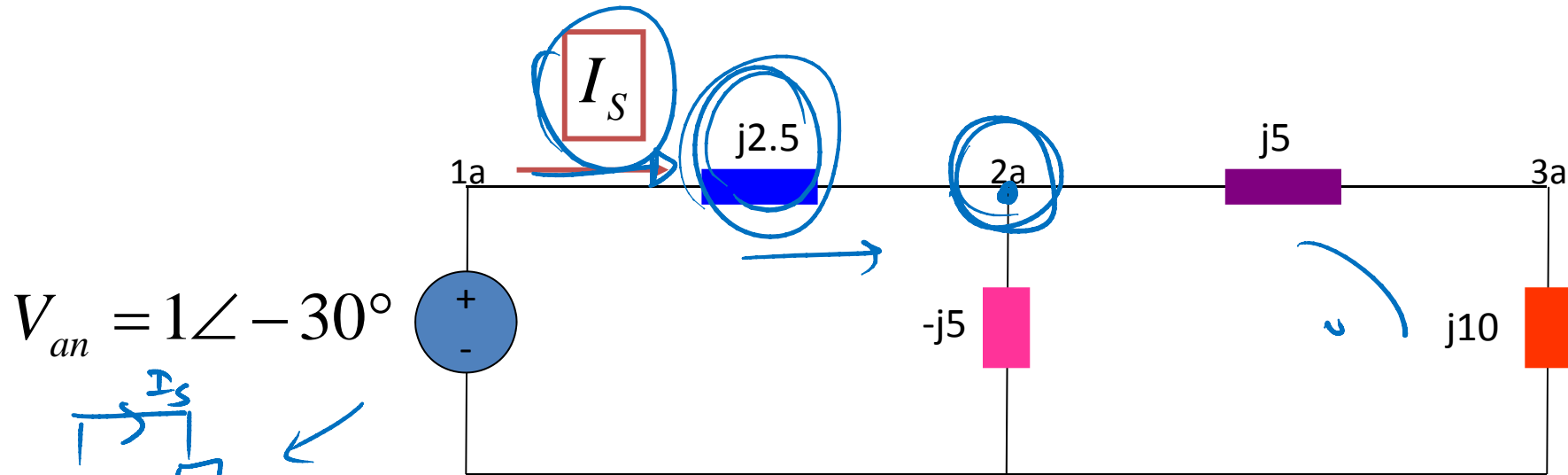


$$Z_{eq} = \underline{j2.5} + \left( \frac{(j10 + j5)(-j5)}{(j10 + j5) + (-j5)} \right) = \underline{-j5}$$

$$I_s = \frac{V_{an}}{Z_{eq}} = \frac{1\angle -30^\circ}{-j5} = \frac{1\angle -30^\circ}{5\angle -90^\circ} = \underline{0.2\angle 60^\circ \text{ A}}$$

$$\underline{V_{2a}} = \underline{V_{an}} - \underline{j2.5} \times \underline{I_s} = \underline{1.5\angle -30^\circ} \quad \text{We will use this to find } \boxed{I_C}$$

# Example 2: Final Calculation

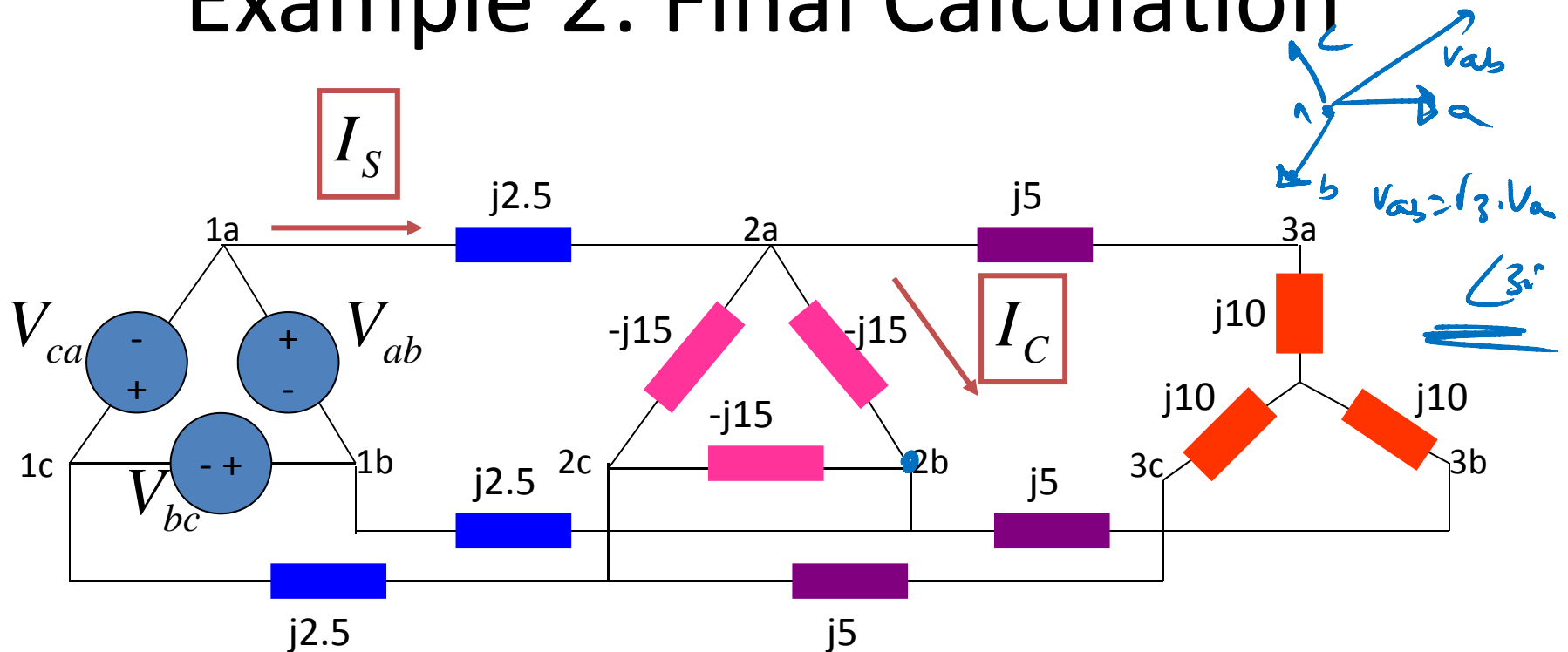

$$V_{2b} = V_{2a} \angle -120^\circ$$

$$I_C = \frac{V_{2a} - V_{2b}}{-j15} = \frac{1.5 \angle -30^\circ - 1.5 \angle (-30^\circ - 120^\circ)}{15 \angle -90^\circ} = \frac{\sqrt{3}}{10} \angle 90^\circ \text{ A}$$


$$\text{Ans: } I_S = 0.2 \angle 60^\circ, I_C = 0.1732 \angle 90^\circ$$




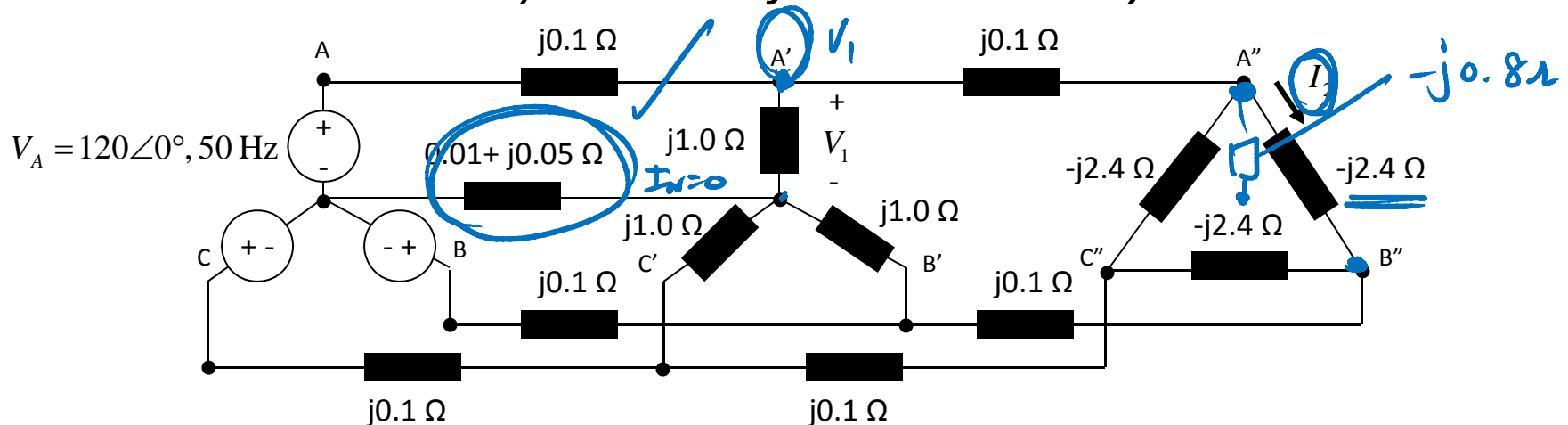
# Practice Problem 1

- (Final EE2022 AY2011/12 semester 1) Find the voltage  $V_1$  and current  $I_2$ .

– *Hint: remove the impedances that are in neutral line (why can we do this?) and transform delta to wye connection.*



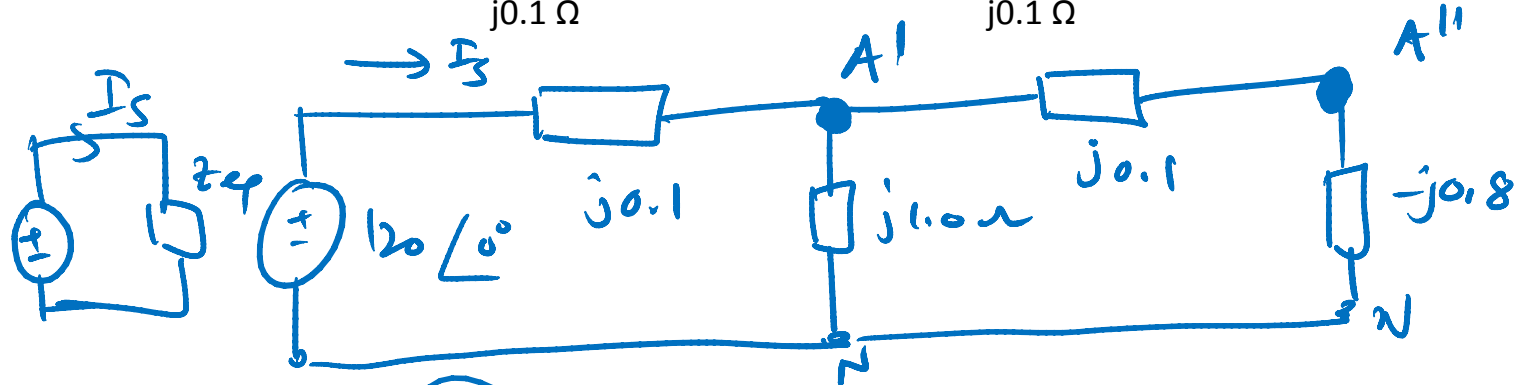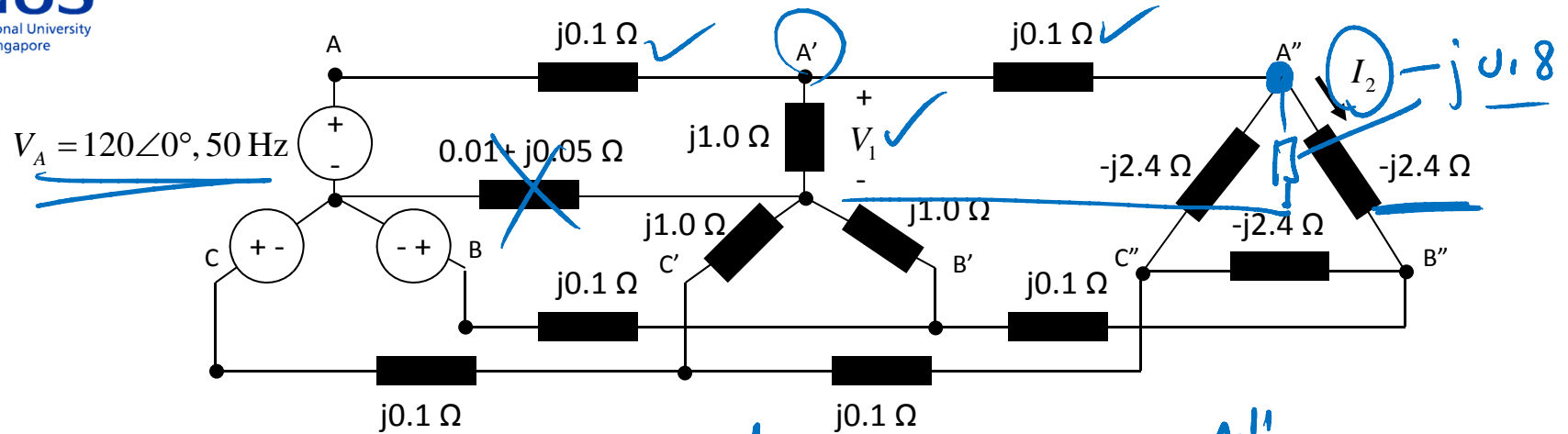Ans:  $V_1 = 125.37\angle 0^\circ, I_2 = 103.41\angle 120^\circ$



① Find  $I_s$ .


②  $V_{A'N} = 120\angle 0^\circ - I_s \times j0.1$

③  $V_{A''N} = V_{A'N} \times \frac{-j0.8}{j0.1 - j0.8}$

④  $V_{A''B''} = \sqrt{3} \cdot V_{A''N} \angle 30^\circ$  — ⑤  $I_2 = \frac{V_{A''B''}}{-j2.4}$

$$V = 208, Z_{\Delta}?, \text{ p.f.} = 0.8, Z_{\Delta} = \frac{(V)^2 \times \text{p.f.}}{P} = \frac{208^2 \times 0.8}{2000/3}$$

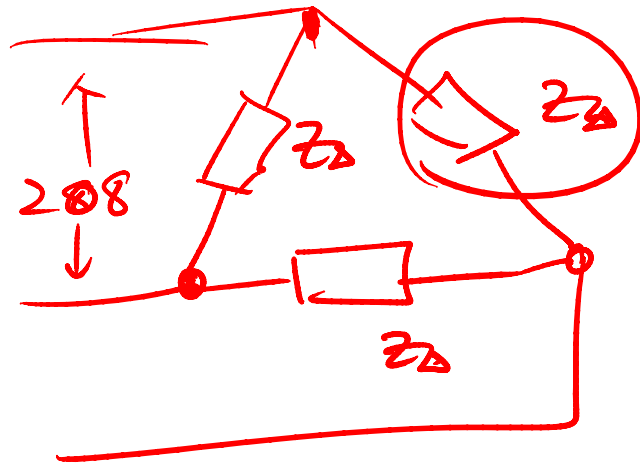8. In a 208-V three-phase circuit a balanced  $\Delta$  load absorbs 2 kW at a 0.8 leading power factor. Find  $Z_{\Delta}$ .  $= 51.91$   
(Answer:  $51.9 \angle -36.87^\circ \Omega$ )  
 $\theta = -\cos^{-1}(0.8)$



$$V_L = 208 \text{ V.} \quad \left\{ \begin{array}{l} Z_{\Delta} = 51.9 \angle -36.87^\circ \\ P_{3\phi} = 2 \text{ kW.} \end{array} \right.$$

$$\text{p.f.} = 0.8 \text{ leading.}$$

$$Z_{\Delta}?$$

Power consumed by each element is  $P_{1\phi} = \frac{2000}{3}$ .

Voltage across each element = 208V

$$P = |S| \times \text{p.f.} = V(I) (\text{p.f.}) = V \cdot \frac{V}{Z} \cdot \text{p.f.} = \frac{V^2}{Z} \cdot \text{p.f.}$$