

# **EE2022**


# **Electrical Energy Systems**

## **Lecture 3: Quiz on AC Systems Fundamentals**

## Revision:

- 1) Why 50/60HZ Sinusoidal AC is used in most power systems?
- 2) All about sinusoidals: Peak, RMS, Average, frequency, Angular frequency, Phase Angle, Phase difference.  
*Handwritten: 230V (RMS) with an arrow pointing to 'Average'*
- 3) Importance of RMS value in Power Calculation.  
*Handwritten: 230V (RMS) with a circle around 'RMS'*
- 4) Phasor: What is it? And How does this help?
- 5) What is impedance? Formulas.
- 6) How Phasor and Impedance are used in AC analysis.
- 7) Feeling at home with complex number calculations!

# Sinusoidal Currents And Voltages

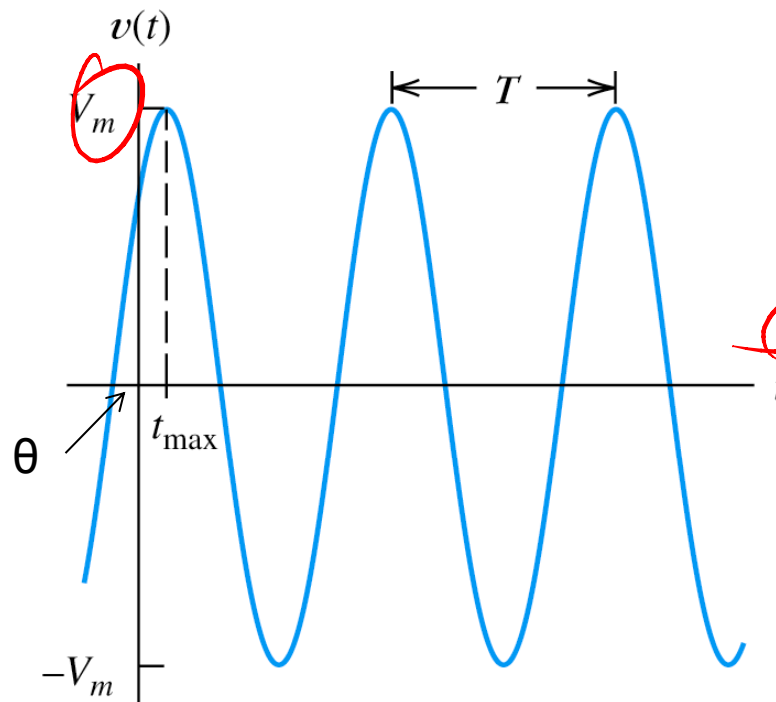

$V_m$  is the peak value

$\omega$  is the angular frequency in radians/sec

$$2\pi \times f \quad f = \frac{1}{T}$$

$\theta$  is the phase angle

$T$  is the period


phase angle

A sinusoidal voltage waveform given by  $v(t) = V_m \cos(\omega t + \theta)$ .

Note: Assuming that  $\theta$  is in degrees, we have  $t_{\max} = \frac{-\theta}{360} \times T$ .

For the waveform shown,  $\theta$  is  $-45^\circ$ .

# Root-Mean-Square Values

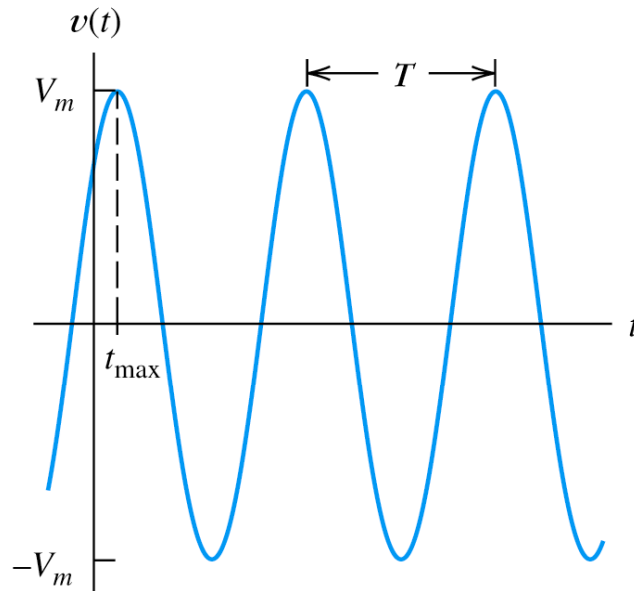

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \frac{V_m}{\sqrt{2}}$$

**Figure 5.1** A sinusoidal voltage waveform given by  $v(t) = V_m \cos(\omega t + \theta)$ .

Note: Assuming that  $\theta$  is in degrees, we have  $t_{\text{max}} = \frac{-\theta}{360} \times T$ .

For the waveform shown,  $\theta$  is  $-45^\circ$ .

# RMS value in Power Calculation


It is desirable to have same form of equation for power in both a.c. and d.c. circuits mainly because of

- Convenience
- Consistence

For d.c. circuits, we have  $V_{rms} = V_{dc}$  and  $I_{rms} = I_{dc}$ . So, for both a.c. and d.c., the power in a resistor is

$$P = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

# What is Phasor?

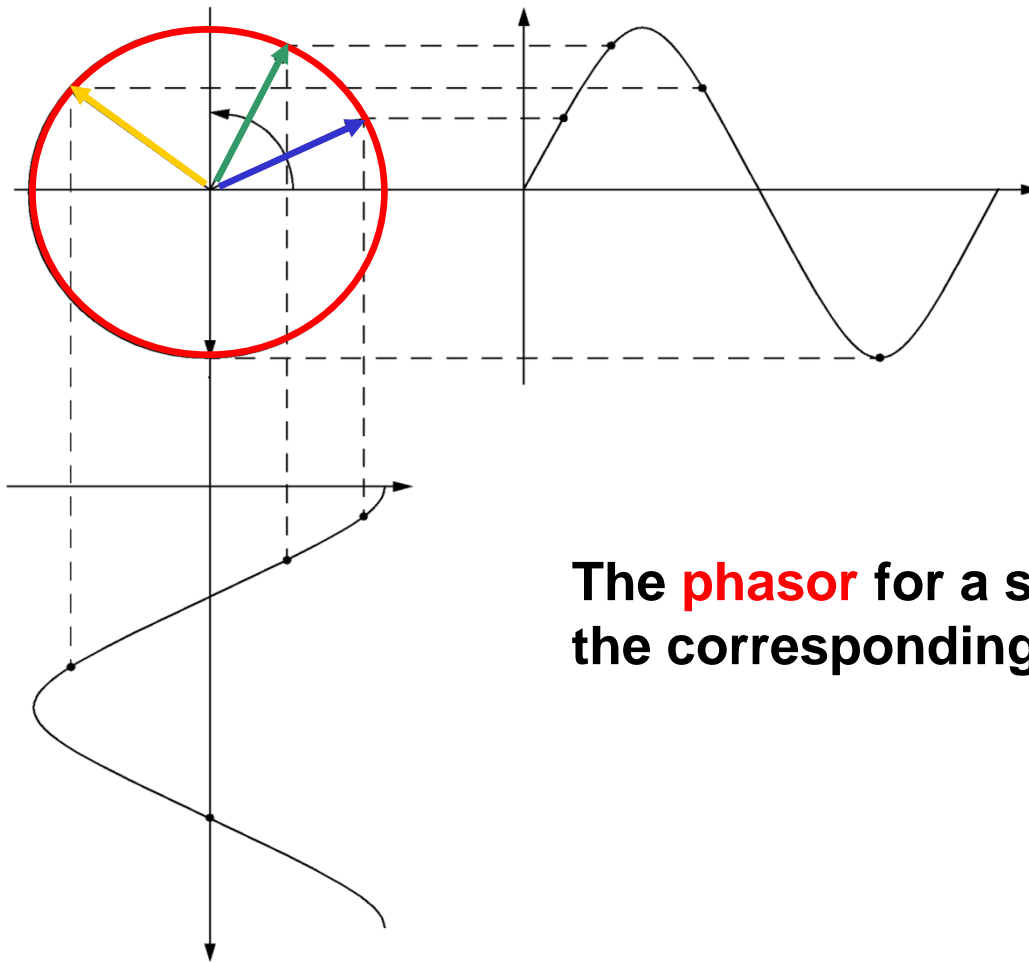

The **phasor** for a sinusoid is a snapshot of the corresponding rotating vector at  $t = 0$ .

## Example 1: Converting sinusoidal time-domain expression to phasor form



$$v(t) = \sqrt{2} \cdot 20 \cos(\omega t - 45^\circ)$$

$$V_{rms} = V_m / \sqrt{2} = 20$$

$$\mathbf{V}_1 = 20 \angle -45^\circ$$
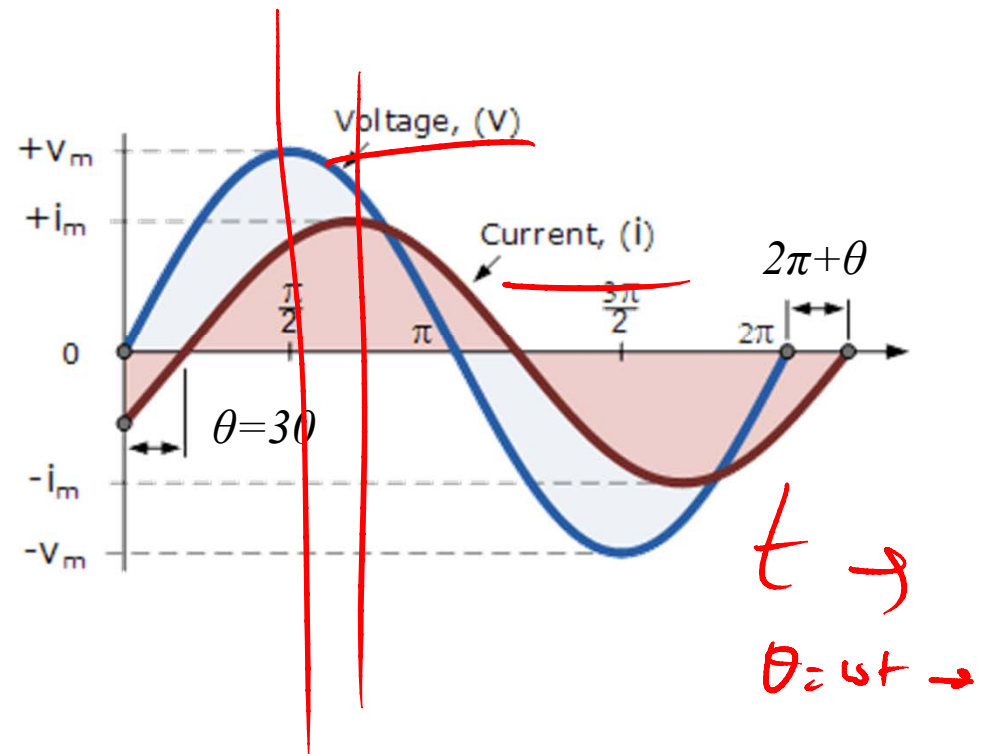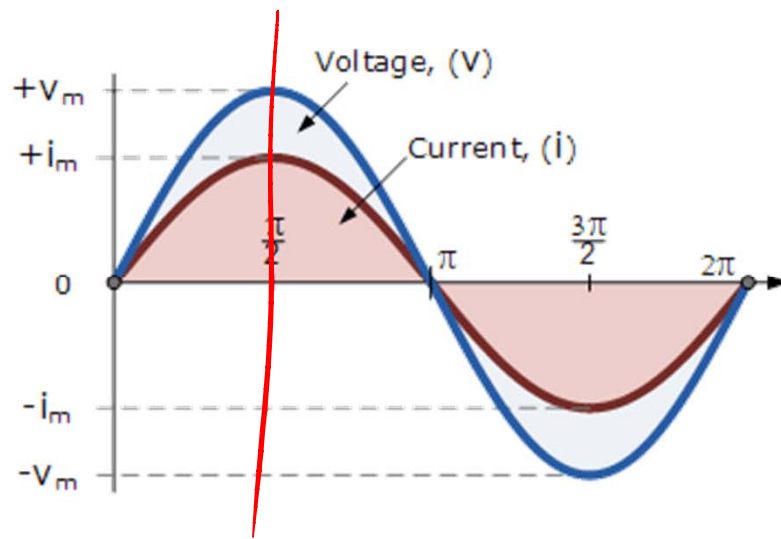
# Phase Relationships

Sometimes when we are analysing alternating waveforms we may need to know the position of the phasor, representing the alternating quantity at some particular instant in time especially when we want to compare two different waveforms on the same axis






# Phase Relationships

To determine phase relationships from a phasor diagram, consider the phasors to rotate counterclockwise.

Then when standing at a fixed point, if  $V_1$  arrives first followed by  $V_2$  after a rotation of  $\theta$ , we say that  $V_1$  leads  $V_2$  by  $\theta$ .

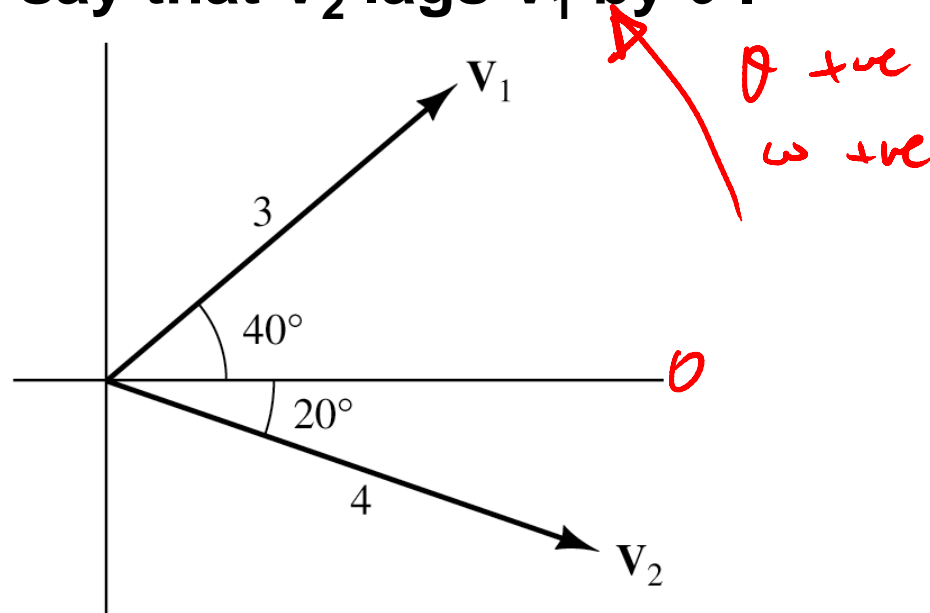Alternatively, we could say that  $V_2$  lags  $V_1$  by  $\theta$ .



Because the vectors rotate counterclockwise,  $v_1$  leads  $v_2$  by  $60^\circ$  (or, equivalently,  $v_2$  lags  $v_1$  by  $60^\circ$ .)

# Impedance for Circuit Components R, L, C

$$R: \quad v = R \cdot i \quad \rightarrow \quad V = R \cdot I$$

$$\boxed{Z = \frac{V}{I}}$$

$$L: \quad v = L \cdot \left( \frac{di}{dt} \right) \quad \rightarrow \quad V = j\omega L \cdot I$$

$$\underline{Z_L = j\omega L}$$

$$C: \quad v = \frac{1}{C} \int i \, dt$$









$$V = \frac{1}{j\omega C} \cdot I \quad \underline{Z_C = \frac{1}{j\omega C}}$$

$$\frac{d}{dt} (\sin \omega t) = \underline{\underline{(\cos \omega t) \times \omega}}$$

$$= \sin(\omega t + 90^\circ) \times \underline{\underline{\omega}} \quad \underline{\underline{j\omega}}$$

$$\int \sin \omega t \cdot dt = -\frac{\cos \omega t}{\omega} = \frac{\sin(\omega t - 90^\circ)}{\omega} \quad \begin{matrix} -j\frac{1}{\omega} \\ \underline{\underline{j\frac{1}{\omega}}} \end{matrix}$$
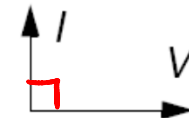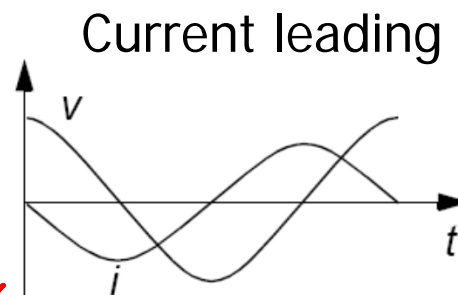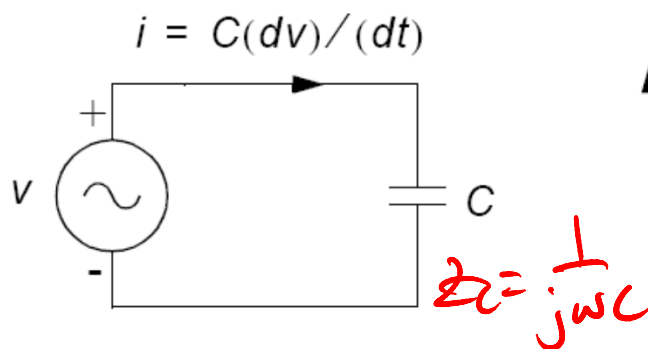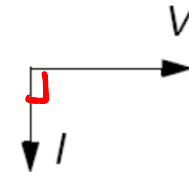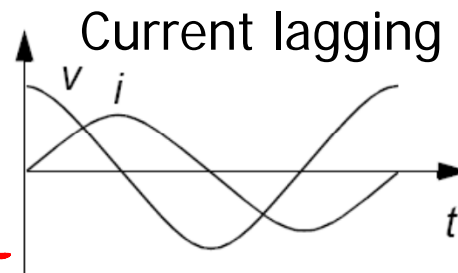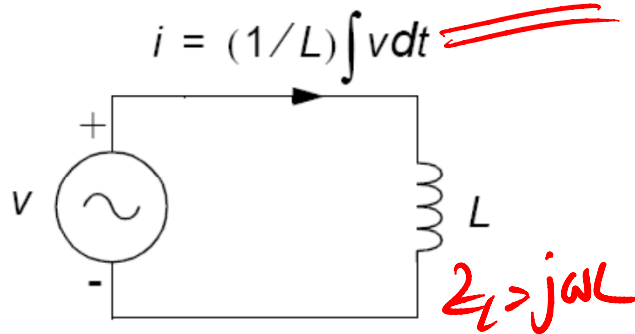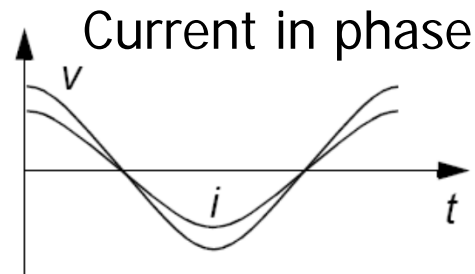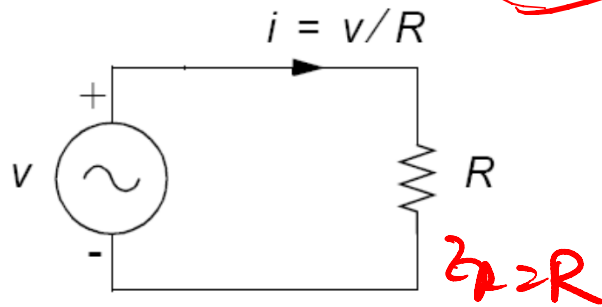
# Summary: Time $\Leftrightarrow$ Phasor domains



## Example 3: Using Phasors to Add Sinusoids

$$v_1(t) = \sqrt{2} \cdot 20 \cos(\omega t - 45^\circ) \quad v_2(t) = \sqrt{2} \cdot 10 \cos(\omega t - 30^\circ)$$

$$\downarrow \quad v_1(t) + v_2(t) = \frac{1}{\sqrt{2}} \times 20 \cos(\omega t - 45^\circ) + \frac{1}{\sqrt{2}} \times 10 \cos(\omega t - 30^\circ)$$

$$V_1 = 20 \angle -45^\circ$$

$$V_2 = 10 \angle -30^\circ$$


$$v_1(t) + v_2(t) \rightarrow \underline{V_1 + V_2 = 20 \angle -45^\circ + 10 \angle -30^\circ}$$

$$= \underline{29.77 \angle -40^\circ}$$


$$= 29.77 / \sqrt{2} \cos(\omega t - 40^\circ)$$

# Equivalent time domain and phasor representations


A.C. circuit with a resistance

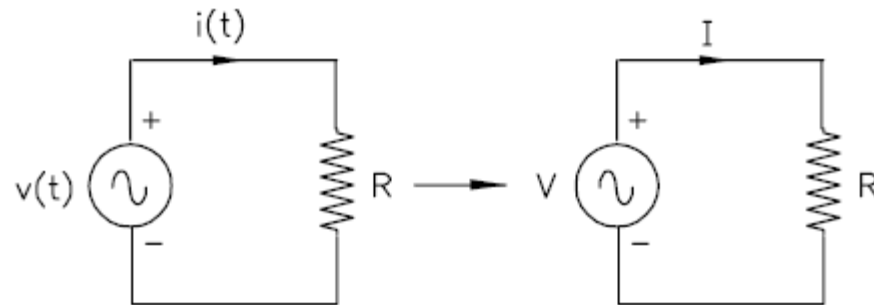

A.C. circuit with an inductance




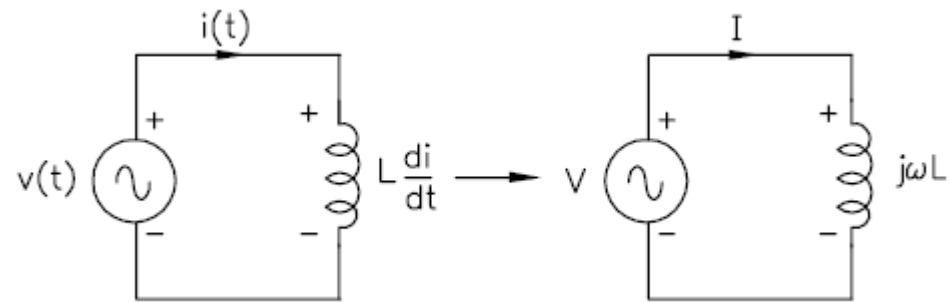


A.C. circuit with a capacitance

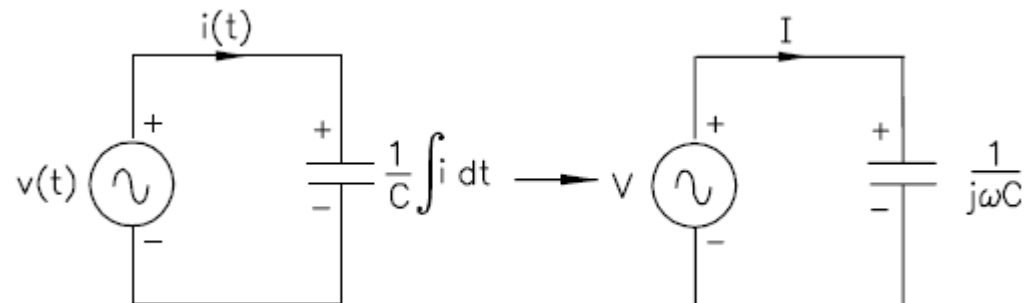

Element	Voltage	Current	Impedance
R	$ V  \angle 0^\circ$	$\frac{ V  \angle 0^\circ}{R}$	$R$
L	$\omega L  I  \angle 90^\circ$	$ I  \angle 0^\circ$	$j\omega L$
C	$ V  \angle 0^\circ$	$\omega C  V  \angle 90^\circ$	$\frac{1}{j\omega C}$

# Complex Impedance

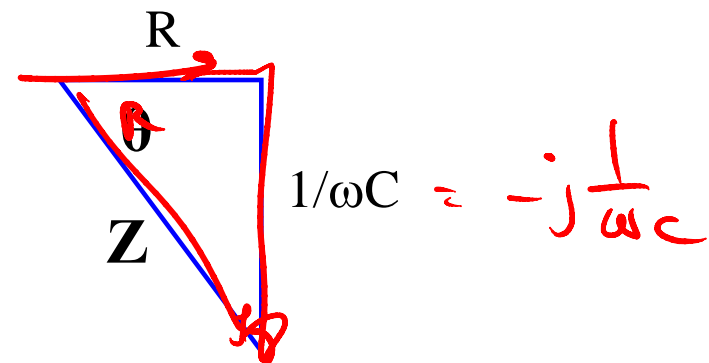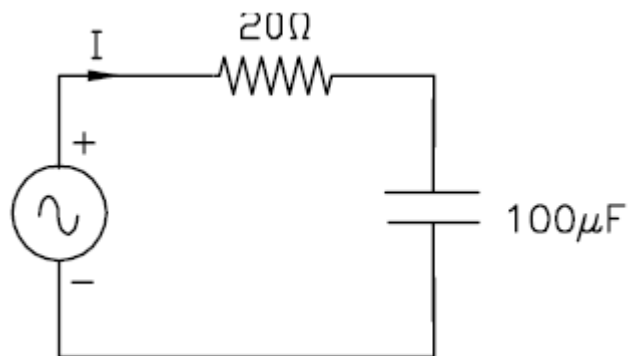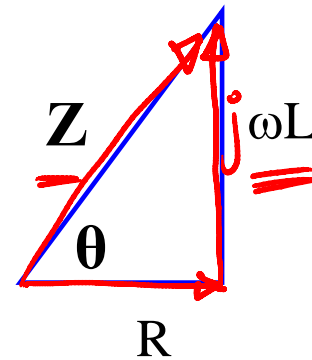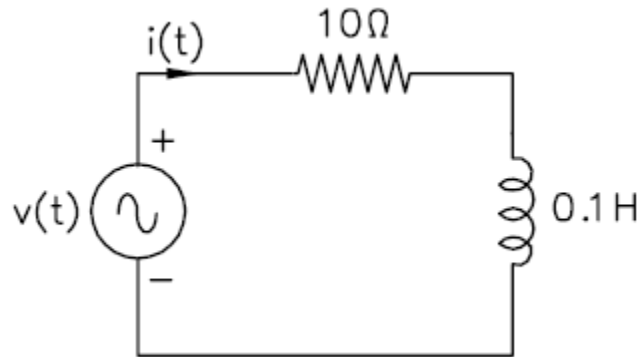

## Class Quiz

\* write Matrix No. and Name

\* Use 1 page per question.

Q1:  $v_1(t) = 5\sqrt{2} \sin(314t + 20^\circ)$ ,  $v_2(t) = 10\sqrt{2} \cos(314t + 40^\circ)$

$v_3(t) = 15\sqrt{2} \cos(314t - 20^\circ)$ ,  $v_4(t) = 5\sqrt{2} \sin(314t + 240^\circ)$

Find : (a) Phasors  $V_1, V_2, V_3, V_4$  (b)  $V = V_1 - V_2 + V_3 - V_4$

(c)  $v(t) = v_1(t) - v_2(t) + v_3(t) - v_4(t)$

Q2 : Find : (a)  $Z_R, Z_L, Z_C$  (b) Over-all impedance seen by the source

(c) Current ( Phasor ) drawn from the source,  $I_S$

(d) Voltage phasors  $V_R, V_L, V_C$ .

(e) Draw phasor diagram showing  $V_S, V_R, V_L, V_C, I_S$ .

$R = 10\Omega, L = 100mH, C = 47\mu F$

